

THE No 1 UK MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

EPE EVERYDAY PRACTICAL ELECTRONICS

www.epemag.co.uk

www.epemag.com

DIGITAL INSTRUMENT DISPLAY FOR CARS FOR A VARIETY OF SENSORS



Amazing Performance!

BUILD OUR "BB"

METAL DETECTOR

WITH JUST FIVE COMPONENTS



Widgy Box

Distortion effects for your guitar

Vol 35 No 6 \$5.95 US \$7.99 CAN
JUNE 2006 PRINTED IN THE UK



Copyright © 2006, Wimborne Publishing Ltd
(408 Wimborne Road East, Ferndown, Dorset, BH22 9ND, UK)

and TechBites Interactive Inc.,
(PO Box 857, Madison, Alabama 35758, USA)

All rights reserved.

WARNING!

The materials and works contained within *EPE Online* — which are made available by Wimborne Publishing Ltd and TechBites Interactive Inc — are copyrighted. You are permitted to make a backup copy of the downloaded file and one (1) hard copy of such materials and works for your personal use. International copyright laws, however, prohibit any further copying or reproduction of such materials and works, or any republication of any kind.

TechBites Interactive Inc and Wimborne Publishing Ltd have used their best efforts in preparing these materials and works. However, TechBites Interactive Inc and Wimborne Publishing Ltd make no warranties of any kind, expressed or implied, with regard to the documentation or data contained herein, and specifically disclaim, without limitation, any implied warranties of merchantability and fitness for a particular purpose.

Because of possible variances in the quality and condition of materials and workmanship used by readers, *EPE Online*, its publishers and agents disclaim any responsibility for the safe and proper functioning of reader-constructed projects based on or from information published in these materials and works. In no event shall TechBites Interactive Inc or Wimborne Publishing Ltd be responsible or liable for any loss of profit or any other commercial damages, including but not limited to special, incidental, consequential, or any other damages in connection with or arising out of furnishing, performance, or use of these materials and works.

ISSN 0262 3617

PROJECTS ... THEORY ...
NEWS ... COMMENT ...
POPULAR FEATURES ...


VOL. 35. No. 6 JUNE 2006

EPE EVERYDAY PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS TODAY INTERNATIONAL

www.epemag.co.uk

EPE Online: www.epemag.com

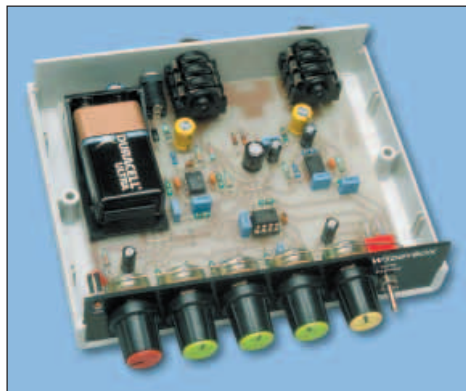


Projects and Circuits

- POOR MAN'S METAL LOCATOR** by Thomas Scarborough 10
Just five components give surprisingly good results
- DIGITAL INSTRUMENT DISPLAY FOR CARS PART 1** by John Clarke 18
Convert analogue instruments to a digital display
- WIDGY BOX DISTORTION EFFECTS FOR YOUR GUITAR** by Peter Smith 30
Great sounds – cheap and easy to build
- INGENUITY UNLIMITED – Sharing your ideas with others** 51
Super Vibration Switch, Simple Sonar
- PHONE RING & TEST** by Terry de Vaux-Balbirnie 56
UK, US and European ring tones, plus a basic test




Series and Features

- PIC N' MIX** by Mike Hibbett 16
Random Number Generation
- TECHNO TALK** by Mark Nelson 26
The Memory Lingers On
- INTERFACE** by Robert Penfold 28
PC Interfacing Software
- TEACH-IN 2006** by Mike Tooley BA 42
Find out how circuits work and what really goes on inside them
Part 8: Digital Electronics: Introducing logic circuits; logic families; logic gates
- CIRCUIT SURGERY** By Ian Bell 65
Op amp Output Capabilities
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 68
VoIP Phones; Video Stars

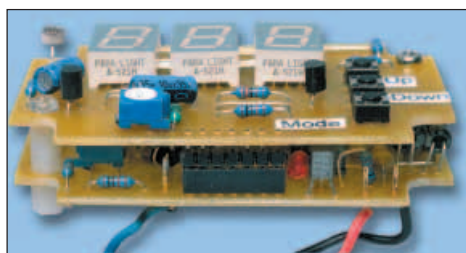

Regulars and Services

- EDITORIAL** 7
- NEWS** – Barry Fox highlights technology's leading edge 8
Plus everyday news from the world of electronics
- CD-ROMS FOR ELECTRONICS** 53
A wide range of CD-ROMs for hobbyists, students and engineers
- SUBSCRIBE TO EPE** and save money 69
- READOUT** John Becker addresses general points arising 71
- DIRECT BOOK SERVICE** 73
A wide range of technical books available by mail order, plus more CD-ROMs
- BACK ISSUES** 76
Did you miss these?
- EPE PCB SERVICE** 78
PCBs for EPE projects
- ADVERTISERS INDEX** 80

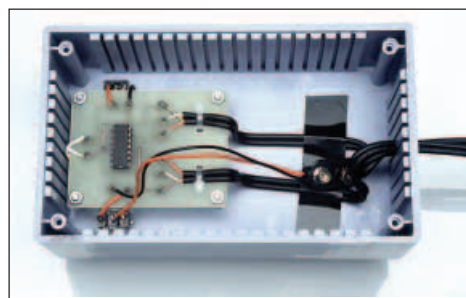

© Wimborne Publishing Ltd 2006. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our July 2006 issue will be published on Thursday,
8 June 2006. See page 80 for details

Readers Services • Editorial and Advertisement Departments 7

EPE EVERYDAY PRACTICAL ELECTRONICS

THE UK's No.1 MAGAZINE FOR ELECTRONICS TECHNOLOGY & COMPUTER PROJECTS

VOL. 35 No. 6

JUNE 2006

Popular

The new format and style *EPE* has proved to be very popular, with many readers being unable to get copies of the first two redesigned issues. Both Jan. and Feb. '06 issues have now completely sold out and we can no longer supply back issues, only reprints of articles. That popularity also shows through in the projects we publish, in particular those for cars and music – with the *Speed Camera Watch MK2* (Nov. '05) being the most popular project we have published in recent years, closely followed by the other car projects and by music related designs.

Last month's *LED Lighting For Your Car* projects have attracted much attention but we must point out that these should not be used to replace normal car stop, side or indicator lamps, they were not designed for that purpose. As discussed in the article most l.e.d.s. have a very narrow emission angle and the designs are not suitable (indeed are illegal) to use as replacements for conventional tail, stop and indicator lamps. Uses were suggested so please don't be misled, our intention was to add to safety, not to make your vehicle illegal and your lighting unsafe!

More

No doubt this issue will also prove popular, with the eagerly awaited *Widgy Box* and our *Digital Instruments For Cars* projects, but please don't feel these are the only areas we cover, next month there is a *PC Infra Red Remote Receiver*, John Becker's PIC-based *Sudoku Unit* plus a *Dirt Cheap High Current Bench Supply* design – something for everyone.

In order not to miss out – like some have already – please place an order with your newsagent or take out a subscription – see pages 67 and 69.

Mike Kenward

AVAILABILITY

Copies of *EPE* are available on subscription anywhere in the world (see opposite), from all UK newsagents (distributed by SEYMOUR) and from the following electronic component retailers: Omni Electronics and Yebo Electronics (S. Africa). *EPE* can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased and downloaded for just \$15.99US (approx £9.50) per year available from www.epemag.com

SUBSCRIPTIONS

Subscriptions for delivery direct to any address in the UK: 6 months £17.50, 12 months £33, two years £61; Overseas: 6 months £20.50 standard air service or £29.50 express airmail, 12 months £39 standard air service or £57 express airmail, 24 months £73 standard air service or £109 express airmail. To subscribe from the USA or Canada see page 69. Online subscriptions, for downloading the magazine via the Internet, \$15.99US (approx £9.50) for one year available from www.epemag.com. Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subs. Dept., Wimborne Publishing Ltd, 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £7.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery – more for overseas.

Payment in £ sterling only please. Visa, Amex, Diners Club, Maestro and MasterCard accepted. Send, fax or phone your card number, card expiry date and card security code (the last 3 digits on or just under the signature strip), with your name, address etc. Or order on our secure server via our UK web site. Overseas customers – your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editorial Offices:

EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown,
Dorset BH22 9ND
Phone: (01202) 873872. Fax: (01202) 874562.

Email: enquiries@epemag.wimborne.co.uk

Web Site: www.epemag.co.uk

EPE Online (downloadable version of *EPE*): www.epemag.com

EPE Online Shop: www.epemag.wimborne.co.uk/shopdoor.htm

See notes on *Readers' Technical Enquiries* below – we regret technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY PRACTICAL ELECTRONICS ADVERTISEMENTS
408 Wimborne Road East, Ferndown, Dorset BH22 9ND
Phone: 01202 873872 Fax: 01202 874562

Email: stewart.earn@wimborne.co.uk

Editor: MIKE KENWARD

Consulting Editors: DAVID BARRINGTON
JOHN BECKER

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

General Manager: FAY KEARN

Editorial/Admin: (01202) 873872

Advertising Manager:

STEWART KEARN (01202) 873872

On-Line Editor: ALAN WINSTANLEY

EPE Online (Internet version) **Editors:**
CLIVE (MAX) MAXFIELD and ALVIN BROWN

READERS' TECHNICAL ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**. We are not able to answer technical queries on the phone.

PROJECTS AND CIRCUITS

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

A number of projects and circuits published in *EPE* employ voltages that can be lethal. **You should not build, test, modify or renovate any item of mains powered equipment unless you fully understand the safety aspects involved and you use an RCD adaptor.**

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; readers should check local laws.



REPAIRING BROKEN CSS

DVD Encryption Security Has Been Hacked

– By A Schoolboy! Barry Fox reports

BRAD Hunt, Chief Technical Officer of the Motion Picture Association of America – which speaks for Hollywood – admitted to the International Recording Media Association conference in California recently that “CSS is broken”. CSS is, of course, the encryption system used to stop people making digital copies of DVDs. But it was quickly hacked by a schoolboy and his DeCSS program is widely used to let legitimate copy programs make illegitimate copies of DVDs.

“There’s work going on in this area”, Hunt said, but would give no details on how the MPAA hopes to fix broken CSS. The encryption cannot be changed without making future discs unplayable on existing DVD players – which is the reason why the Advanced Access Content System built into both new blue laser systems (Blu-ray and HD-DVD) uses renewable keys for discs and players. A recent patent filed round the world by Bradley Thomas Collar

of Warner Bros gives one clue to what the MPAA may have in mind (WO 2005/098832). The patent exploits the technical trick used by some deCSS copy programs to justify the legal argument that owners of DVDs should be able to make one digital clone copy, just as the SCMS system used to protect CDs permits one digital copy.

“The reasoning (albeit a flawed one) is that one archival copy should be allowed, but not rampant copying”, says the patent. The DVD archive copy programs (like the now deceased DVD X-Copy and many others that have crept onto the market) put a file on the copy disc that identifies it as an “archive” copy. The program then looks for this file whenever it is asked to make a copy. If there is no archive file, the copy is made; if there is an archive file, no copy is made.

Warner is patenting the idea of putting an archive file on original discs. So any copy

software that argues legality by refusing to copy a copy, will also refuse to copy an original disc. Another recent patent (US 20050232612), this time from Disney, claims the idea of putting many different trailers and promotional adverts on a DVD, along with “random” or “shuffle play” software. So a few of the promos play every time the disc is played, but they are different each time, or in different order.

The idea seems sensible. But what makes the patent especially interesting is the way it is worded. Referring to the current situation where tapes and discs contain a few promos that insist on playing every time you want to watch the movie, Disney’s patent admits: “You must endure the same previews every time you play the movie, or be forced to “fast forward” through the previews to reach the actual movie ... (this) detracts from the enjoyment ... becomes annoying and has a detrimental effect on the viewer.”


Miniature AM Receiver Module

The new AM-HRR30 “super-regen” AM receiver module from RF Solutions has a compact hybrid construction and is approximately half the size of other hybrid modules on the market. With overall dimensions of just 25.4mm × 8.9mm × 4mm, the AM-HRR30 can be easily integrated into customer applications. Its robust electrical and mechanical construction makes it especially useful in portable devices and other small form factor pieces of equipment.

The AM-HRR30 is able to capture undecoded data from any AM transmitter (for example RF Solutions’ AM-RT4/5 range). The module has a receiving range of up to 50 metres and a data rate of up to 4800 bits/sec. The new devices can be supplied with operating frequencies between 300MHz and 450MHz. Standard parts are available with frequencies of either 315MHz or 433MHz.

Supply current for the AM-HRR30 is 3mA maximum. For applications where ultra-low power consumption is of paramount importance, RF Solutions offers the AM-HRR60 which draws a supply current of just 0.5mA.

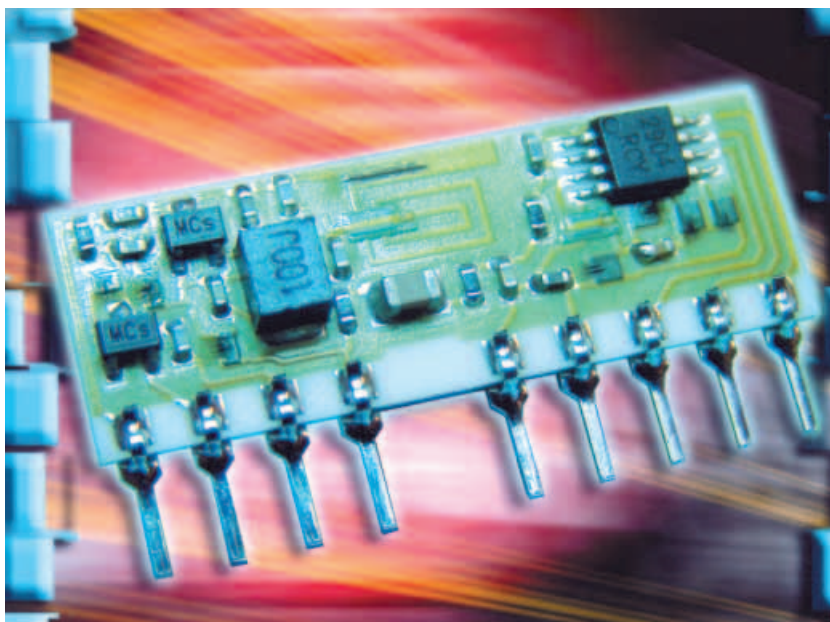The new modules specify very high frequency stability over their wide –25°C to +80°C operating temperature range. The durable construction of the AM-HRR30 ensures that its performance is maintained



even in applications where it is subjected to mechanical vibration and manual handling. A unique patented laser trimming process gives a highly accurate on-board inductor that conveniently alleviates the need for any adjustable components in the design.

The ETSI300-220 compliant AM-HRR30 features a CMOS/TTL compatible

output and requires no radio licence to operate. The only connections required are to an antenna and a 5V power supply.

Further information, contact: R.F. Solutions, Dept EPE, Unit 21, Cliffe Ind. Estate, South Street Lewes, East Sussex, BN8 6JL. Tel: +44 (0) 1273 898000. Fax: +44 (0) 1273 480661. Web: www.rfolutions.co.uk. Email: sales@rfolutions.co.uk.

Marconi Exhibition

A special exhibition at the Museum of the History of Science is being held to mark the acquisition by the Museum and the Bodleian Library of the extraordinary Marconi Collection. The exhibition covers the history of radio from Marconi's early demonstrations in the 1890s to the beginning of regular public broadcasting in the 1920s.

This is the story of a technology that has shaped the modern world. At first, the major purpose for "wireless" seemed to be for sending individual messages in Morse code, with much greater flexibility than the established telegraph system, which relied on connections by wires. "Wire-less" would have military applications and would be especially valuable for communications at sea. However, there was nothing to stop people "listening in" and, with the coming of voice messages, enthusiasm grew for a completely different concept in communication – broadcasting.

The exhibition concentrates on the dramatic and memorable events in the early story:

- Marconi's celebrated early demonstrations, including cross-Channel signals
- The achievement of a trans-Atlantic signal in December 1901
- The *Titanic* disaster and the use of radio to rescue survivors
- The development of radio in World War One
- The birth of broadcasting, up to the foundation of the BBC

These are illustrated by original instruments and documents of outstanding interest, including:

Form No. 1-100-121111
The Marconi International Marine Communication Company Ltd.
WATERSIDE HOUSE, YORK BUILDINGS, ADELPHI, LONDON, W.C.
No. 111111 OFFICE 19
Prefix Code Words
Office of Origin
Service Instructions
Charges to Pay:
Marconi Charge
Other Line Charge
Delivery Charge
Total
Office sent to Time sent By whom sent
To: Captain Calverton
J. Marconi
J. P. Marconi
READ THE CONDITIONS PRINTED ON THE BACK OF THE FORM
RECEIVED BY THE OFFICE OF THE MARCONI INTERNATIONAL MARINE COMMUNICATION COMPANY LTD. LONDON, W.C.

• Apparatus from Marconi's very first demonstrations, including the trans-Atlantic signal

• Famous original experimental notebooks and patents

• "Marconigram" messages sent from the *Titanic* and between ships in the vicinity (see above) after the fatal collision; this material has not been displayed before and is of great public interest

• Early radios and broadcast equipment, including the microphone used in Dame Nellie Melba's celebrated recital on 15 June 1920, the first live public entertainment broadcast.

The exhibition was opened on 24 April by Lord Patten of Barnes, Chancellor of the University of Oxford, and Princess Elettra Marconi, daughter of Guglielmo Marconi.

The exhibition dates are 25 April to 1 October 2006, Tuesday to Saturday 12pm to 4pm, Sunday 2pm to 5pm, admission free. There is also a range of special events.

For further information, please contact Dr Jim Bennett, tel: 01805 277281 (or 277280), email: jim.bennett@mhs.ox.ac.uk.

The Museum's website is at:
www.mhs.ox.ac.uk.

PIXAR EXHIBITION

The Science Museum has opened a new exhibition examining the work of Pixar Animation Studios' artists, bringing together 250 drawings and paintings, 50 sculptures plus computer generated multimedia artworks. All of these works demonstrate the rich creativity behind the development of the studio's technologically advanced films.

Pixar: 20 Years of Animation, opened on 1 April 2006 and provides artistic and technological insight into the studio's hugely successful movies, ranging from *Toy Story*, *A Bug's Life*, *Toy Story 2*, *Monsters, Inc.*, *Finding Nemo*, *The Incredibles* and the forthcoming Disney presentation of the Pixar film *Cars*, each of which are revolutionary films in animation.

To accompany the exhibition, the Museum will run a series of events for a range of audiences, from workshops for seven to 14 year olds, to talks with animators, directors, producers, Oscar winners and nominees, revealing the details and secrets of their work. Jon Tucker, Head of the Science Museum said:

"This exhibition will give our visitors a unique glimpse into Pixar Animation Studios, one of the most creative film studios in the world".

The exhibition will also look at the history of animation in film, using objects from the Science Museum's collection, including original Victorian magic lanterns,

zoetropes, cameras and early pieces of animated film.

The exhibition has an exclusive 10-week run at the Science Museum until 10 June 2006. Admission: adult £9; child/student £7; Educational groups £4 per person; family: 2 adults + 1 child £20; 2 adults + 2 children £27. Exhibition tickets can be pre-booked on 0870 870 4868 or via the museum website.

Further information on the exhibition and all accompanying events can be found at www.sciencemuseum.org.uk/pixar.

Radio-Electronics Website

Ian Poole, author of our earlier *New Technology Update* column, tells us that his website www.radio-electronics.com now serves over 200,000 pages a month and is continuing to grow. Coupled with this, the site had over 60,000 visitors, proving its popularity. The site, which is run and edited by Ian, of Adrio Communications Ltd, aims to provide concise, useful overviews and tutorials in an easy to read form.

The website now has well over 300 pages of full content, making it one of the largest on the Internet and a significant resource of useful information. It covers a wide range of radio and electronics topics ranging from receiver technology and phase-locked loops, through antennas, feeders, circuits and components to the latest technologies including cellular telecommunications, Wi-Fi, Bluetooth, UWB and more. There are also some pages of interest covering radio and electronics history.

The site has been in existence for several years and over this time many positive comments have been received from a variety of users.

RAPID'S NEW PRODUCTS

We have received the latest edition of Rapid Electronics' *New Products Focus* publication. This is devoted to Rapid's new products, but it now also incorporates Rapid's *Focus* magazine. As such it also has a variety of feature articles of general interest, as well as product information.

Rapid are one of the industry's leading components distributors, and no hobbyist workshop should be without a copy of their main catalogue, of which the 2006 edition is now available.


For more information, contact Rapid Electronics Ltd., Dept EPE, Severalls Lane, Colchester, Essex CO4 5JS. Tel: 01206 751166. Fax: 01206 751188. Email: sales@rapidelect.co.uk. Web: www.rapidelectronics.co.uk.

EOCS Magazine

The April '06 issue of the *Electronic Organ Magazine* has been received from the Electronic Organ Constructors Society (EOCS). If you are interested in electronic organs and such, contact: Treasurer EOCS, Dept EPE, 2 Boxhill Nurseries, Tadworth, Surrey KT20 7JF. Email: Treasurer@eocs.org.uk. Web: www.eocs.org.uk.

By
Thomas
Scarborough

Poor Man's Metal Locator

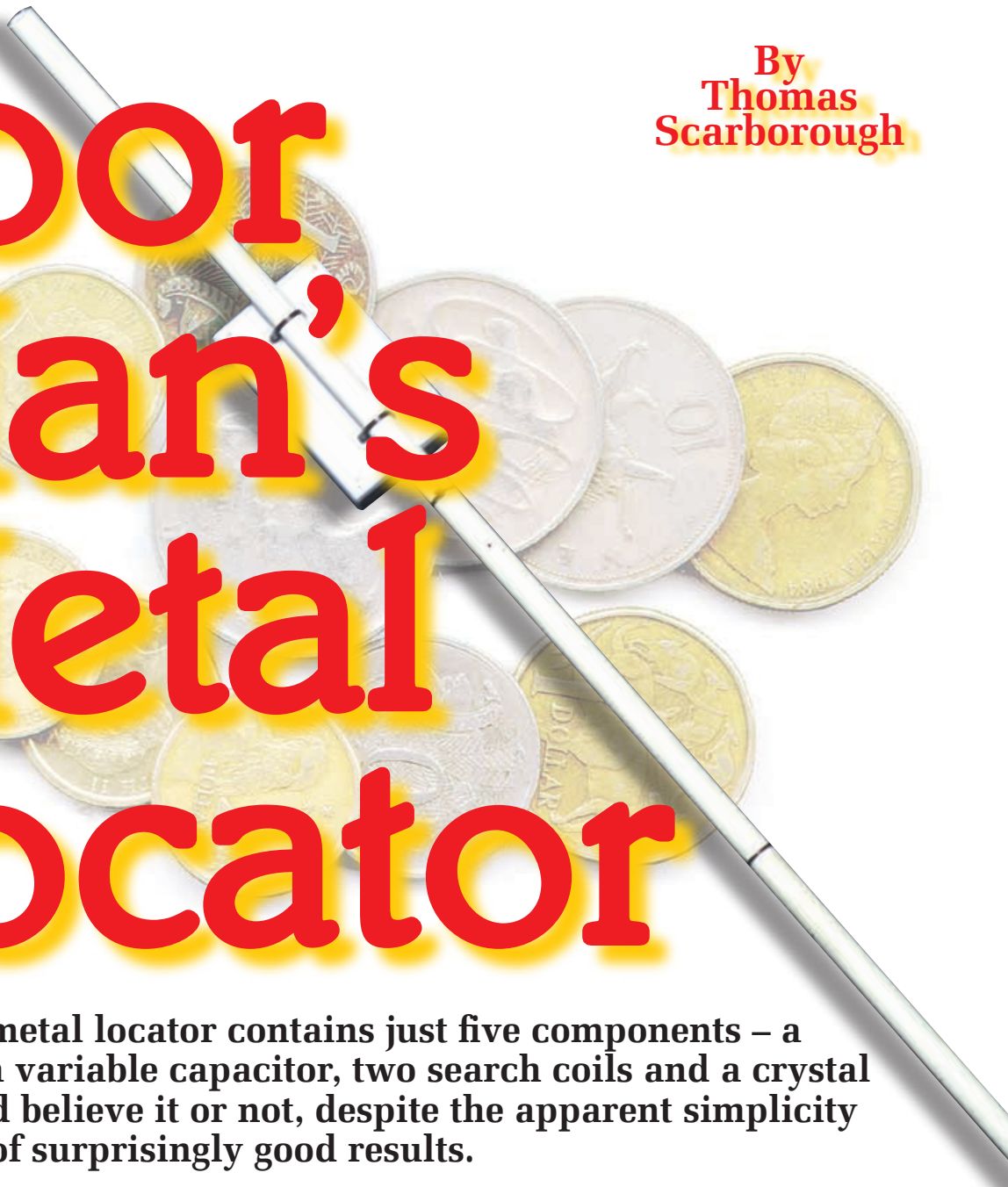

This unique metal locator contains just five components – a low-cost IC, a variable capacitor, two search coils and a crystal earpiece. And believe it or not, despite the apparent simplicity it is capable of surprisingly good results.

THIS CIRCUIT represents a genre of metal locator. Although it borrows from other kinds of locators/detectors, its basic principle of operation is different.

And while this may seem to stretch one's credulity, the performance matches that of a budget Induction Balance (IB) detector. Build it – and you will see! This design is even more simple than the original Beat Balance design published previously (*EPE* May 2004).

During testing, it detected an old English penny at 150mm (6") in air. However, I would only put my neck on the block for 125mm (5"), since a number of factors influence sensitivity.

This locator may therefore represent the writing on the wall for budget IB types and even puts paid to most of the advantages (the few remaining ones) of Beat Frequency Operation (BFO) detectors.

Overview

Instead of using a search and a reference oscillator (as in the BFO type), or transmit and receive coils (as in IB), this detector uses two transmitters (or search oscillators) with IB-style coil overlap.

As will be seen from Fig.1 and our photographs, these are extremely simple in design. Each oscillator comprises just one-quarter of a common

quad op amp IC plus the search coil!

The frequencies of the two oscillators are then mixed (in similar fashion to a BFO) to produce an audible heterodyne.

On the surface of it, this design would seem to represent little more than a twinned BFO metal locator. However, what makes it different above all else (and significantly increases its range) is that each coil modifies the frequency of the adjacent oscillator through inductive coupling. This introduces the "balance" that is present in an IB metal locator and boosts sensitivity well beyond that of a BFO.

Beyond this, all that is required is a means to control the mixer output

frequency, so that the metal locator can be tuned. This could be accomplished in a number of ways but the method chosen here is a variable capacitor (a standard 100pF AM radio tuner) wired between the two oscillator outputs.

Since the concept borrows from both BFO and IB, we give a nod to each of these by calling the principle “Beat Balance”.

Characteristics


The main characteristics of beat balance (BB) are as follows:

- Depending on the way it is designed, a BB metal locator potentially offers the same sensitivity as IB.
- It requires no receiver amplifier or level detector, thus vastly simplifying design and reducing cost. The present circuit uses just two main components, while matching the performance of a budget IB metal locator (which would probably have 10-20 parts).
- Both search oscillators are identical, therefore BB offers high immunity to voltage and temperature variations. This obviates the need for compensation circuits, including voltage regulation.
- Each search coil has the opposite response to metal, thus BB has a high degree of immunity to ground mineralisation. At the same time, it offers good discrimination at the point where the two search coils overlap

The circuit

The design is based on the simplest of inverter oscillators.

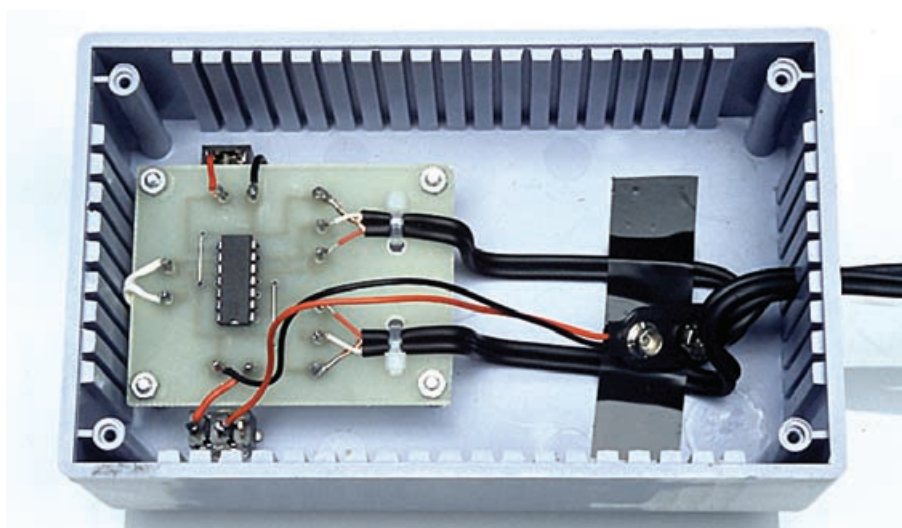Let us focus first on IC1a. Since an inductor resists rapid changes in voltage (called reactance), any change in the logic level at IC1a's output (pin 1) is delayed during transfer to inverting input pin 2. An approx. 8V/ μ s slew rate further delays switching



This view inside the box shows the WHOLE circuit (with the exception of the coils, of course, and the tuning capacitor hidden under the PC board).

of IC1a, thus setting up a rapid oscillation.

One end of the search coil is further wired to the non-inverting input (pin 3), which stabilises operation. While pin 3 could be left “floating”, this would be a less satisfactory arrangement.


Since different ICs have different slew rates, as well as different input impedances, they are unlikely to work in this circuit. However, the TL074CN IC is widely available and there should be no sourcing problems.

The search coil is a critical part of the oscillator and needs to be suitably

designed to achieve oscillation and to obtain the required frequency.

While this frequency needs to be high, it should not be so high that noise or instability are introduced. Both the characteristics of IC1 and the inductance of the coil influence oscillator frequency, which lies around 260kHz without a Faraday shield. The Faraday shield approximately doubles the inductance of the coil, thus roughly halving the frequency.

IC1b is wired in exactly the same way as IC1a, except that its search coil is connected in opposite phase.

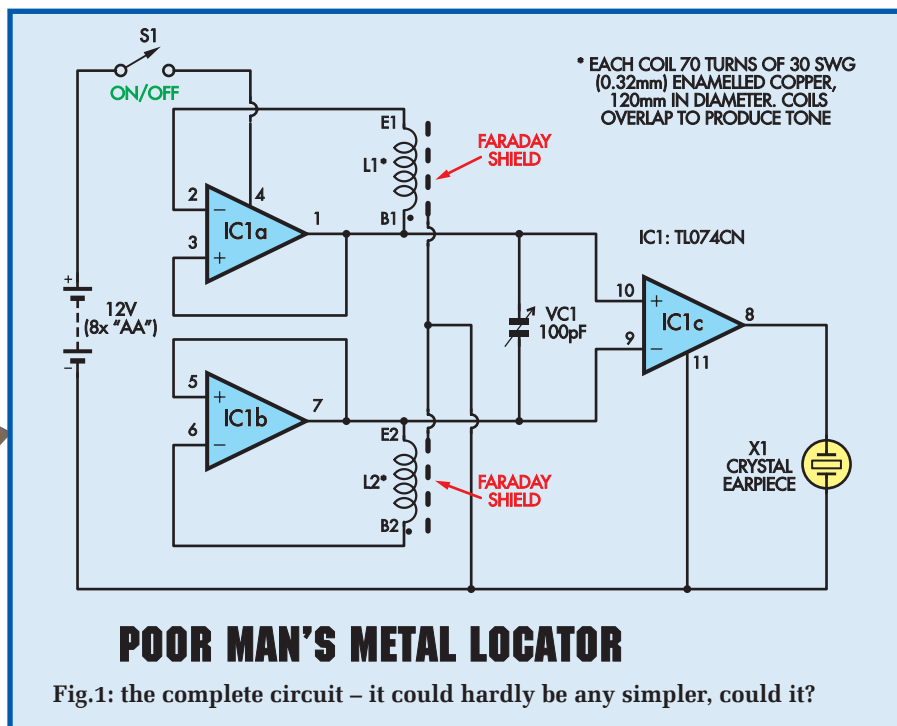

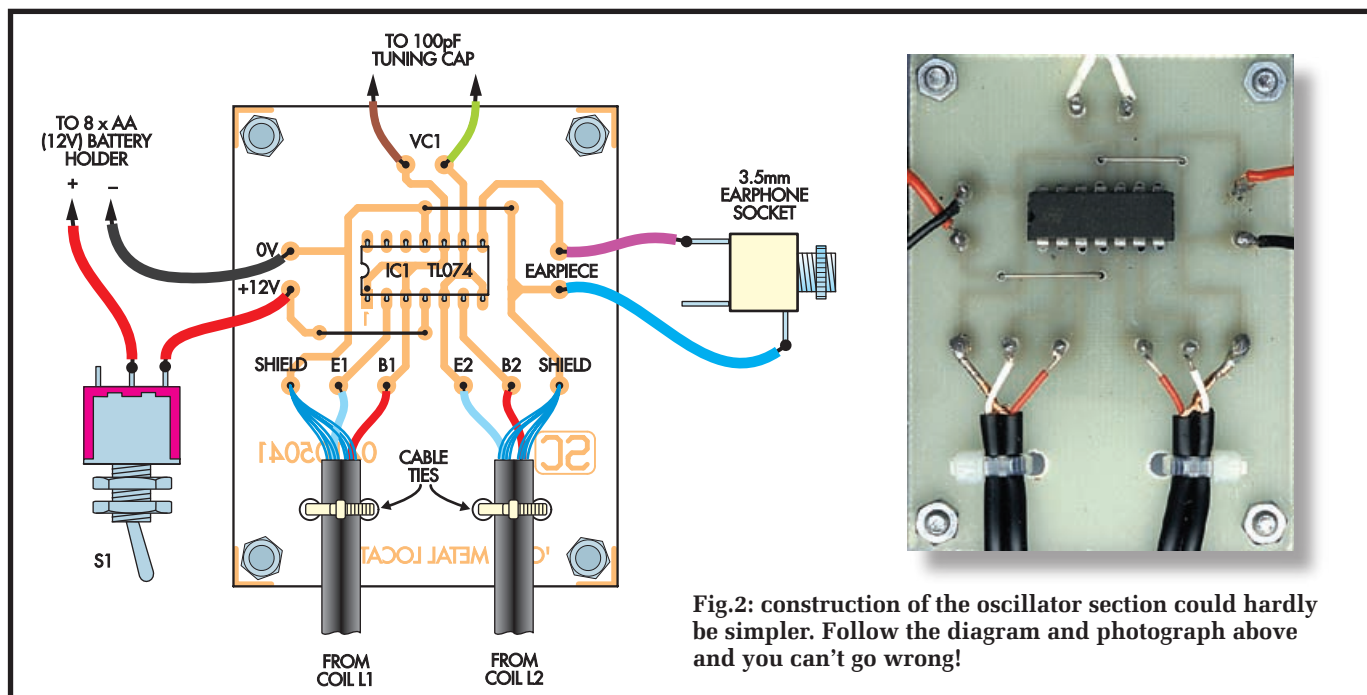


Fig.2: construction of the oscillator section could hardly be simpler. Follow the diagram and photograph above and you can't go wrong!

As the search head is swept over the ground, the presence of metal increases the inductance of L1 and then L2, or vice versa, thus bringing about a dip in the oscillator frequencies. A third op amp, IC1c, is used to mix the output of the oscillators, thus creating an audible difference frequency, or beat frequency.

This leads us to the one distinctive feature of BB. Not only does the presence of metal alter the frequency of a search oscillator but as in the case of IB, it also influences the adjacent coil. In fact, both coils influence each other through mutual induction, thus greatly enhancing the sensitivity of the system.

Beyond this, we only need to find a method of tuning the metal locator. This is achieved using variable capacitor VC1, which further couples the two inductors (the search coils), thus offering a means of controlling balance. Almost any variable capacitor should work in this position, although it should preferably have a smaller value; eg, 47pF to 100pF. A small value capacitor (eg 47pF) can be wired in series with VC1 to reduce a larger value.

A crystal earpiece is used for sound output. While a piezo sounder may be used (without integral electronics), this is not likely to offer good volume. If the volume in the earpiece is too high, use a suitable series resistor to reduce it. An inductive sounder or

earpiece is not recommended, because it could overload IC1c.

Current consumption is around 15mA. Therefore an 8 x AA battery pack should last around 70 hours.

Construction

There's so little on the PC board that it would be difficult to make a mistake. OK, so you could put the IC in back-to-front, likewise the search coils' starts and ends could be inadvertently swapped. Apart from that, there's precious little to worry about.

Fit the 12 stakes to the PC board and solder them into place, then solder the two jumper wires as shown. Normally we would say use resistor lead cutoffs for this – but there aren't any! You'll have to use some tinned copper wire instead.


Now comes the challenge of populating the PC board! Since this is a

sensitive, high-frequency circuit, I would recommend that IC1 be soldered directly to the PC board (ie, not socketed). So long as you insert this component the right way round, there would appear to be little to go wrong! The TL074CN is a fairly "tough bird" – but be reasonably quick with the soldering iron.

Wire up the variable capacitor VC1, the socket for the crystal earpiece and the battery and switch (carefully note the polarity of the battery leads – an error here could destroy the circuit). It's usual to insert the on-off switch in the positive battery lead. Some battery holders have solder tags, others (such as the one we used) need a 9V battery snap to connect them. Again, watch the polarity!

Now mount the on-off switch and the jack socket (for the crystal earpiece) on the case. I used long bolts to clamp

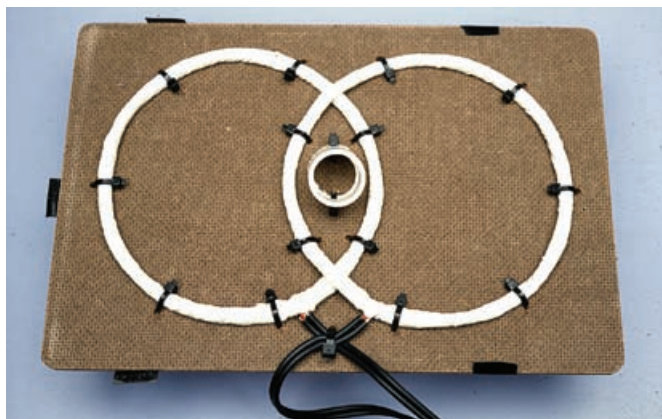Two overlapping coils are wound using 30SWG wire and fastened to a non-metallic base. Figure-of-8 screened microphone cable connects the coils to the oscillator.



VC1 underneath the PC board and found this an easy and effective way of fixing the variable capacitor to the case. Use a slice of non-conductive rubber to isolate VC1 from the back of the PC board.

Next, wind the two search coils. They are 70 turns of 30SWG (0.315mm) enamelled copper wire on 120mm diameter formers. Faraday electrostatic shields are essential for circuit stability. These are connected to 0V and should use balanced (figure-8) screened microphone cable. Winding of the coils is not critical and a little give and take is permissible. However they should be as close as possible to identical.

Wind the coils around the formers, temporarily holding them together by passing stubs of insulating tape under them and pressing them together over the top. Once you have wound the coils, bind them tightly with insulating tape around their entire circumference. Scrape the enamel off the ends of the coils' enamelled copper wires to solder them to the microphone cables.

Now add Faraday shields. Prepare some long, thin strips of aluminium or tin-foil. Twist a 100mm length of bare wire around each coil, over the insulating tape. This wire provides electrical contact with the foil and is soldered to the microphone cable screens.

Beginning at the base of the bare wires, wind the foil around the circumference of the coils, so that no insulating tape is still visible under the foil – but the foil should not complete a full 360°.

Leave a small gap (say 10mm) so that the foil does not meet after having done most of the round. Now again tightly bind the coils with insulating tape around their entire circumference.

Attach the coils to the circuit by means of the specified microphone

Parts List – Poor Man's Metal Locator

- 1 PC board, code 570 available from the *EPE PCB Service*, 51 x 64mm
- 1 plastic case, 150 x 90 x 50mm
- 1 TL074CN quad op amp (IC1)
- 1 10-100pF variable (tuning) capacitor, with knob
- 1 crystal earpiece
- 1 3.5mm mono earphone socket
- 1 8 x AA battery holder and batteries
- 1 battery snap (if required by holder)
- 1 SPST power switch
- 55m (approx.) 30SWG enamelled copper wire
- 2 lengths twin shielded balanced microphone coax (figure-8), approx. 2m long hookup wire
- 2 20mm lengths tinned copper wire (for PC board links)
- 2 lengths of aluminium foil, approx. 20mm wide (for shield)
- 1 length PVC conduit to suit (handle)
- 4 20mm M3 screws and nuts
- Suitable cable ties
- Clear polyester resin

cables, being careful to identify the beginning and end wires correctly as shown. If these are not correctly identified, there could be a 20% loss of sensitivity. The Faraday shields should be connected to the cable screens and to 0V on the PC board as shown.

Hardware

The "hardware" construction is just as simple as the rest of the design. The two search coils are fixed to a plate of hardboard or Masonite, with a single PVC electrical conduit shaft

attached. The control box, containing all of the electronics apart from the coils, attaches to the shaft via a pair of cable ties.

The top of the shaft is then held in the hand just above the control box, while its upper length rests against the back of one's forearm.


Use a stiff, non-metallic plate for the search head. Hardboard or Masonite is both stiff and easy to work with (I cut up an old Masonite clipboard for the purpose). Before the coils (or anything else) are attached to the baseplate, their best operating position needs to be determined.

Begin by placing the two coils on the search head plate, directly on top of one another (that is, "meshed"), with their beginning and end wires positioned as shown. Turn VC1 to its mid-position. Switch the detector on, then slowly move the coils apart.

When the coils have all but been separated from one another, a tone will be heard in the crystal earpiece. Adjust the coil positions so that this is a fairly low tone – then drill holes and use cable ties (several for each coil) to fasten them in this position on the plate.

Once the cable ties have been tightened, carefully bend the coils until a low tone is again heard in the crystal earpiece. To lower the tone, create a greater overlap of the two coils (ie, a larger segment in the middle), and vice versa.

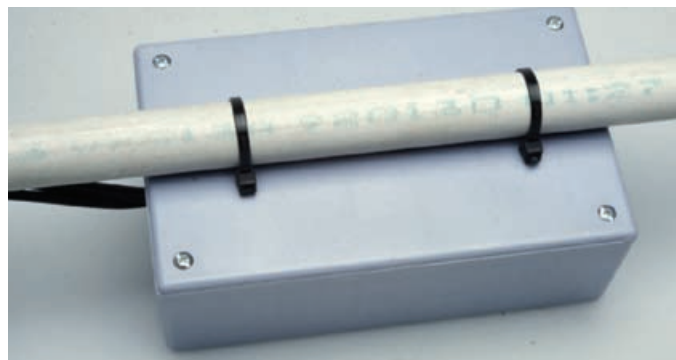To construct a shaft, saw the end off a length of PVC piping at a 25° angle. Drill holes through the pipe close to its bottom end and holes through the centre of the search plate. Then bind the pipe to the search plate with cable ties. The pipe (or shaft) will later be fixed permanently to the search plate with clear polyester resin (see photographs).



The lid is secured to the PVC pipe by means of a couple of cable ties. When these are pulled tight, they really grip well! Then the lid (which is effectively now the base) is screwed onto the box – and presto!



The “works” box (left) is mounted near the top of the PVC tube. This view shows the front of the box, with the earpiece socket, tuning capacitor and on/off switch. We haven’t put a fancy label on this project – it would sort of ruin the effect, wouldn’t it? Besides, the label would be on the underside. At right is the coil end, showing how it mounts to the PVC tube.



The two coils need to be set rigidly in position on the search head, so that they will not move even slightly when the metal locator is in use. I would recommend that they be potted in clear epoxy resin, which is available from most hardware stores, together with the necessary hardener or catalyst.

A section of one coil should be left exposed where the two coils intersect, so as to enable final fine adjustment. This section of coil may be temporarily protected with Blu-Tac.

Be sure to plug the holes beneath the search head before pouring the resin, since it is very runny and sticks faster than many glues! The detector’s PVC shaft is bound to the search head with the resin.

I tied the control box to the shaft with cable ties and used a little all-purpose glue to assist. Cable ties were further used to bind the cables to the shaft. No hand grip was attached to the prototype but the shaft was kept long at the top, so as to rest against the back of my forearm as I gripped the shaft with my hand.

Checking it out

Once construction is complete and everything checked, switch on and tune VC1 until a clear difference

frequency or heterodyne is heard in the crystal earpiece. This should ideally be a low tone of just a few tens of Hertz. It will be found that sensitivity is dependent to some extent on tone and some experimentation will yield the best frequency. If necessary, further adjust the coils, moving them further apart if the circuit is silent, or closer together if the frequency is too high.

Bring a metal item close to the coils. It will be found that one coil causes the tone in the crystal earpiece to rise, while the other causes it to fall, with the overlapping segment offering discrimination between ferrous and non-ferrous metals.

The detector should pick up a large coin (eg, 50p) at up to 150mm in air (125mm is a sure bet), while large metal objects (eg, a cake tin) will be detected at half a metre. At close range, it is capable of picking up a pin. When in use, hold the search head close to the ground, sweeping it to and fro. Unlike IB, the two coils give opposite responses to metal, which one soon becomes accustomed to.

While the detector is unusually stable, readjustment by means of VC1 will inevitably be required, particularly immediately after switch-on. **EPE**

The Patent That Came Close – But No Cigar!

US Patent 4,196,391 of 1980, by Harold J Weber, was a good piece of original thinking that makes fascinating reading. It came so close to Beat Balance – but no cigar!

The patent describes a metal locator which uses two transmitters, as does ours, balanced by a variable capacitor. However, the patent seeks “least interaction between the inductors”, while ours is almost entirely dependent on such interaction.

In the patent, a variable capacitor is used to balance the frequencies of the two transmitters. Ours, on the other hand, uses variable capacitor VC1 to obtain a beat frequency.

The patent mixes the two transmitter frequencies with a third frequency from a Beat Oscillator. The purpose of this is to provide binaural location of metal objects, which is the “primary object” of the patent. Ours obtains an audible heterodyne by mixing the two transmitter frequencies directly, its primary object being to boost sensitivity.

Harold J. Weber states in his patent that he is “surprised” to find “pronounced improvement” by alternating the signals in the ears – for which he employs a Gate Oscillator and a Gate Switch Driver. Why the expression of surprise? It is hardly scientific language.

My hunch is that the pronounced improvement lay not in the ears but in the coils. He considered that he had merely invented another “beat frequency detector type”, thus missing a significant breakthrough by a whisker.

Reproduced by arrangement with
SILICON CHIP magazine 2006.
www.siliconchip.com.au

PIC N' MIX

MIKE HIBBETT

Our periodic column for your PIC programming enlightenment

Random Number Generation

ON the whole, microcontrollers are deterministic: they faithfully follow the instructions we give them. Barring hardware faults or coding errors, when asked to perform a sequence of instructions they will execute them in exactly the same way time and time again. That's all part of the microcontroller design; every operation is synchronised to the processor clock. That's a very good thing too; when we write a piece of software we would want it to work the same way on every processor, every time it is run.

Sometimes, however, it is useful to introduce a bit of randomness into the operation of a program. In a game of hangman for example, you would want to select a random word from a dictionary; some problem solving algorithms, for example navigating a maze, can benefit from making random decisions on which path to take. In the latter case it may not always be the most efficient method but it would be simple to implement and a lot of fun to watch!

Software testing is also an area where randomness is useful, since it can provide interesting input data that the person who wrote the software may not have considered. You could run the routine in a test harness thousands of times with random input data to verify that it performs correctly with a wide range of input data.

What is Randomness?

So what exactly is randomness? Surprisingly, it's difficult to find a useful definition of the word. The *Oxford English Dictionary* offers "made, done, or happening without method or conscious decision". A more workable definition can be found in mathematics: "Being or relating to a set whose numbers have an equal probability of occurring". What this means is that given a group of "things", such as the words in a dictionary, the group of numbers between 0 and 255 or the possible directions to turn in a maze, any one of the values in that group has the same probability of being chosen as any other.

That last definition of random is nice and concise, but achieving it in real life is almost impossible. There are some natural sources of randomness; radio-active decay is probably one of the best known. While the half-life of a particular radio-active element can be clearly defined the time between decay events is completely unpredictable, and if monitored by a sensor connected to your system it would form a very good random number generator. That's not a very practical solution however, so we need to look elsewhere for our source of random numbers.

Achieving Randomness

There are two approaches to this problem: make your own, or get some pre-calculated from somewhere else. This is not as crazy as it sounds. There are many websites dedicated to generating "very random" numbers including some respectable research establishments such as Fourmilab in Switzerland. The site www.random.org provides further information on randomness and has a form with which you can submit requests for up to 10,000 random numbers at a time. They also, amusingly, link to an alternative site that can serve up very non-random numbers: www.noentropy.net – worth a quick visit!

Once you have your random numbers you can store them away in your application and just call them up one at a time. If you record the index into the table in non-volatile memory such as EEPROM, then you will be able to give the appearance of randomness, pulling a new random number out each time. This is a very fast implementation, requiring just a lookup table.

The downside is that at some point you will reach the end of the list and need to repeat again from the beginning. Also, as you will need to store between one and four bytes per entry this method would consume a large amount of non-volatile memory. Not a practical solution.

White noise, which can be created by amplifying electron noise (from a diode source for example), produces a signal which can be clipped to output a sequence of random ones and zeros. This technique requires additional analogue circuitry in your design and a software process to clock in "bits" to build up a byte or word. It will also be susceptible to interference from internal or external signals.

Linear Congruential Generator

Fortunately, there is an alternative, simple, algorithmic solution to the problem: the Linear Congruential Generator. This is a trivial equation that can be used to generate a pseudo random number sequence. "Pseudo" means that it is only an approximation; in particular, the sequence will repeat itself after a (possibly large) number of iterations. Microsoft used this system in their implementation of the BASIC programming language.

The detailed explanation behind the equation is extremely complicated. Fortunately the equation itself and its application is not. Here it is:

$$x1 = (x0 * a + b) \text{ MOD } (2^N)$$

where $x0$ is the previous random number generated, $x1$ is the new one, "a" is the

constant 1140671485 and "b" is the constant 12820163. The equation will give numbers in the range of 0 to 16777215, ie a 24 bit number.

This method can be implemented easily in any programming language, for example in C the following would do:

```
nt main(int argc, char* argv[])
{
    unsigned long rndVal = 50000L;
    int i;
    float rndFloat;

    for (i=0;i<10;i++)
    {
        rndVal = (rndVal * 1140671485L +
        12820163) & 0xfffffL;

        // rndVal returns a number less than
        16777216;
        // divide by 16777216 to get a fraction
        between 0 and 1
        rndFloat = (float)rndVal /
        (float)16777216.0;

        printf("Value is %.15f\n",rndFloat);
    }
    return 0;
}
```

The reasons for the choice of values "a" and "b" are complex (in an early version of Basic, Microsoft choose a bad pair, resulting in a poor random number generator) but as you can see, it is a very straightforward algorithm to translate into software.

For us microcontroller fans, however, there is a big problem: the numbers in the equation are very large, and require the use of floating point division. This would require several hundred bytes of program code and several hundred clock cycles to execute. Is there no simpler way?

Simpler PRBS Method

Fortunately, a small, simple and fast solution does exist, that can produce acceptably random numbers. The method, called *pseudo-random bit sequence generators*, comes from the electronics world. They consist of a series of shift registers with a multiple input exclusive-OR feedback to the input. Depending on the number of shift registers used and the position of feedback taps, you can create a digital signal with random characteristics that repeats after a very long series of clock.

An example is shown in Fig.1. This is a 9-bit shift register with feedback taps at positions five and nine. The two input exclusive-OR gate (shown at "B") feeds these feedback taps back into the input.

At each shift of the circuit the last 8 bits can be copied out into a register (shown at “C”) to provide a random number between 0 and 255. The circuit will produce a random bit stream that repeats after 511 cycles.

Certainly 551 cycles is not a lot, but fortunately the circuit can scale very easily. A 31-bit shift register with taps at positions 31 and 28 will not repeat for over 2000 million cycles!

One of the nice things about PRBSs is that there is a very strong similarity between the electronics implementation and what you do in software, showing how close the two disciplines are.

Implementing PRBS

We can implement the shift registers as a series of RAM memory locations; a 31-bit shift register will require four bytes. To cycle to the next random value we simply need to perform an exclusive-OR of bits 31 and 28, shift the register to the right and stick the feedback value into the lefthand bit. You can extract your random value – 8, 16, 24 or 32-bit – from the righthand side by just reading the appropriate memory locations.

There is only one thing we need to take account of: the shift register must be given a non-zero value at the beginning. If you start with all zeros in the shift register then it will stay that way.

The code is straightforward. First, consider the initialisation of the shift register:

```
initRand
; Give the PRBS a non-zero start value
movlw    SEED_VALUE_1
movwf    shiftReg1
movlw    SEED_VALUE_2
movwf    shiftReg2
movlw    SEED_VALUE_3
movwf    shiftReg3
movlw    SEED_VALUE_4
movwf    shiftReg4
return
```

The seed value should be any non-zero value. To avoid starting at the same random value each time your application starts you should use a different SEED value when you call the initialisation routine. The simplest way is to just record the values stored in the shift register bytes into non-volatile memory and reload them in your initialisation routine. You can store them periodically or on each cycle of the PRBS, whichever is convenient.

To generate a random number, use the following:

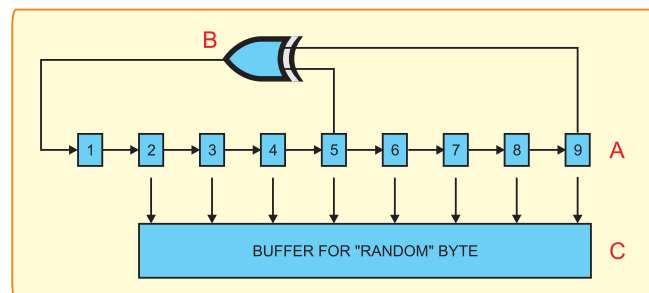


Fig.1. Flow chart of simple PRBS method

```
generateRand
; XOR bits 28 and 31
rrf      shiftReg4, W
movwf    tmpReg
swapf    shiftReg4, W
xorwf    tmpReg, F

; Put result in the Carry bit
rrf      tmpReg, F

; Perform the shift
rrf      shiftReg1, F
rrf      shiftReg2, F
rrf      shiftReg3, F
rrf      shiftReg4, F
return
```

As you can see, there is not much to it. Just nine instructions, five RAM locations used and an execution time of nine instruction cycles. Because the code is so efficient you can place it in an interrupt routine (should you wish to do so) and call it on a timer, for example once per second, to give yourself some extra “randomness”. Calling it once every time you extract a random number is perfectly acceptable though. If you do update it in an interrupt, take care how you read the random number – your code may be interrupted during the read.

So finally, to read the random number, just read as many bytes from the shift register as you wish, with the “righthand” byte being the least significant. Here are some examples:

```
get8bitRand
movfw    shiftReg4
movwf    rand
return

get16bitRand
movfw    shiftReg3
movwf    randh
movfw    shiftReg4
movwf    randl
return
```

Random Entropy

When we extract data from the PRBS in this way – copying out a range of bits to form a byte or word – we are “cheating” slightly. The random nature of the PRBS is reduced, but when you consider that the bit sequence does not repeat over a 2000 million range, it is unlikely to be a problem. As with many of the choices we make when we design a system, we must make some compromises, ones that (generally!) go unnoticed by the end user.

The degree of randomness a system has

is called its “entropy”. It’s a measure of the level of chaos or disorder in a system. If our random number generator always returned “1”, it would be considered to have a very low entropy. We can increase the level of entropy in our system by making calls to

the generateRand function in parts of our program that do not occur at specific times, for example when a key is pressed, or some external event occurs. Operating systems like Linux do this; when a programmer writes a device driver for the Linux kernel they can signal to the kernel that it can contribute to the system entropy (due to the random nature of incoming events for example.)

An Illusion

Computers are purely deterministic; what they do can always be predicted. Our PRBS generator will provide the illusion of randomness, but it will always be an illusion.

In some cases, such as software testing, this is actually a benefit. If a particular sequence of pseudo random test values causes a problem, they can always be regenerated if the starting point is known. The generator detailed above will produce exactly the same 2000 million sequence if it is run on a PIC, a PC or the largest super computer.

To improve the randomness of your generator consider using external events (such as time elapsed between keypresses or incoming serial bytes) to increase the entropy. True randomness is an unachievable goal but an acceptable, workable compromise is perfectly possible with an incredibly small code and memory overhead. May your next project be truly unpredictable!

An example of the practical use of a PRBS is used in the software of the PIC Sudoku unit to be published next month. Ed.



- * Suitable for use with a variety of sensors
- * Use it to show fuel level, oil pressure or engine temperature
- * Alarm output
- * Display auto-dims at night

Digital Instrument Display For Cars

Based on a PIC microcontroller, this simple project lets you convert the analogue instruments in your car to a digital display. It's suitable for use with fuel gauges, oil pressure gauges and temperature gauges, and even features an alarm output.

Pt.1: By JOHN CLARKE

MOST cars have analogue readouts for displaying fuel level and engine temperature. Similarly, the oil pressure is either shown on an analogue gauge or more commonly, there's no gauge and just an "idiot" warning light instead.

Of course, there's nothing wrong with analogue gauges – it's just that some drivers would rather have these outputs displayed in digital format instead.

That's where this Digital Instrument Display comes in – it's designed to operate with any sensor or sender unit which varies its resistance or voltage signal output and display the result on a 3-digit LED readout. Basically, it's ideal for use with sender units that have relatively slow changing values; eg, as found in fuel level, oil pressure and temperature gauges.

In operation, the unit can be calibrated so that the display will show

any value in the range from -99 through to 999. The decimal point can also be placed in one of two positions, so that the values can be from -99 to 9.99 or from -9.9 to 99.9. In addition, the unit can be calibrated to display metric or imperial units.

Alternatively, the values do not need to relate to any particular unit and could refer to percentages instead – eg, 100% for full.

Of course, fuel and temperature gauges don't usually show precise values. Instead, they give a general indication of how things are going – eg, remaining fuel level somewhere between full and half-empty, or temperature midway between hot and cold. By contrast, you can calibrate this digital display unit to show the actual values – eg, fuel remaining in litres (or gallons if you prefer) or engine temperature in °C or °F, or some other function.

In practice, the Digital Instrument Display is calibrated at two values

and the instrument calculates the remaining values from these in a linear fashion. For example, if the unit is to be used as a fuel gauge, it is best calibrated when the fuel tank is full (eg, 55 litres fuel) and then calibrated when the tank is close to empty (eg, 10 litres). The display will then subsequently be able to show the remaining fuel in the tank (in litres) over the complete range from full to empty.

Alarm output

An alarm output is available to warn of impending “doom”. For example, it could be set to trigger an alarm when the fuel tank approaches empty. Alternatively, it could be used to alert the driver if the engine is overheating or if the oil pressure is too low.

In operation, the unit is set up to trigger the alarm when the display reading goes above or below a particular value. Under alarm conditions, the righthand decimal point lights as a visual indication. In addition, the alarm output can also drive a low-current piezo siren if an audible indication is required or it can be used to trigger an external relay-driver circuit.

Presentation

The unit is housed in a small plastic case, with the display showing through a transparent red Perspex or acrylic window.

There are no user controls on the front panel. Instead, the three calibration switches (Mode, Up and Down) are hidden behind the front panel as they are not needed once the unit has been calibrated.

Different modes

The Mode switch is used to display the calibration values. On the first press, the display initially goes blank and then shows the first calibration value. This value is initially set at “0” and can be changed to any number up to 999 (disregarding the decimal point) using the on-board Up and Down switches.

Pressing the Mode switch again then brings up the second calibration value. This is initially set at 100 but again can be set to any number from 0-999 using the Up and Down switches.

Similarly, pressing the Mode switch a third time brings up the alarm value and once more, this is adjusted using the Up and Down switches. The sense of the alarm can also be set – ie, so

MAIN Features

- Suitable for connection to variable resistance or voltage output sensors.
- Programmable display values; shows readout on a 3-digit LED display.
- Alarm output signal with visual alarm output indication at righthand decimal point.
- Adjustable alarm level.
- Can be set to alarm either above or below set value (optional).
- Displays values from 999 maximum to -99 minimum.
- Decimal point selection at x.xx or xx.x position (optional).
- Automatic display dimming in low light levels.
- 2-second display update period.

that it is either on for values above the alarm setting (and off for values below this) or on for values below the alarm setting.

The required alarm sense is selected at power up. Pressing the Mode switch when power is first applied will keep the display blank and upon release the display will show either AL or AL-. An “AL” display indicates that the alarm will be on for values above the alarm value and off for values below the alarm value.

Conversely, an “AL-” display indicates that the alarm will be off for values over the alarm setting and on for values below this.

To change from one to the other, you simply switch off the power and then hold down the Mode switch and apply power again. The display will now show the alternative setting when the switch is released.

Returning now to the normal Mode switch operation, the fourth press of this button displays the actual measured value of the voltage applied to the input of the unit. This is to allow the unit to be set up correctly – ie, it allows you to ensure that the applied input voltage is within the permissible range.

The fifth pressing of the Mode switch brings up three dashes (- - -) for a short period, after which the unit returns to the “normal” display mode. In this mode, it displays the calculated value, which is based on the input voltage and calibration values. In this mode, the alarm LED will either be lit or unlit, depending on the alarm setting and the input signal level.

In summary, at power up, the display is in its normal mode. Repeatedly pressing the Mode switch then brings up the following modes: 1 – First Calibration Value; 2 – Second Calibration Value; 3 – Alarm Threshold; 4 – Measured Input Level; and 5 – Normal Mode again. Modes 1-4 are all indicated with a flashing alarm LED.

Circuit details

Fig.1 shows the circuit for the Digital Instrument Display. It's dominated by IC1, a PIC16F84-10P microcontroller. This monitors the input signal voltage via comparator stage IC2a, processes the information and drives the three 7-segment LED displays (DISP1 – DISP3).

OK, let's start with the input sensing circuit. In operation, the incoming analogue signal from the sensor (or sender) is filtered using a 10k Ω resistor and 100 μ F capacitor and fed to pin 2 of comparator stage IC2a. Note that provision has been made for a pullup resistor directly at the input, since this will be necessary with some sensors. Similarly, resistor R2 can be used to attenuate the input signal if necessary (more on this later).

In operation, IC2a compares the voltage on its pin 2 input with a DC voltage on its pin 3 input. This DC voltage is derived by applying a pulse-width modulated (PWM) square-wave signal from the RA3 output of IC1 to a 390nF capacitor via a 200k Ω resistor and trimpot VR2.

As a result, pin 1 of IC2a switches low whenever the voltage on its pin 2 input is greater than the voltage on pin

Parts List

- 1 Microcontroller PC board, code 571, available from the *EPE PCB Service*, 78 x 50mm
- 1 Display PC board, code 572, available from the *EPE PCB Service*, 78 x 50mm
- 1 front panel label 80 x 53mm
- 1 plastic utility case measuring 83 x 54 x 30mm
- 1 Perspex or Acrylic transparent red sheet, 56 x 20 x 3mm
- 1 10MHz parallel resonant crystal (X1)
- 1 LDR
- 3 SPST micro tactile switches
- 5 PC stakes
- 3 7-way pin header launchers
- 1 DIP18 socket for IC1
- 2 DIP14 low cost IC sockets with wiper contacts (cut for 3 x 7-way single in-line sockets)

Screws & spacers

- 1 9mm long x 3mm ID untapped brass spacer
- 1 10mm long x 3mm ID tapped Nylon spacer (can be made from 2 x 6mm spacers with one cut to 4mm)
- 2 6mm long M3 tapped Nylon spacers
- 2 M3 x 6mm screws
- 1 M3 x 15mm brass screw
- 1 M3 x 15mm Nylon screw

Wire & cable

- 1 300mm length of 0.7mm tinned copper wire
- 1 2m length of red automotive wire
- 1 2m length of yellow automotive wire
- 1 2m length of black or green automotive wire (ground wire)

Semiconductors

- 1 PIC16F84-10P or PIC16F84-20P

microcontroller programmed with INSTRUM.HEX, available for download from the *EPE* website at www.epemag.co.uk (IC1)

- 1 LM358 dual op amp (IC2)
- 1 7805 5V 1A 3-terminal regulator (REG1)
- 3 BC327 PNP transistors (Q1-Q3)
- 1 BC547 NPN transistor (Q4)
- 2 BC337 NPN transistors (Q5, Q6)
- 3 HDSP5301, LTS542A common anode 7-segment LED displays (DISP1-DISP3)
- 1 3mm red LED (LED1)
- 1 LM336-2.5 reference diode (REF1)
- 1 16V 1W Zener diode (ZD1)
- 4 1N914 switching diodes (D1-D4)

Capacitors

- 2 100µF 16V PC electrolytic
- 3 10µF 16V PC electrolytic
- 1 390nF (0.39µF) MKT polyester
- 2 100nF (0.1µF) MKT polyester
- 2 18pF ceramic

Trimpots

- 1 20kΩ horizontal trimpot (VR1)
- 1 250kΩ horizontal trimpot (VR2)
- 1 500kΩ horizontal trimpot (VR3)

Resistors (0-25W, 1%)

- | | |
|---------|------------|
| 1 1MΩ | 1 1kΩ 0.5W |
| 1 200kΩ | 3 680Ω |
| 7 10kΩ | 10 150Ω |
| 2 3.3kΩ | 1 10Ω 1W |

Miscellaneous

Automotive connectors, heat-shrink tubing, cable ties, etc.

output from RA3 is at 5V while a low output is at 0V.

The RC network on RA3 filters this PWM waveform to derive a DC voltage that is the average of the PWM waveform. This means that if the duty cycle is 50% (ie, a square wave), the average at RA3 will be 50% of 5V or 2.5V. Varying the duty-cycle either side of 50% produces higher or lower DC voltages accordingly.

Operation of the A-D converter is as follows: initially, the RA3 output is set to a 50% duty cycle and this sets the voltage at pin 3 of IC2a at 2.5V. At the same time, an 8-bit register inside IC1 has its most significant bit set high so that its value will be 10000000.

During this process, the comparator's output is monitored by IC1's RB0 input. If the measured voltage is lower than 2.5V, IC2a's output is high and the PWM output at RA3 is reduced to a 25% duty cycle to produce an average of 1.25V. The internal register is now set to 01000000.

Alternatively, if the measured voltage is above 2.5V, corresponding to a low comparator output, the RA3 output is increased to a 75% duty cycle to provide an average of 3.75V. The register is thus set to 11000000, with the most significant bit indicating a 2.5V 50% duty cycle and the next bit indicating the 1.25V 25% duty cycle (adding the two bits gives us the 3.75V).

The comparator output is again checked, after which the microcontroller adds or subtracts a 12.5% duty cycle (0.625V) and compares this against the input voltage again. The register is then set to X1100000 (with X a 1 or 0 as determined by the previous operation) if the input voltage is higher than the PWM waveform.

Conversely, if the input voltage is lower than the PWM voltage, the register is set to X0100000.

This process continues for eight cycles, the microcontroller progressively adding or subtracting smaller amounts of voltage (ie, 0.312V, 0.156V, 0.078V, 0.039V and 0.0195V) and the lower bits in the 8-bit register being either set to a "1" or a "0" to obtain an 8-bit A-D conversion.

Further resolution is obtained by altering the counter that's used to generate the PWM output. By adding or subtracting a number to the count, we can alter the filtered PWM signal by a small amount – corresponding to

3. This signal is then fed via a 3.3kΩ limiting resistor to the RB0 input of IC1. This resistor limits the current from IC2a when its output switches high to a nominal 12V, while internal clamp diodes at RB0 limit the voltage on this pin to 5.5V.

A-D converter

Among other things, IC1 functions as an analogue-to-digital (A-D) converter. In operation, it converts the

comparator signal on its RB0 (pin 6) input to a digital value which is then used to drive the 3-digit LED display.

The A-D converter used here operates by using a series of successive approximations and involves just two external connections to IC1. As mentioned earlier, IC1 produces a PWM signal at its RA3 output and this operates at 4.882kHz with a wide-ranging duty cycle. Note that a high

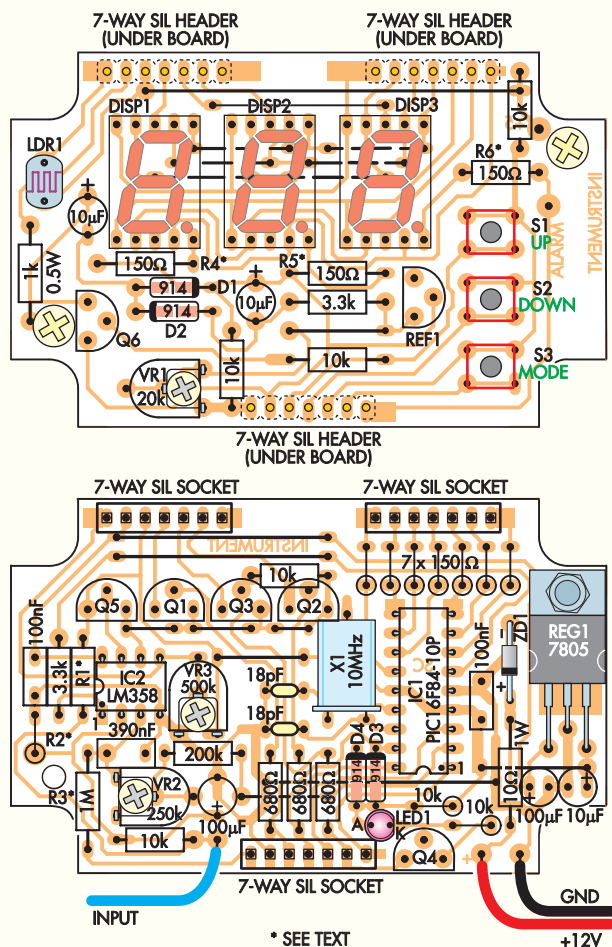


Fig.2: install the parts on the PC boards as shown here . In particular, be sure to install the 7-segment LED displays with their decimal points at bottom right and take care not to get the transistor types mixed up.

Table 2: Capacitor Codes

Value	μ F Code	EIA Code	IEC Code
390nF	0.39 μ F	394	390n
100nF	0.1 μ F	104	100n
18pF	18pF	18	18p

However, it's quite common for automotive sensors to produce signals all the way down to 0V, so we need to cater for this type of sensor. That's done by applying a negative voltage to pin 3 of IC2a, to offset the 375mV minimum from the A-D converter.

This offset voltage is derived from voltage reference REF1, diodes D1 & D2 and transistor Q6 and its associated components.

Q6 is driven by the RA0 output of IC1. When the RA0 output is low, Q6 is off and capacitor C1 charges via a 1k Ω resistor (which connects to the 12V supply) and via diode D1. When the RA0 output subsequently goes high, Q6 turns on and connects the positive side of C1 to ground. As a result, the other end of C1 goes negative and this charges capacitor C2 via diode D2.

C1 is again charged when Q6 turns off, while D2 now becomes reverse biased and prevents C2 from discharging via this path. Instead, the negative voltage across C2 is applied to voltage reference diode REF1 via a 3.3k Ω resistor to produce a fixed -2.49V reference voltage. This voltage is then applied to pin 3 of IC2a via VR1, a 10k Ω resistor and a 1M Ω resistor (R3).

In practice, VR1 is adjusted so that the applied voltage offsets the 390mV minimum output from the A-D converter.

LED displays

The 7-segment display data from IC1 appears at outputs RB1-RB7 and

9.76mV, 4.88mV and 2.44mV – so that we obtain an 11-bit A-D conversion.

The A-D conversion thus has a resolution of around 2.44mV at the least significant bit. The possible number of values for the 11-bit register is from 0000000000 (0) to 1111111111 (2047).

In practice, we are limited to a range from about 152 to 1848 be-

cause the software must have time for internal processing to produce the waveform at the RA3 output. This means that the input signal can only be measured over a particular range of voltage corresponding to the 152 minimum count and the 1848 maximum count.

This corresponds to about 373mV minimum and 4.5V maximum.

Table 1: Resistor Colour Codes

No.	Value	4-Band Code (1%)	5-Band Code (1%)
1	1M Ω	brown black green brown	brown black black yellow brown
1	200k Ω	red black yellow brown	red black black orange brown
7	10k Ω	brown black orange brown	brown black black red brown
2	3.3k Ω	orange orange red brown	orange orange black brown brown
1	1k Ω	brown black red brown	brown black black brown brown
3	680 Ω	blue grey brown brown	blue grey black black brown
9	150 Ω	brown green brown brown	brown green black black brown
1	10 Ω	brown black black brown	brown black black gold brown

these directly drive the cathodes of the three LED displays (DISP1-3) via 150Ω current limiting resistors. Note that the segments common to each display are connected together – ie, the “a” segment cathodes are all connected together, as are the “b” segments and so on.

The displays are driven in multiplex fashion, with IC1 switching its RA0 & RA1 lines low in sequence to drive transistors Q1 & Q2. For example, when RA0 goes low, Q1 turns on and applies power to the common anode connection of DISP1. Any low outputs on RB1 – RB7 will thus light the corresponding segments of that display.

After this display has been on for a short time, the RA0 output is taken high and DISP1 turns off. The 7-segment data on RB1-RB7 is then updated, after which RA1 goes low to drive Q2 and display DISP2.

Transistor Q3, which switches power to DISP3, is driven in a different manner to Q1 & Q2. This transistor is off when either RA0 or RA1 is low (ie, if one of the other displays is on). That's because a low on RA0 or RA1 holds LED1's anode low (ie, at 0.6V) via either diode D4 or D3. As a result, LED1 cannot conduct and so Q4 is off.

However, when RA0 and RA1 are both high, D4 and D3 are reverse biased and Q4's base is pulled high via the 10kΩ resistor on LED1's anode. This turns Q4 on which in turn pulls Q3's base low via a 680Ω resistor. And that, in turn, turns Q3 on and lights display DISP3.



Of course, in practice, DISP1, DISP2 & DISP3 are switched on and off at a very fast rate, so that they appear to be continuously lit.

Finally, note that the decimal point (pin 5) of DISP3 is connected to IC1's RA2 output. RA2 is the alarm output and it normally switches low and turns on DP3 under alarm conditions. It can also be used to activate a low-current piezo siren which has its other side connected to the +5V rail.

Display dimming

Op amp IC2b is used to control the display brightness. This stage is wired as a unity gain amplifier and drives transistor buffer stage Q5 which is inside the negative feedback loop.

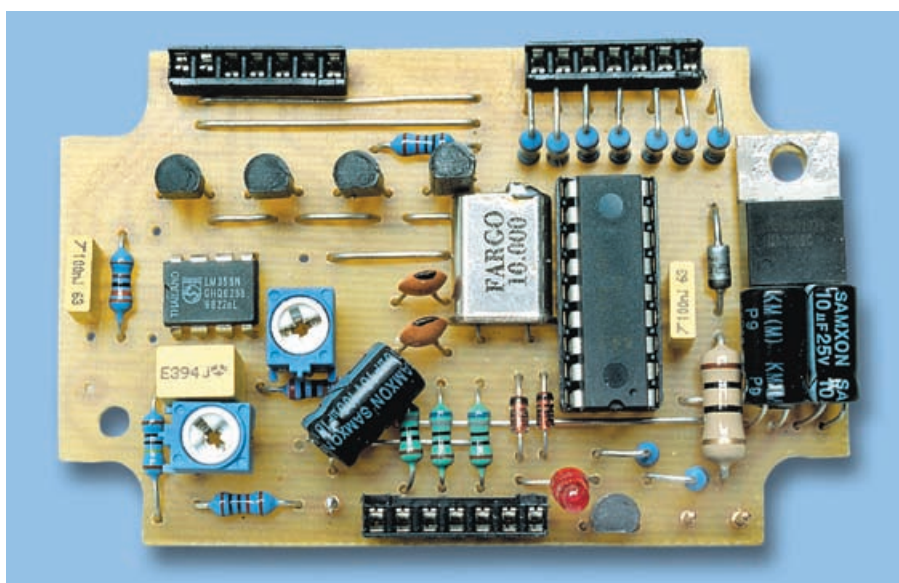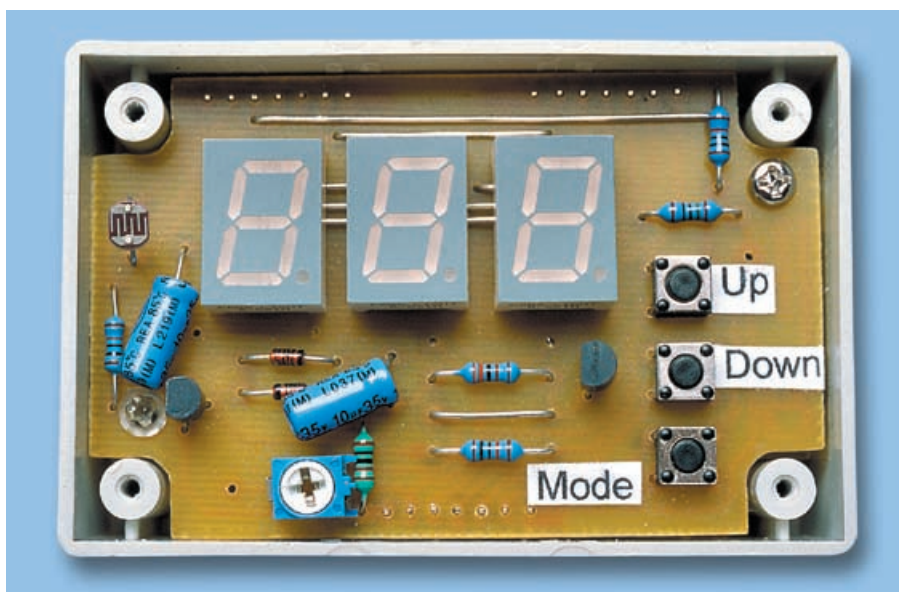Light dependent resistor LDR1 varies the voltage on pin 5 of IC2b



The display board (shown in the case at top) plugs directly into the pin header sockets on the processor board (above), eliminating wiring connections between the two. Notice how the electrolytic capacitors on the two boards are bent over (see text), to prevent them fouling other parts.

according to the ambient light level. In daylight, the voltage on pin 5 (and thus on pin 7) is close to +5V because the resistance of the LDR is low. This means that Q5's emitter will also be close to +5V and so virtually the full supply rail is applied to the emitters of transistors Q1-Q3 and the displays operate at full brightness.


As the ambient light falls, the LDR's resistance increases and so the voltage on pin 5 of IC2b decreases. And when it's completely dark, the voltage on pin 5 is determined by the setting of trimpot VR3 which sets the minimum brightness level. As before, the voltage on pin 5 appears at Q4's emitter and

so the displays operate with reduced brightness.


Mode switches

Switches S1-S3 are all monitored using the RA4 input which is normally at 5V due to a 10kΩ pullup resistor. The other sides of S1 and S2 are connected to the RA0 and RA1 outputs respectively, while S3 connects to Q4's collector.

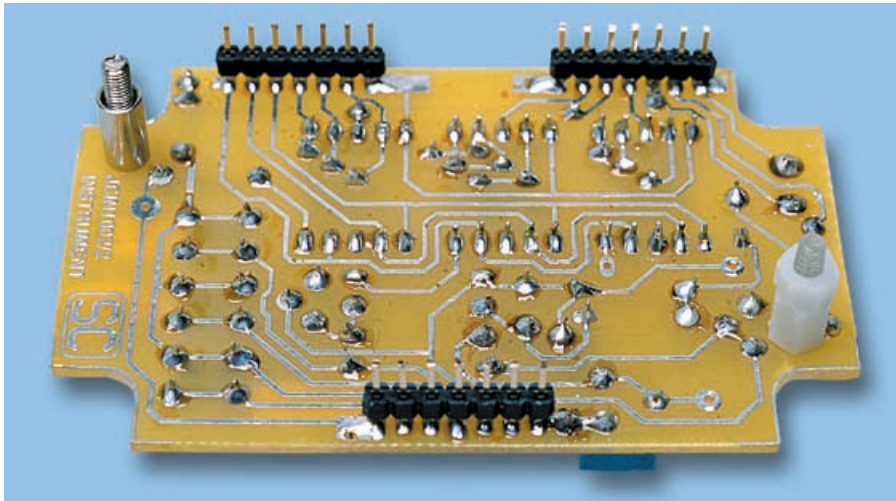This means that pressing S1 will pull RA4 low when RA0 is low. Similarly, S2 can pull RA4 low when RA1 is low, while S3 can pull RA4 low when both RA0 and RA1 are high. As a result, the microcontroller can



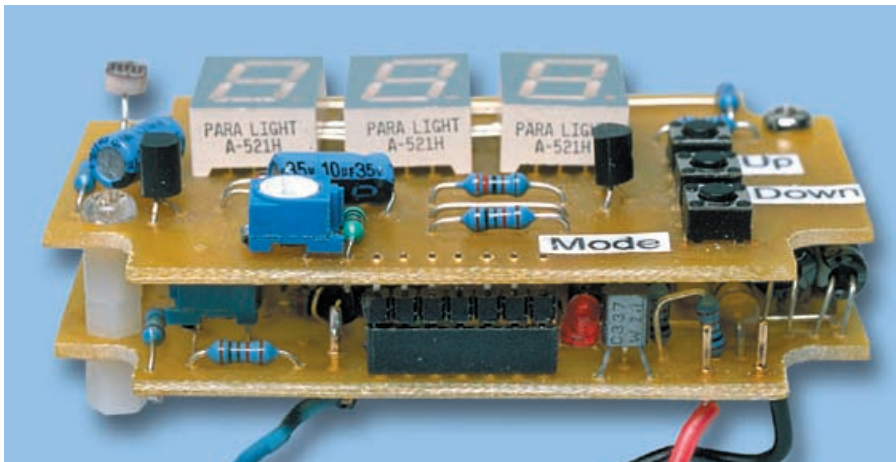The pin headers are installed on the track side of the display board using a fine-tipped soldering iron. Note that it will be necessary to slide the plastic spacers along the leads to allow room for soldering.



This view shows how the two boards are stacked together in "piggyback" fashion to make a compact assembly. Make sure that none of the parts on the processor board contact the back of the display board.

determine which switch has been pressed when RA4 goes low, by checking the status of both RA0 and RA1.

Clock signals for IC1 are provided by an internal oscillator circuit which operates with crystal X1 (10MHz) and two 18pF capacitors. The two capacitors provide the correct loading for the crystal and ensure that the oscillator starts reliably.

The crystal frequency is divided down internally to produce clock signals for the microcontroller operation and for the display multiplexing.

Power

Power for the circuit is derived from the vehicle's ignition supply line. A 10Ω 1W resistor and a 100μF capacitor decouple this supply line, while 16V Zener diode ZD1 protects the circuit against transient voltage spikes.

The decoupled ignition supply is then fed to regulator REG1 which provides a +5V rail. This rail is then used to power the microcontroller and display circuitry, while IC2 and Q6 are powered directly from the decoupled ignition supply (+12V).

That completes the circuit description. Of course, most of the clever stuff takes place inside the PIC microcontroller under software control. You can purchase a pre-programmed PIC from Magenta Electronics or download the source code (instrum.asm) from the *EPE* website if you want to figure out how it works. The source code is fully commented, so you shouldn't have too much trouble.

Construction

All the parts are mounted on two PC boards: (1) a microcontroller board

coded 571, and (2) a display PC board coded 572. These boards are stacked together using pin headers and sockets to make the interconnections, so there's no external wiring (apart from the power supply and sensor connections).

Fig.2 shows the assembly details. Begin by checking the PC boards for shorts between tracks and possible breaks and undrilled holes. That done, install all the wire links on both boards. It is important that these be installed now, as other parts mount over the top of some of the links.

You can now concentrate on building the microcontroller board. Begin by installing all the resistors using Table 1 as a guide to determining the correct values. It's also a good idea to check them using a digital multimeter, just to make sure.

Note that some of the resistors including the 7 × 150Ω units at top right, are mounted end-on to save space. Leave out R1 and R2 for the time being but be sure to install R3 (1MΩ) as shown.

Next, install a socket for IC1 (taking care with its orientation), then install IC2, Zener diode ZD1 and diodes D3 & D4. That done, install REG1 by bending its leads down by 90° so that its metal tab sits flat against the PC board. Make sure that the hole in the metal tab lines up with the hole in the PC board before soldering the leads.

Trimpots VR2 & VR3 can go in next (don't get them mixed up), followed by the capacitors. Note that the two electrolytic capacitors near the regulator must be mounted so that their bodies lie flat against REG1's leads (see photo). Similarly, the 100μF capacitor near VR2 must be mounted so that it lies between the adjacent 200kΩ and 680Ω resistors (see photo).

In practice, this simply involves bending the capacitor leads down by 90° before installing them on the board. Note that the two electrolytic capacitors near REG1 are oriented in opposite directions.

Next, install three PC stakes at the external wiring points, then install the transistors. Q1 – Q3 are all BC327s (PNP), while Q5 is a BC337 NPN type so don't get it mixed up with the others. The remaining transistor on this board (Q4) is a BC547.

Crystal X1 also mounts horizontally on the PC board. It is secured by soldering a short length of tinned copper

wire between the end of its metal case and an adjacent PC pad.

Finally, the three 7-way in-line sockets can be fitted. These are made by cutting two 14-pin IC sockets into single in-line strips using a sharp knife or a fine-toothed hacksaw. Clean up the rough edges with a file before installing them on the microcontroller board.

Display board

Now for the display board. The wire links should already be in place but if not, install them now, followed by the resistors, diodes and trimpot VR1. **At this stage, you can also decide if you want the decimal point showing. Install R4 if the display is to show x.xx, or R5 if the display is to show xx.x instead. Alternatively, do not install either resistor if the decimal point is not required.**

Next, install the three 7-segment LED displays with their decimal points at bottom right. REF1, Q6 (BC337) and the two electrolytic capacitors can then be installed. As before, the two electrolytics are installed so that their bodies lie flat against the PC board.

The LDR is mounted so that its top face is about 3mm above the displays (it can go in either way). Install it now, followed by the three pushbutton switches.

Finally, complete the display board assembly by installing the pin headers. These are installed from the copper side of the board, with their pins protruding about 1mm above the top surface.

You will need a fine-tipped iron to solder these pin headers. Note that you will also have to slide the plastic spacers along the pins to give sufficient room for soldering.

Preparing the case

Work can now begin on the plastic case. First, use a sharp chisel to remove the integral side pillars, then slide the microcontroller board in place and use it as a template to drill two mounting holes in the base – one through the hole in REG1's tab and the other immediately to the left of R3.

In addition, you will have to drill a hole in the back of the case to accept the power leads, plus an extra hole for the input signal lead.

Once that's done, plug the display board into the microcontroller board and secure them together using machine screws and spacers as shown

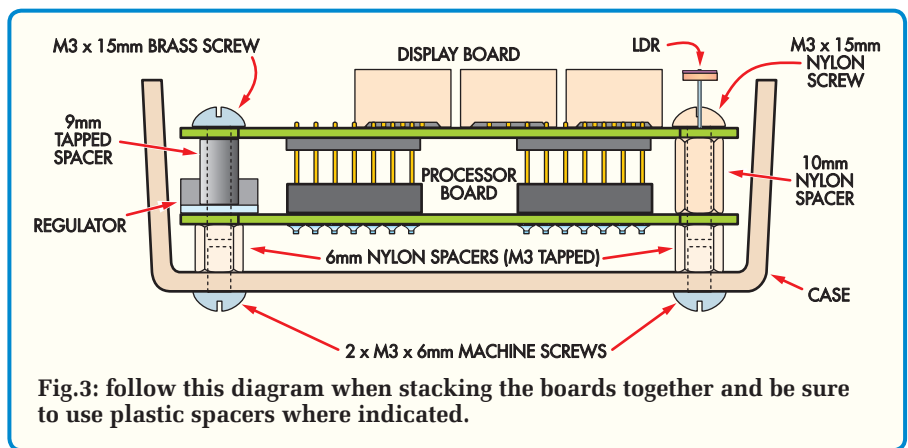


Fig.3: follow this diagram when stacking the boards together and be sure to use plastic spacers where indicated.

in Fig.3. Check that the leads from the parts on the display board do not interfere with any parts on the microcontroller PC board. If necessary, trim the leads of the display board parts to prevent this.

The front panel artwork (to be published next month) can now be used as a template for marking out the display cutout and the position of the hole for the LDR. That done, drill the LDR hole and drill a series of closely-space holes around the inside perimeter of the rectangle for the display cutout.

The centre-piece can then be knocked out and the job filed to a smooth finish.

Be sure to make the cutout just large enough, so that the red Perspex or acrylic window is a tight fit. This window can then be further secured by applying several small dabs of super glue along the inside edges.

Testing

It is best to check the power supply before plugging the microcontroller IC into its socket.

To do this, first unplug the display board and put it to one side. That done, connect the +12V and GND leads to the microcontroller board, apply power and use a multimeter to check that there is +5V on pins 4 & 14 of IC1's socket (use REG1's metal tab for the GND connection).

If this is correct, disconnect power and insert IC1 in place, ensuring that it is oriented correctly. That done, plug the display board back in and apply power with the input lead connected to ground. The display should light and show three dashes (- - -).

After about two seconds, the display should then show a number. Our prototype showed -4, but this will depend

on the settings of VR1 and VR2.

Now press the Mode switch – the display should now show “0” and the alarm LED should flash. Pressing the Mode switch again should now cause the display to show “100”. Press it again and the display should show 50, while the fourth press should bring up the current input reading.

Our prototype showed 97 but this will again depend on the settings for VR1 and VR2.

Now test the dimming feature by holding your finger over the LDR. Adjust VR3 until the display dims. Note: this trimpot is best adjusted in the dark to set the minimum brightness.

Finally, check that there is -2.5V at the negative terminal of voltage reference REF1. Note, however, that this voltage could vary from this value by about 200mV due to tolerances in the reference.

Next month

That's all we have space for this month. In Pt.2 next month, we will describe how to connect different sensors to the unit and describe the calibration procedure for these various sensors.

EPE

Reproduced by arrangement with
SILICON CHIP magazine 2006.
www.siliconchip.com.au



THE MEMORY LINGERS ON

Do you ever wonder how some electronic and electrical manufacturers got their name? If so, join Mark Nelson on a ramble down Memory Lane.

FERRANTI, Plessey legacy fuels analogue start ups." That was the intriguing headline of an article in the trade paper *Electronics Weekly* recently and I had to read on to find out what it was all about.

The story in fact concerned the burgeoning number of new British start-up companies specialising in analogue, rather than digital, integrated circuits. It quoted Hans Rohrer, head of analogue chips company Zetex, saying "There's more analogue talent in the UK than in other regions because of Marconi, Ferranti and Plessey. The good old Ferranti and Plessey bipolar processes can go down to voltage levels you can't do with CMOS. Europe has more bipolar designs than the rest of the world put together."

Fraud Leads To Bankruptcy

It's nice to know that Britain still excels in something but where did Ferranti, Marconi, Plessey and all the other grand old electronics companies go? Ferranti's semiconductors division became Zetex Semiconductors, the company from which Mr Rohrer in fact hails.

Fortunately for Zetex, it parted from the rest of the Ferranti dynasty before the main company became embroiled in a disastrous takeover that in 1993 ended in bankruptcy. The surviving divisions either became independent companies or were taken over by GEC-Marconi. A breakaway company, Dennis Ferranti Meters, which made telephones for British Telecoms, had split off already in 1951 and is still going strong.

GEC and Marconi merged in 1968. Marconi Electronic Systems, later GEC-Marconi, was the defence arm of GEC and was sold to British Aerospace in 1999 to become BAe Systems, whilst GEC itself was renamed Marconi plc the same year. The majority of the business was sold to Swedish Ericsson in January of this year, with the remainder taking the new name of Telent. Incidentally, there was never any connection between the British GEC and General Electric of America, despite the similarity of their trademarks; the British firm was founded several years before the US corporation.

Unhappy Merger

Plessey and GEC became embroiled in rival takeover bids in the 1980s, resulting in an unhappy merger called GEC-Plessey Telecommunications (GPT) that seemingly managed to perform worse than either of the partners' previous incarnations. Somehow or other Plessey South Africa stayed out of the fray and a few years ago launched its products on the UK market, complete with the old Plessey oscilloscope trace "twiddle". Since then, however, it has changed its name to the less alluring Tellumat.

What's In A Name?

But where did these names come from? Marconi and Ferranti are straightforward Italian surnames, whilst Plessey was both the name of an original shareholder, Plessey Parker, and also the home village of the founder's wife.

Other trade names are more complex, however. You may well remember the name Pifco but be unaware that it was established in Manchester in 1900 as the Provincial Incandescent Fittings Company. Unless you have a long memory for old advertisements, you will probably not recall that soldering iron manufacturer Antex was originally the Anglo-Netherlands Technical Exchange.

Exide was the trade name of The Electric Storage Battery Company and was introduced in 1900, short for "Excellent Oxide". Vidor, another battery company, was run by a Mr Thomas Cole and folklore has it that he named the product after his daughters Violet and Doris. It appears, however, that the daughters were actually called Valerie and Denise, with the 'R' coming from the name of his wife Rebecca.

Disputed Provenance

Another name with a disputed provenance is AMPEX, famous over several decades for tapes and tape recorders. What is not in doubt is that AMP are the initials of its founder, Alexander Michael Poniatoff. For the EX you can take your pick, as some say it stands for excellent whilst others argue in favour of excellent.

The AMP in AMP connectors has a different origin. Today the brand is part of the giant Tyco Electronics conglomerate but when founded in 1941 it was known as Aero-Marine Products.

Another connector maker, Amphenol, was the American Phenolic Corporation, phenol being used for the Bakelite shells of many of their products.

Abbreviations feature in the names of many electronic connector designs and from Europe we have DIN and SCART, both named after the committees that designed them. DIN is the Deutsche Industrie Normenausschuss (German Industrial Standards Committee), whilst SCART or Peritel connectors recalls Syndicat des Constructeurs d'Appareils de Radio et de Télévision (Radio and Television Equipment Manufacturers' Association).

Coaxial Connectordom

Coaxial connectors have names that are shorter but no less abstruse. The UHF connector once widely used by CB and amateur radio enthusiasts is also known as an F&E, in

Europe as a PL-type and in Japan as an M-type. The name UHF is confusing as it recalls the connector's wartime radar use at ultra high frequencies, whilst F&E (Films and Equipment Ltd) made many kinds of connector, not just this one (they later became Cannon UK Ltd, by the way).

The N connector is the Neill or Navy type, originated in 1942 by Paul Neill of Bell Labs and standardised on a Navy Bureau of Ships drawing. C-type connectors recall the name of developer Carl Concelman of Amphenol. Mix the two and you get BNC, standing for Baby (or Bayonet) Neill Concelman. This was a baby-size combination of the designs of Neill and Concelman.

EIAJ connectors were devised by the Electronics Industry Association of Japan, whilst MUSA plugs, still used in television studios, recall those originally used for rapid changing of antenna feeders on a pre-war transatlantic radiotelephone project, the Multiple Unit Steerable Array. Not many people know that!

Generic Terms

Tannoy is effectively a generic name for any kind of public address equipment but its makers entered this business entirely by accident. Originally they produced mains power supplies for battery radio sets. A special tantalum alloy was used as the rectifier, hence the trade name.

You can probably guess what kind of product The Automatic Coilwinder Company made but when they introduced a new multimeter that measured amps, volts and ohms all with the same instrument, they coined the slogan AVO. The rest is history and for some people any make of multimeter is an "AVO" to them.

Export Variants

Some products assumed different names when produced for export. British audio valves made by GEC were called Genalex in the USA and Ever Ready batteries sold outside the United Kingdom took on the name BEREK (standing for British Ever Ready Company). In both cases this was to avoid confusion with names already established overseas by the American General Electric and Eveready (one word, not two!) companies. Presumably to avoid similar kinds of confusion European-made Philips products were sold in the USA as Norelco.

Do I detect your eyes glazing over with boredom? Should I stop now? Yes, because I've nearly overshot the word count for this page. But if you know the origins of any other names (or think I've got any of these wrong), please write or email and tell us!

INTERFACE

Robert Penfold



PC INTERFACING SOFTWARE

IN this month's *Interface* article we will consider the software side of PC interfacing, which is something that seems to be problematic for many readers.

Matters were easier in the days of the GW BASIC and Q BASIC interpreters. One or other of these was supplied as part of the MS-DOS operating system, and they provided a simple but reasonably effective way of writing programs for use with PC electronic projects. The Quick BASIC compiler was available at reasonably low cost, and enabled faster stand-alone programs to be compiled.

Things became more difficult when MS-DOS became obsolete, because Windows 95 and later versions of Windows were not supplied with any form of BASIC. It was necessary to buy a programming language such as Visual BASIC. On the face of it, Visual BASIC is ideal for writing the software for do-it-yourself computer projects. The visual approach makes it easy to produce good virtual controls, meters, or whatever. The standard BASIC functions, arrays, and so on are still there, making it fairly straightforward to manipulate data.

The problem with Visual BASIC is that it has no built-in means of directly accessing the ports. In GW/Q BASIC this was handled by the INP and OUT instructions, as it is in many other computer languages. This shortcoming was solved by Jan Axelsson's excellent **Inpout32.dll**, which is suitable for use with Windows 95/98/ME. This is still available at no cost from Jan's web site (www.lvr.com).

Another version of **Inpout32.dll** is also available from the Logix4u web site (www.logix4u.net/inpout32.htm), and this works with versions of Windows up to Windows XP. This site also has a 64-bit version for use with 64-bit versions of Windows.

Details of using **Inpout32.dll** have been provided several times before in *Interface* articles, and the same ground will not be covered again here. Anyway, both versions are supplied complete with instructions, and further information is provided on the relevant web sites.

Progress?

Visual BASIC 6 plus an add-on to enable it to control the ports is just about the ideal combination for writing software for PC projects. Unfortunately, things move on and Visual BASIC 6 was superseded by Visual BASIC Net, which was a much more powerful program than its predecessor, but was not well suited to writing relatively simple programs, which had always been one of Visual BASIC's selling points. In fact, the new version did not seem to be well suited to most of the areas of programming where its predecessor had excelled.

Microsoft responded to the widespread criticism of Visual BASIC Net by developing a new version, aided by feedback from users. This version is now available in the form of Visual BASIC 2005, and there is a version for hobbyists called Visual BASIC 2005 Express Edition.

It is debatable whether this program is really the equal of Visual BASIC 6 for applications such as control programs for computer hardware projects. It does, however, have one huge advantage though, which is that it is available as a free download from the Microsoft web site!

used to download and install the main program, or downloading the main program itself as an image or ISO file. This file is burned to a CD-ROM and then used to install the program in the normal fashion.

The CD-ROM method is probably the best approach since it avoids the need to download the file again if it should be necessary to reinstall the program. It also makes it easy to install the program on several PCs, which is allowed under the licensing conditions.

The program does not really look much like Visual BASIC 6 once it has been

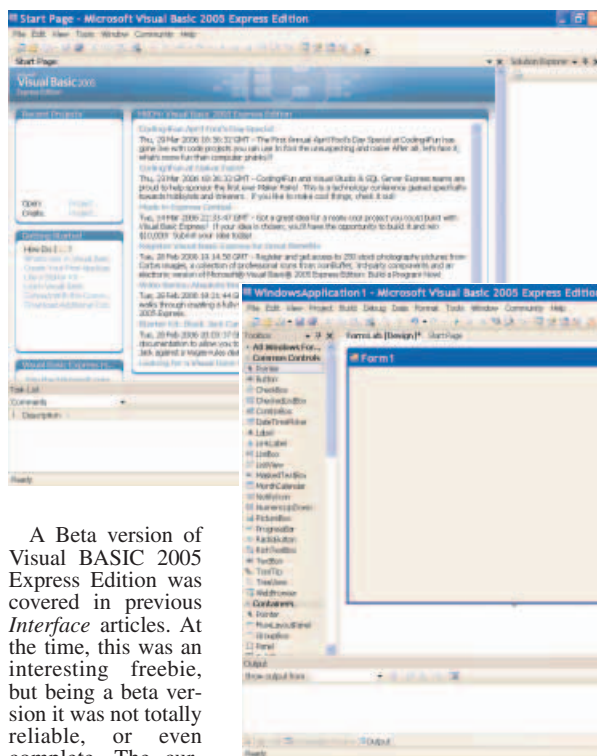


Fig.1. (Left) Initially the program looks a bit gimmicky, with a page that gives the latest news about Visual BASIC 2005 Express Edition

A Beta version of Visual BASIC 2005 Express Edition was covered in previous *Interface* articles. At the time, this was an interesting freebie, but being a beta version it was not totally reliable, or even complete. The current version is the fully finished product. As such it should be fully functional and have good reliability.

One slight drawback is that the size of the download is around 450 megabytes. With a broadband connection of some kind it should only take an hour or two to download, but it could take more like a day or two using a 56k dialup connection. This is the page on the Microsoft site that deals with the program:

<http://msdn.microsoft.com/vstudio/express/vb/>

This page has some general information about the program and a link to the download page. There is a choice of downloading a small setup program which is then

Fig.2. The program has something close to the traditional Visual BASIC look once it is properly "up and running"

installed and run (Fig.1). Assuming there is an active Internet connection, the main panel provides the latest news about Visual BASIC Express Edition. This disappears when you start using the program in earnest (Fig.2.).

The Toolbox that gives access to components such as control buttons, labels, etc. is conspicuously absent. However, it can be activated by selecting Toolbox from the View menu. It is then possible to select objects and place them on the form in the usual way. Adding the Toolbox gives a screen layout that is not too far removed from the one traditionally used for Visual BASIC.

Upgrading

With the beta version of the Visual BASIC Express Edition it was not possible to modify a Visual BASIC 6 program by loading it directly in the normal way. Instead, it was necessary to go through a simple conversion process. In Microsoft's terminology the program had to be upgraded. This remains the case with the final version of the program. As before, it is just a matter of selecting Open Project from the file menu, and selecting the appropriate file. Trying to open a Visual BASIC 6 project results in the Visual BASIC Upgrade Wizard automatically appearing (Fig.3).

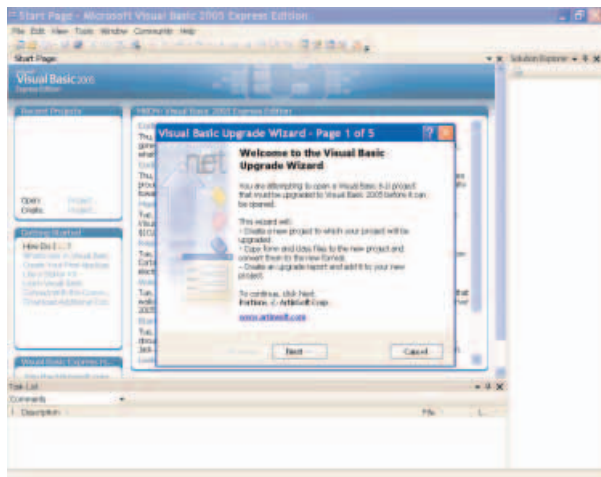


Fig.3. Trying to load a Visual BASIC 6 program results in the Upgrade Wizard being launched automatically

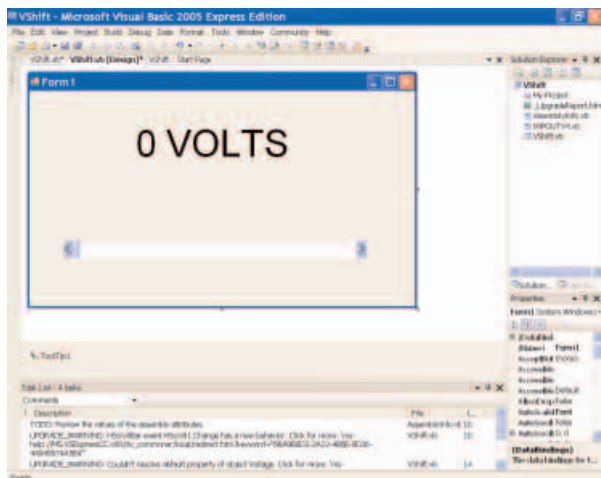


Fig.4. A Visual BASIC 6 program has been successfully upgraded and loaded. It can now be modified, debugged, saved, compiled, etc

When upgrading a simple program it is likely that the wizard will offer few options, if any. However, if given the choice, make sure that an EXE project is selected and not a DLL type.

Upgrading a very simple project that used **Input32.dll** proved to be successful (Fig.4), although there were some warning messages added into the code. Strangely, these related to the scrollbar and the label components and not to **Input32.dll**. The program compiled without any problems, and almost ran properly. For some reason the label component was not always large enough to take the text in a single line, causing it to wrap onto a second line. Simply making the label a little wider

and recompiling the program cured this problem (Fig.5).

In order to write programs that use **Input32.dll** it is not enough to have it available to the system. The file with a BAS extension that is supplied with **Input32.dll** must be loaded into Visual BASIC so that the INP and OUT instructions are added to its repertoire.

The problem with the beta version of Visual BASIC Express Edition, and the final version, is that there is no apparent means of loading the BAS file. There is no Add File option in any of the menus. An Open File option is available in the File menu, but this does not load the file in the correct manner. Neither does the Add Existing Item in the Project menu.

It is possible to work around the problem by producing a dummy program in Visual BASIC 6 that has the BAS file loaded, but is otherwise empty. This file can be loaded into Visual BASIC 2005 Express Edition and upgraded in the usual way. It then provides a starting point that has **Input32.dll** preloaded, with the INP and OUT instructions fully operational.

DIY Project Menu

The upgrade process seems to add a module that makes the new commands operational. An alternative to the rigmarole of the upgrade process is to simply add this module yourself. This is done by going to the Project menu and selecting the Add Module option. A pop-up window is then used to provide a name for the new module, or the default can be accepted. The following code is then entered for the module:

Option Strict Off Option Explicit On Module inport

```
Public Declare Function Inp Lib  
"inport32.dll" Alias "Inp32" (ByVal  
PortAddress As Short) As Short
```

```
Public Declare Sub Out Lib  
"inport32.dll" Alias "Out32" (ByVal  
PortAddress As Short, ByVal Value As Short)
```

End Module

The INP and OUT commands should then work correctly provided **Input32.dll** is available to the system. If everything is

all right, the usual hint text will appear when you are entering an INP or OUT instruction. The hint text will not appear if something is not quite right, and the word INP or OUT will be underlined to show that it has not been recognised.

The module can be saved by right-clicking its tab and selecting the Save option from the pop-up menu. It will be saved under whatever name you used, plus a "vb" extension. In order to use the INP and OUT commands in the future it is just a matter of starting a new project and then adding the module to it. This is done by selecting Add Existing Item from the Project menu, and using the file browser to find and open the correct module file. Do not use the Open File option in the File menu. This will load the module's file, but not in a way that will produce the desired result.

Finally

Visual BASIC Express Edition inevitably has some omissions compared to the standard product, although it is likely that many of the missing facilities would be of little use in the current context. It does include a potentially very useful SerialPort component, although it is something that has been added to Visual BASIC a bit late in the day. Serial ports are currently being phased out, although many PCs still have at least one of them.

Two regrettable omissions are the Line and Shape components of Visual BASIC 6. These make it easy to draw on-screen circles, lines, and ellipses when producing virtual meters, switches, rotary controls, and so on. They also make it easy to control these objects, so that a meter can be made to produce the correct reading for example. It is still possible to produce these objects with Visual BASIC Express Edition, but it

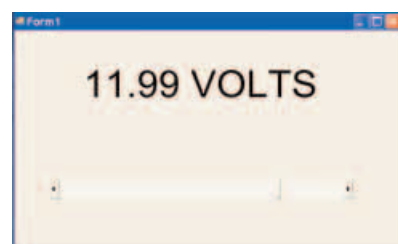


Fig.5. With the label component made slightly wider, the compiled program ran properly

seems to be a matter of resorting to the old fashioned method of normal program code. This is usually much slower than using the visual method to get the basic elements in place, with some "fine tuning" the co-ordinates then being applied if necessary.

Anyway, Visual BASIC 2005 Express Edition is a step forward from the previous free versions of Visual BASIC in that it does have the ability to compile programs which can then run independently. It is certainly a very worthwhile download for those who do not already own a full retail version of Visual BASIC. It should also be of interest to owners of older retail versions of Visual BASIC such as versions 5 and 6, although it might not be a viable replacement for them.

Express News

Delving into the pricing of VB 2005 Express Edition, it seems that it is free provided it is downloaded before the 6th November 2006. Thereafter it will cost \$49 US. Unlike previous low-cost versions of VB, it can be used to produce commercial software.



Widgy

Distortion effects for y

Do you own a guitar but don't have an overdrive (or distortion or fuzz) box yet? Well your prayers have been answered! This one sounds great, it's cheap and it's easy to build!

By PETER SMITH

IF YOU'RE A GUITAR PLAYER, then you'll certainly know all about the various "effects" that can be used to enhance guitar sounds. Over the years, many great players have combined these effects with their own unique styles to create unmistakable signature sounds.

Some of the most sought-after sounds are produced by deliberate harmonic distortion of the music content. Originally, this type of effect was produced exclusively by over-driving the output stage of valve amplifiers.

About overdrive & distortion

These days, distortion effects are generated by dedicated electronics equipment. Perhaps in an attempt to capitalise on the success of past legends more than

anything, much of this equipment boasts valve-like distortion qualities.

Valve amplifiers have a reputation for soft-clipping the output signal when they are overdriven, at least at moderate levels. If the signal is a pure sinewave, the peaks are simply rounded off, with a certain amount of wave shape compression occurring.

These rounded peaks create predominantly lower-order harmonics. Essentially, this means that the harmonics are closely related to the fundamentals and therefore tend to sound quite natural. Perhaps we could say that they "resonate" or "ring" with the fundamental tones.

Harmonics, by the way, are referred to as "partials" in the music world. They are simply some multiple of the original, fundamental frequencies.

Once the input to any amplifier is increased well beyond its design limit, the output signal is either hard clipped or transformed into indistinguishable noise, depending on the amplifier's overload characteristics.

Unlike the rounded peaks of a soft-clipped waveform, hard clipping is characterised by flat, sharp-edged waveforms. This is due to the output stages driving all the way to the power supply rails, slicing the peaks off and compressing, or "crunching", the signal.

Hard clipping results in many higher-order harmonics of the fundamentals. The resulting sound is often described as "reedy", "rather harsh" and "more metallic".

A side effect called "intermodulation distortion" occurs when all these harmonics inevitably mix. The product of two frequencies is both the sum and difference of the originals, and they may not necessarily be "musically" related to the content. Therefore, intermodulation distortion is unwanted noise that is quite easily detected by the ear.

Ideal distortion?

As far as we can discern, there is no easy way of generating the ideal distortion effect. Why? Primarily

Box

your guitar

because it would be impossible to get broad agreement on what that sound is. It has more to do with music type,

personal preference and playing styles than the pure technicalities.

Many commercial distortion effects units combine both soft and hard clipping and user-accessible controls are included to provide adjustment between these two extremities, thus accommodating a range of music and styles. Some also include tone controls for increased versatility.

The *EPE* “WidgyBox” (like the name?) is based on these ideas. The design criterion was simple: it had to be uncomplicated, low-cost and easy to build. We think it will make a worthwhile addition to any guitarist’s basic effects line-up.

Reproducing the sound

Now for the \$64,000 question: if valve amplifiers already produce the desired sound, then why bother trying to reproduce it? Why not just use a valve amplifier?

Well for a start, valve amplifiers are expensive. In addition, they need to be over-driven to produce the effect. This means lots of volume, which can obviously be a real problem. In the words of one disaffected player, “I have good tone when I play loud but I get kicked out of clubs and bands”.

MAIN FEATURES

- Low cost.
- Easy to build.
- Battery-powered.
- Adjustable distortion.
- Three tone controls.
- Optional stomp switch.

Dedicated effects boxes (also known as “effects pedals” and “stomp boxes”) address these issues. They create the desired effect before the amplifier input, allowing the musician to play at any volume. They also allow easy experimentation for those in search of a unique sound. What’s more, you don’t need a valve amplifier – a (much) cheaper solid-state amplifier will suffice!

How it works

Fig.1 shows the details of our design – it’s based entirely around the TL07x series op amps. Like most effects pedals, the circuit is designed to connect directly in-line with the guitar’s output.



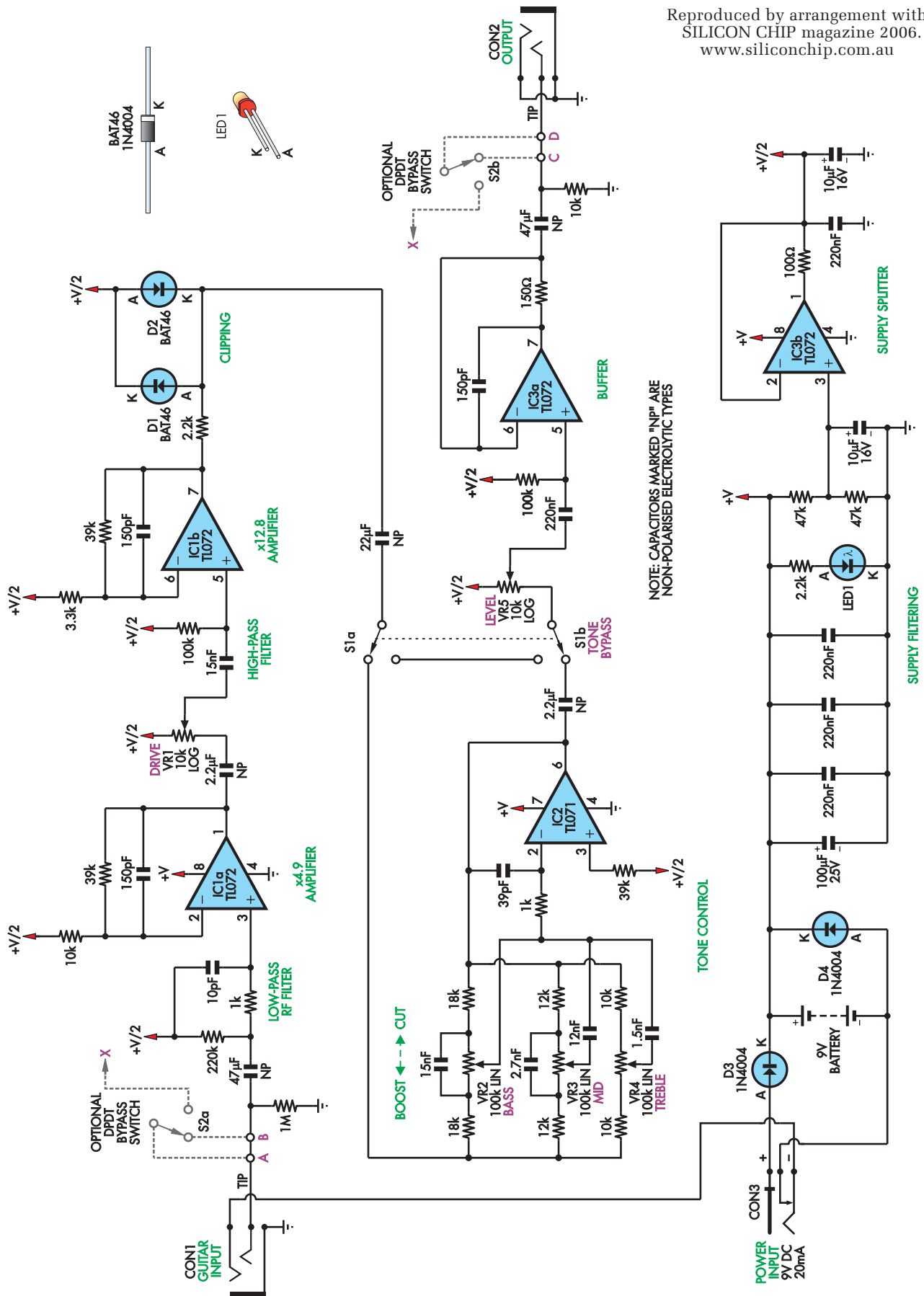


Fig.1: the circuit uses three low-cost op amps (IC1-IC3) and operates from a 9V battery. Schottky diodes D1 & D2 provide the soft clipping function, while IC1b provides hard clipping, depending on the setting of VR1.

A 47 μ F capacitor AC-couples the input to the first op amp stage (IC1a). This capacitor is much larger than you might expect in order to ensure low noise performance. As with all the following stages, IC1a's input is biased to one-half the supply rail voltage (+V/2), in this case via a 220k Ω resistor. The 1k Ω resistor and 10pF capacitor at the input act as a low-pass filter, preventing RF (radio frequency) signals from being coupled into the circuit.

IC1a is wired in a non-inverting configuration with a gain of 4.9, as set by the 39k Ω and 10k Ω feedback resistors. The 150pF capacitor in the feedback path rolls off the frequency response above the audio spectrum.

IC1a's output appears at pin 1 and is coupled via a 2.2 μ F capacitor to Drive pot VR1. This pot controls the signal level into the next stage, for reasons that will become clearer shortly.

The signal from the VR1's wiper is in turn AC-coupled to op amp IC1b via a 15nF capacitor. This capacitor also acts with a 100k Ω bias resistor to form a high-pass filter, to provide a small measure of pre-distortion equalisation. This is necessary to reduce the effects of harmonics from the lower strings. Apparently, these low frequency harmonics tend to sound a little "fruity" during chord work.

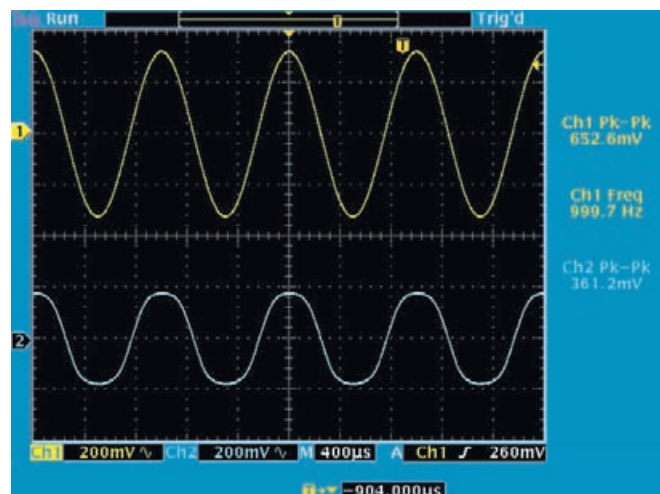


Fig.2: moderate soft clipping. The top waveform shows the signal into op amp IC1b, while the bottom waveform shows the signal across the clipping diodes (D1 & D2). Note the smooth waveform peaks. Compression is already quite noticeable, nearing a 2:1 ratio.

Effects Bypassing: The Different Methods

Generally, it's desirable to be able to switch effects in and out during a performance. A popular means of doing this is via a foot switch built into the same box that houses the electronics. This arrangement is part of all commercial effects pedals.

Another common method relies on a dedicated bypass box, which is simply wired in series with the effects input and output leads.

In the latter approach, the bypass function physically switches the effects box out of the signal path. This is termed "hard" bypassing, as opposed to "soft" bypassing, where some part of the effects electronics is still in-circuit (usually an input buffer and/or line driver).

"Hard" bypassing is a popular approach because it ensures that the effect has no impact whatsoever on the signal, especially in relation to loading or otherwise distorting the signal source. A good example of a do-it-yourself bypass box can be found on the web at www.geofex.com/Article_Folders/Millenium/millen.htm

Alternatively, the WidgyBox has provision for an internal DPDT "hard" bypass switch. It's simply a matter of removing the two wire links adjacent to the input and output sockets and wiring up switch S2 as shown on the circuit diagram (Fig.1).

We envisage an internal switch being used in conjunction with a more robust ("stomp proof") metal case!

In addition, cutting the low end response may also help with guitar pickup equalisation.

IC1b is configured as a non-inverting stage and operates with a gain of 12.8. It has two important roles, the first being to drive a pair of back-to-back diodes (D1 & D2) whose job it is to perform the soft clipping function.

Clip job

The way that this works is quite straightforward. Once the peak

signal level exceeds the forward voltage (0.2–0.4V) of the diodes, they start to conduct, thus clipping the highs and lows off the waveform. In addition, the non-linear conduction characteristic of the diodes give the peaks a smooth, rounded appearance.

Regardless of increasing drive level, the diodes continue to clip the signal to about the same voltage, resulting in even more waveform compression (and distortion).

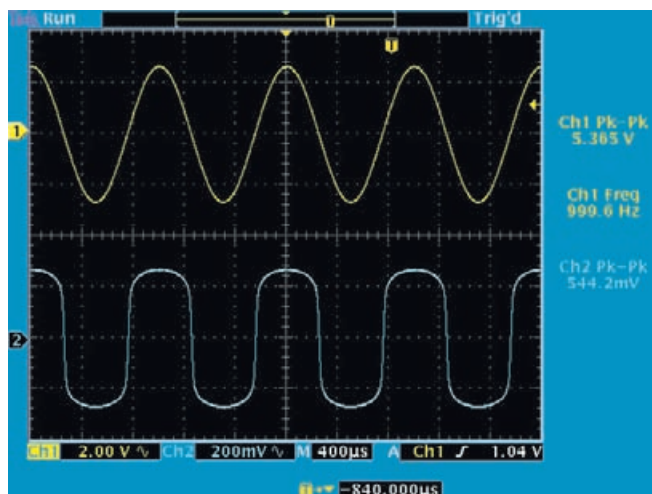


Fig.3: this is the maximum soft clipping signal, again taken across diodes D1 & D2. Note that the rising and trailing edges are almost vertical now but we still have rounded peaks. The compression is now quite high and this also imparts quite a degree of sustain.

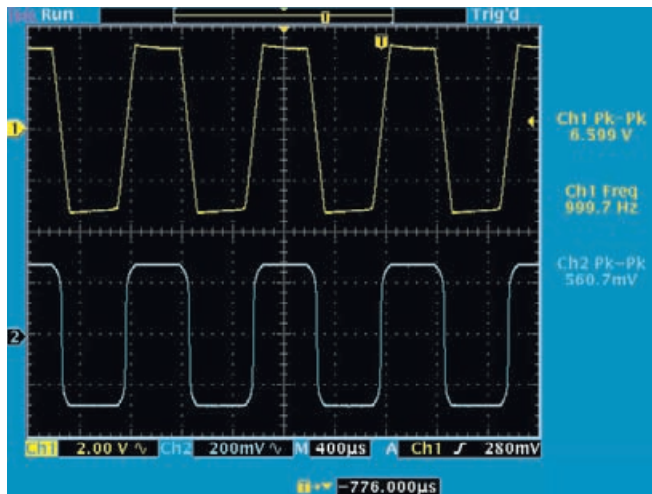


Fig.4: maximum hard (and soft) clipping. The top waveform shows the hard-clipped op amp output. At the bottom, we can see what it looks like across the diodes. The amplitude isn't much different to Fig.3 but the peaks have been "flattened".

At very high drive levels, IC1b's second role comes into play – it starts to hard clip the signal. What happens is that the amplified signal level exceeds the op amp's maximum available output swing – so it is abruptly clipped.

This is normal behaviour for any over-driven op amp and it's exactly what we need for our hard clipping function!

As a matter of interest, the TL072 clips non-symmetrically. This suggests

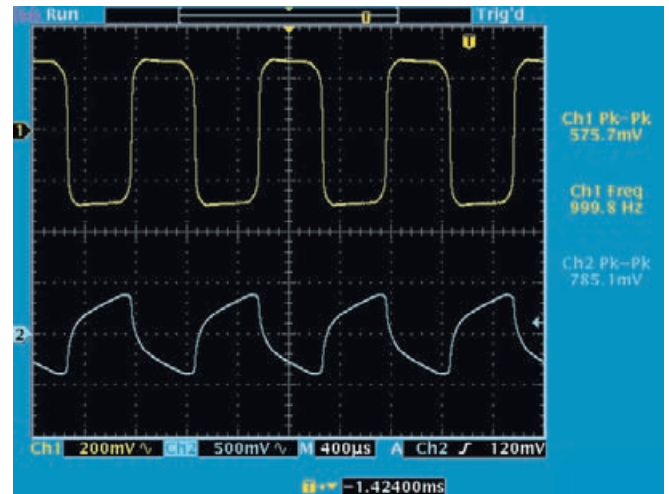


Fig.5: fiddling with the tone controls has a bigger effect than you might expect, because it's boosting or cutting the harmonics as well. Here's what the output of the box looks like (bottom waveform) when we wind up the bass boost.

that not only do we get the higher-order harmonics mentioned earlier but also a larger proportion of even rather than odd multiples.

Note that we've specified Schottky diodes for D1 & D2 as they have a lower forward voltage than the common 1N4148/1N914 varieties. This gives a larger adjustment range between soft and hard clipping, allowing more waveform compression and increasing the "sustain" effect.

Tone controls


The distorted signal is routed to a Baxandall type tone control network, based around op amp IC2 and potentiometers VR2, VR3 & VR4.

These pots and their associated resistors and capacitors form the feedback network between the op amp's inverting input and its output.

Each of the bass, mid and treble networks can be considered separately since they are connected in parallel between the signal input following IC1b and the output of IC2 at pin 6. Furthermore, the wiper of each pot is effectively connected to the inverting input (pin 2) which is a virtual ground.

Operation of the bass control is as follows: with VR2 centred, the value of resistance connected between the output from IC1b and pin 2 of IC2 is the same as that between pins 2 & 6 and this sets the gain to -1. The 15nF capacitor has no effect since it is equally balanced across the potentiometer.

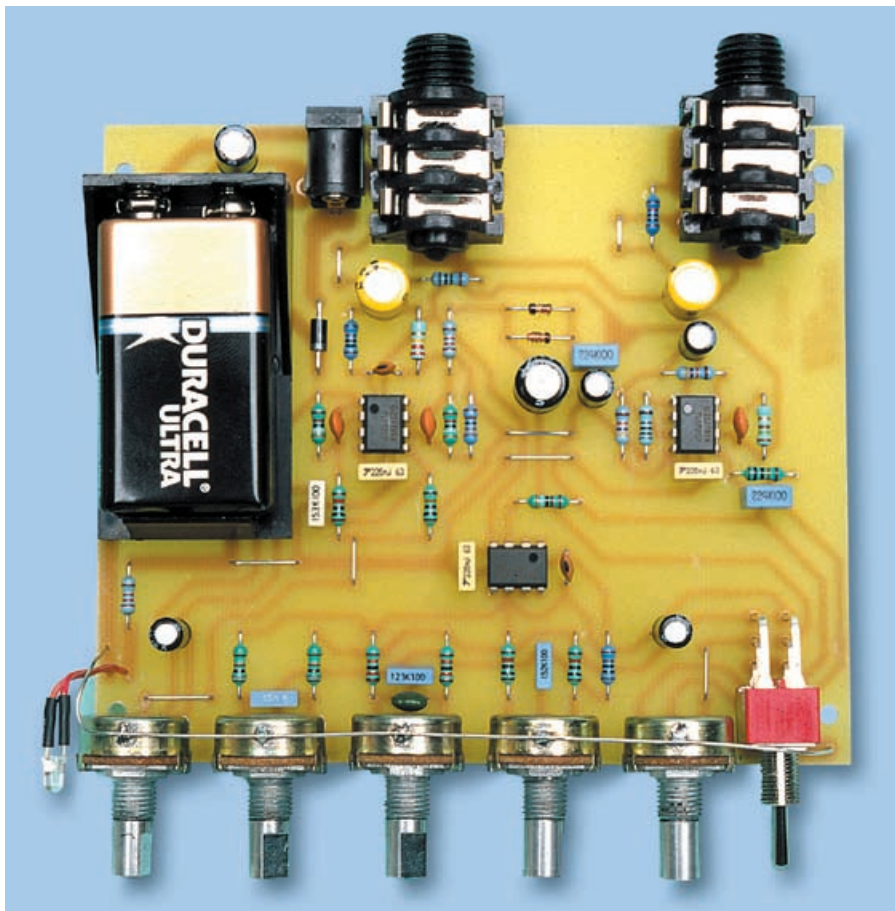If we move the wiper of VR2 to the full boost position (ie, rotate the pot



This close-up view shows the final version of the PCB. Take care to ensure that all polarised parts are installed the right way around.

Value	μ F Code	EIA Code	IEC Code
220nF	0-22 μ F	220n	224
100nF	0-1 μ F	100n	104
15nF	0-015 μ F	15n	153
12nF	0-012 μ F	12n	123
2.7nF	0-0027 μ F	2n7	272
1.5nF	0-0015 μ F	1n5	152
150pF	150pF	150p	150
39pF	39pF	39p	39
10pF	10pF	10p	10

Without the capacitor the gain would be $-119\text{k}\Omega/19\text{k}\Omega$ or -6.3 at all frequencies. But with the capacitor, the gain is high only at around 50Hz and as the frequency rises it comes back to -1 (ie, overall unity gain). Thus we have bass boost.

The midrange section works in a similar manner except that there is now a 12nF capacitor between VR3's






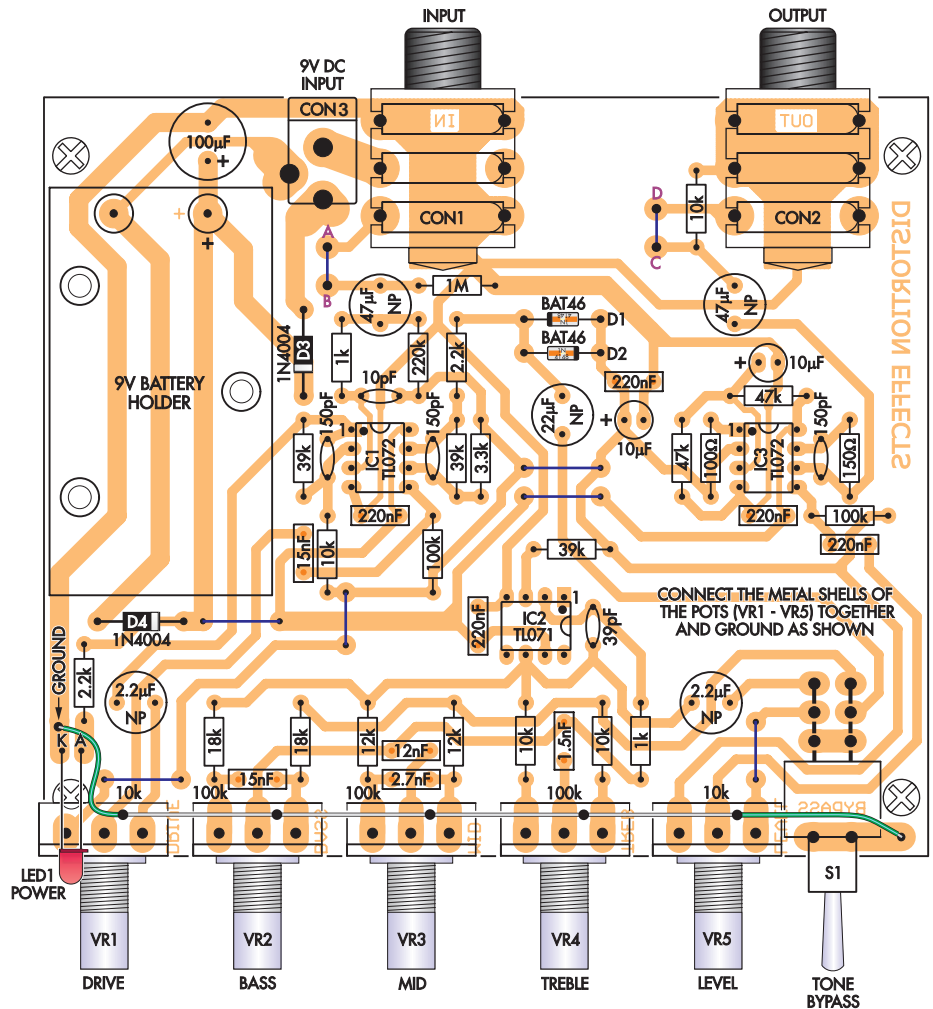 

 


 

 



Fig.6: here's how to install the parts on the PC board. Install the smaller parts first before moving on to the output sockets, the battery holder and (finally) the pots (see text).

The treble control operates with no capacitor across VR4 but has a 1.5nF

capacitor between its wiper and pin 2 to produce a high-frequency boost or cut at 10kHz. A 39pF capacitor between pins 2 & 6 of IC2 provides a high-frequency rolloff to prevent oscillation which could otherwise occur when

	No.	Value	4-Band Code (1%)	5-Band Code (1%)
	1	1MΩ	brown black green brown	brown black black yellow brown
	1	220kΩ	red red yellow brown	red red black orange brown
	2	100kΩ	brown black yellow brown	brown black black orange brown
	2	47kΩ	yellow violet orange brown	yellow violet black red brown
	3	39kΩ	orange white orange brown	orange white black red brown
	2	18kΩ	brown grey orange brown	brown grey black red brown
	2	12kΩ	brown red orange brown	brown red black red brown
	3	10kΩ	brown black orange brown	brown black black red brown
	1	3.3kΩ	orange orange red brown	orange orange black brown brown
	2	2.2kΩ	red red red brown	red red black brown brown
	2	1kΩ	brown black red brown	brown black black brown brown
	1	150Ω	brown green brown brown	brown green black black brown
	1	100Ω	brown black brown brown	brown black black black brown

Parts List

- 1 PC board coded 573, available from the *EPE PCB Service*, 117mm x 100.5mm
- 1 110 x 140 x 35mm (L x W x H) plastic instrument case
- 1 DPDT PC mount toggle switch (S1)
- 2 6.5mm PC-mount stereo switched sockets (CON1 - CON2)
- 1 2.1mm PC mount DC socket (CON3)
- 1 9V PC mount battery holder
- 3 100k Ω 16mm PC mount linear pots (VR2 - VR4)
- 2 10k Ω 16mm PC-mount log pots (VR1, VR5)
- 5 knobs to suit pots
- 20mm length of small heatshrink tubing
- 70mm length of light duty hook-up wire
- 320mm length of 0.71mm tinned copper wire

Semiconductors

- 2 TL072CP dual op amps (IC1, IC3)
- 1 TL071CP op amp IC (IC2)
- 1 3mm high-brightness red LED (LED1)
- 2 BAT43 schottky diodes (D1, D2)
- 2 1N4004 1A silicon diode (D3, D4)

Capacitors

- 1 100 μ F 25V PC electrolytic
- 2 10 μ F 16V PC electrolytic
- 2 47 μ F 16V non-polarised PC electrolytic
- 1 22 μ F 16V non-polarised PC electrolytic
- 2 2.2 μ F 16V non-polarised PC electrolytic
- 5 220nF (0.22 μ F) 50V MKT polyester
- 2 15nF (0.015 μ F) 50V MKT polyester
- 1 12nF (0.012 μ F) 50V MKT polyester
- 1 2.7nF (0.0027 μ F) 50V MKT polyester
- 1 1.5nF (0.0015 μ F) 50V MKT polyester
- 3 150pF 50V ceramic disc
- 1 39pF 50V ceramic disc
- 1 10pF 50V ceramic disc

Resistors (0.25W, 1%)

- | | |
|-----------------|-----------------|
| 1 1M Ω | 3 10k Ω |
| 1 220k Ω | 1 3.3k Ω |
| 2 100k Ω | 2 2.2k Ω |
| 2 47k Ω | 2 1k Ω |
| 3 39k Ω | 1 150 Ω |
| 2 18k Ω | 1 100 Ω |
| 2 12k Ω | |

with many commercial units, which commonly provide only one or two bands of adjustment.

Switch S1 has been included to allow you to quickly bypass the tone circuitry altogether should you wish to control it elsewhere in your setup.

Level control & output

IC2's output is AC-coupled via a 2.2 μ F capacitor to VR5. This pot allows you to set the output level to match the input, thus preventing any noticeable jump in volume when the WidgyBox is switched in and out (see the panel entitled "Effects Bypassing: The Different Methods"). From there, the signal is AC-coupled via a 220nF capacitor to op amp IC3a. This op amp is configured as a voltage follower – it simply buffers the incoming signal and passes it through unchanged.

A 150 Ω resistor decouples IC3a's output from any cable capacitance, thereby ensuring stability under all conditions. This is followed with a 47 μ F capacitor to remove the DC offset. Finally, a 10k Ω resistor terminates the output to ground, ensuring that there are no nasty clicks when the box is hot-switched into the signal path.

Power supply

In keeping with other popular effects pedals, power for the unit is provided by a 9V alkaline battery. The current drain is only about 12-15mA, so you'll get more than a day's continuous use and many days of intermittent use before a swap is required.

Alternatively, power can be provided by a 9V DC plugpack. Be aware,

the treble control is set for maximum boost. Similarly, the 1k Ω resistor in series with pin 2 is there to attenuate RF signals; it stops radio breakthrough.

Being able to boost or cut the distorted signal in three distinct bands gives you a lot of control over your sound – more, in fact, than is possible

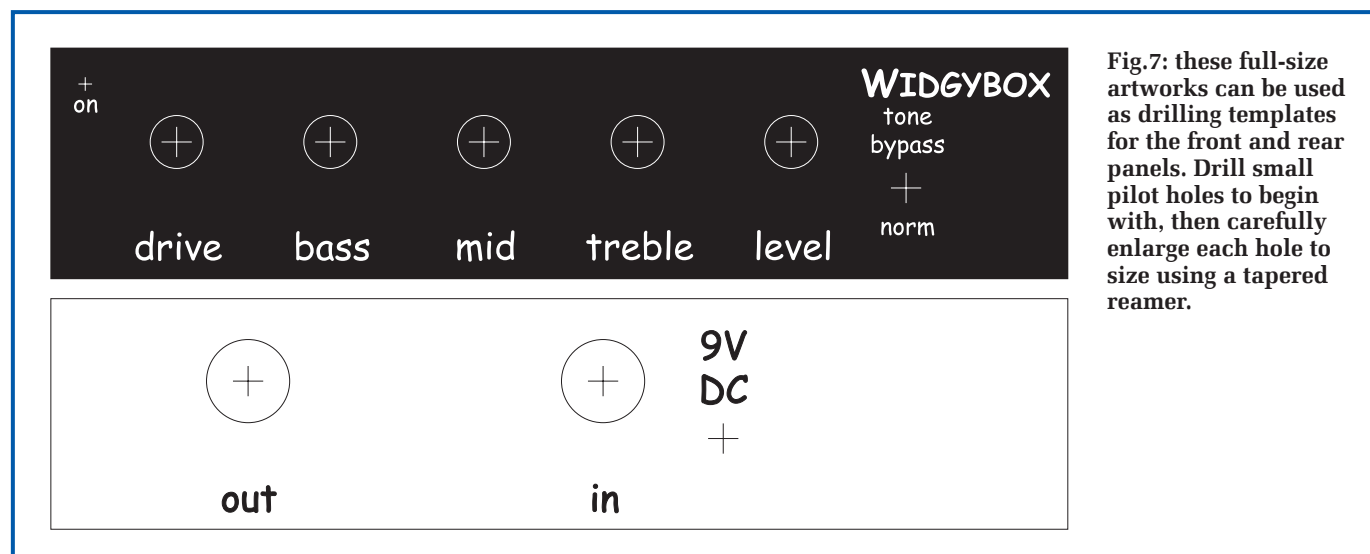


Fig.7: these full-size artworks can be used as drilling templates for the front and rear panels. Drill small pilot holes to begin with, then carefully enlarge each hole to size using a tapered reamer.

though, that most unregulated plugpacks put out much more voltage than their rating at these low current levels.

Although this won't damage your box, the higher voltage will alter the characteristics of the distortion effects at high drive settings.

If you have a plugpack with selectable output voltages, you may find that the 7.5V setting provides about 9.5V under light load, which is ideal.

Note that the negative terminal of the battery connects to earth via the switch contacts of the DC input socket (CON3) and the middle and common contacts of the guitar input socket (CON1). This means that you'll need to plug in your guitar to power up the box.

It also means that when a plug-pack jack is inserted, the battery is disconnected. This feature is very important, otherwise the plugpack would attempt to charge the battery and that could have loud and startling consequences!

Finally, the half supply voltage rail (ie, $+V/2$) needed by all of the bias networks is generated by op amp IC3b and its associated circuitry. Two 47k Ω resistors divide the +V rail in half, after which it is filtered by a 10 μ F capacitor and then buffered by op amp IC3b. A 100 Ω resistor in series with IC3b's output decouples the large 10 μ F filter capacitor.


Construction

With the exception of the power LED, all components mount on a single PC board, coded 573.

Using the overlay diagram in Fig.6 as a guide, begin by installing the eight wire links using 0.7mm tinned copper wire or similar. Note that the two links adjacent to the input and output sockets (CON1 & CON2) can be left out if you intend fitting a foot switch to the box but more on that later.

Install the low-profile components first, beginning with the resistors and diodes (D1-D3). Follow with the three op amp ICs (IC1-IC3). Make sure that you have the pin 1 (notched) end of each IC oriented as per the overlay diagram. In addition, note that IC2 is a TL071 (single) op amp, whereas the others are TL072 (dual) versions. Don't mix them up!

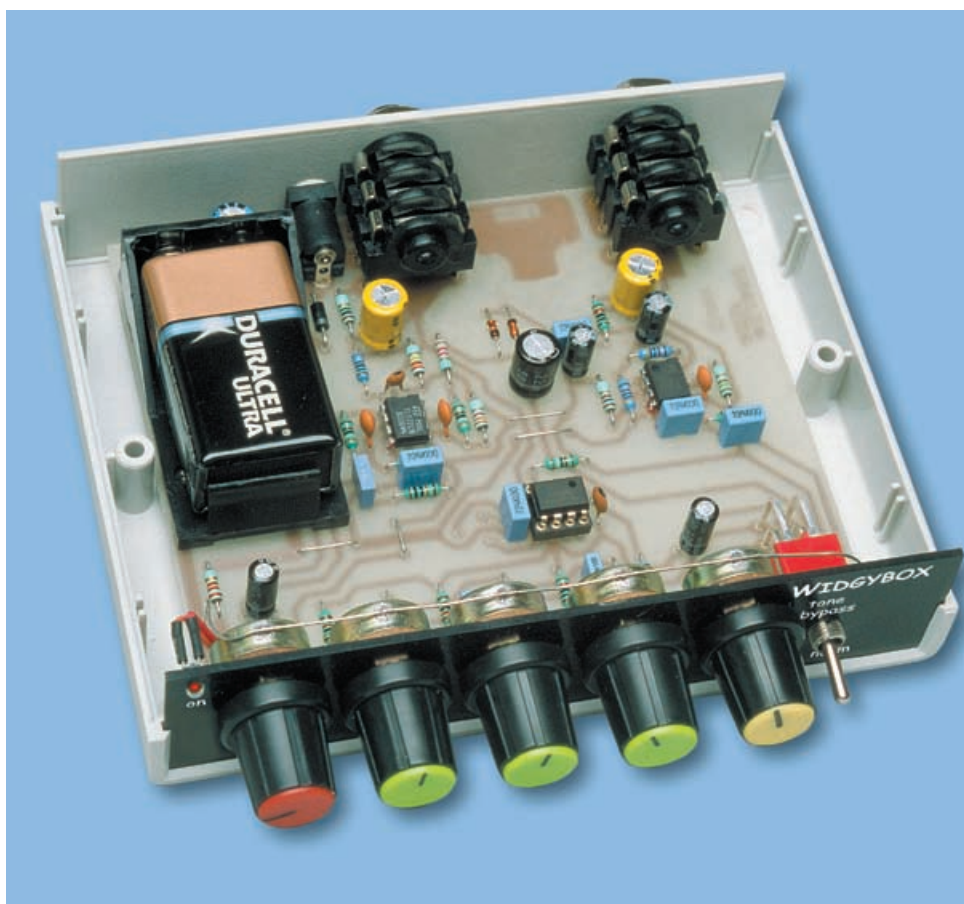The two jack sockets (CON1 & CON2) and the DC socket (CON3) can go in next. When inserting the jack sockets,



The assembled PC board fits neatly into a low-profile plastic instrument case. Note that the PC board shown here is a prototype version and differs slightly from the final version shown in Fig.6.


push them all the way down until the shoulders of all pins make contact with the PC board surface. Follow with the battery holder, which should be secured to the PC board with No. 4 \times 6mm self-tapping screws prior to soldering.

Next, install all the capacitors. The 100 μ F and two 10 μ F electrolytic capacitors are polarised and must go in the right way around. The remaining

five electrolytics are non-polarised (marked "NP" on the overlay) and can go in either way.

Potentiometers VR1-VR5 and switch S1 should be installed last of all. Start with VR1 but solder its middle pin only. Lift the board to eye level and examine the position of the pot from the front and side. It should be sitting perfectly "square".

Fig.8: having heard all the stories about valve distortion, we were consumed with curiosity and had to have a look at it ourselves. A kind gentleman loaned us his valve guitar amplifier and we captured this waveform when it was overdriven. That doesn't look too soft, does it?

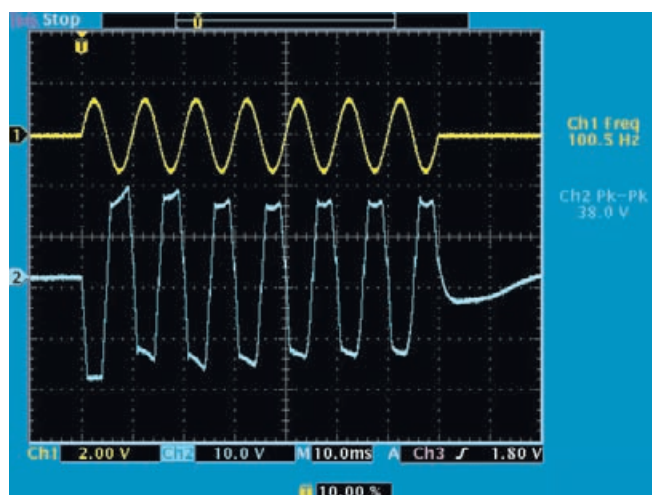



The rear panel carries the 6.5mm stereo switched sockets and includes an access hole for the DC power socket. Note that the PC board in this photo is the final version, as shown in Fig.6.

Why bother? – well, when we eventually fit the front panel, this step helps to ensure that all the pot shafts are aligned, improving appearance

and minimising stress on solder joints when the nuts are tightened.

Adjust the pot position as necessary and then solder the remaining two

pins. Repeat this procedure for the other four pots.

Finally, install the tone bypass switch (S1), ensuring that it is seated firmly on the PC board surface before soldering.

Case preparation

As supplied, the bottom half of the case contains eight mounting posts. The four outermost posts are used to support the PC board, while the four inner posts are not required and must be removed. This can be done using a chisel or an oversized drill bit.

The templates shown in Fig.7 provide the quickest and easiest method of getting all the holes in the right places for the front and rear panels. Photocopy the templates, cut them out and carefully align and tape each one to a blank panel.

First, gently centre-punch the holes directly through the templates, then remove them and drill 1mm pilot holes for each mark. Don't attempt to jump directly to a large diameter drill, as you may split a panel or get the holes off-centre. Instead, drill the holes progressively larger in several steps.

Some constructors won't have fractional drill sizes all the way up to the large diameters of the pot shafts and jack sockets. In this case, a tapered reamer is ideal for enlarging the holes to their final sizes.

Trial fit

The front panel should not be forcibly fitted over the pot shafts. If the holes are correctly sized for the shafts but the panel is still a tight fit (or won't fit!), then the holes are obviously out of alignment. Increase the hole sizes as necessary to get an easy fit. This is quite important; a good fit keeps all the pot shafts in alignment.

With the drilling done, slide the panels into place and loosely install washers and nuts on all the pots and the two jack sockets. The assembly should now slip home in the case bottom without too much trouble. Check that you can sight the four mounting post holes through the PC board holes and that the posts actually make contact with the underside of the board. If all is well, tighten up the nuts by hand.

Grounding the pots

To minimise extraneous noise, the metal shells of the pots must be

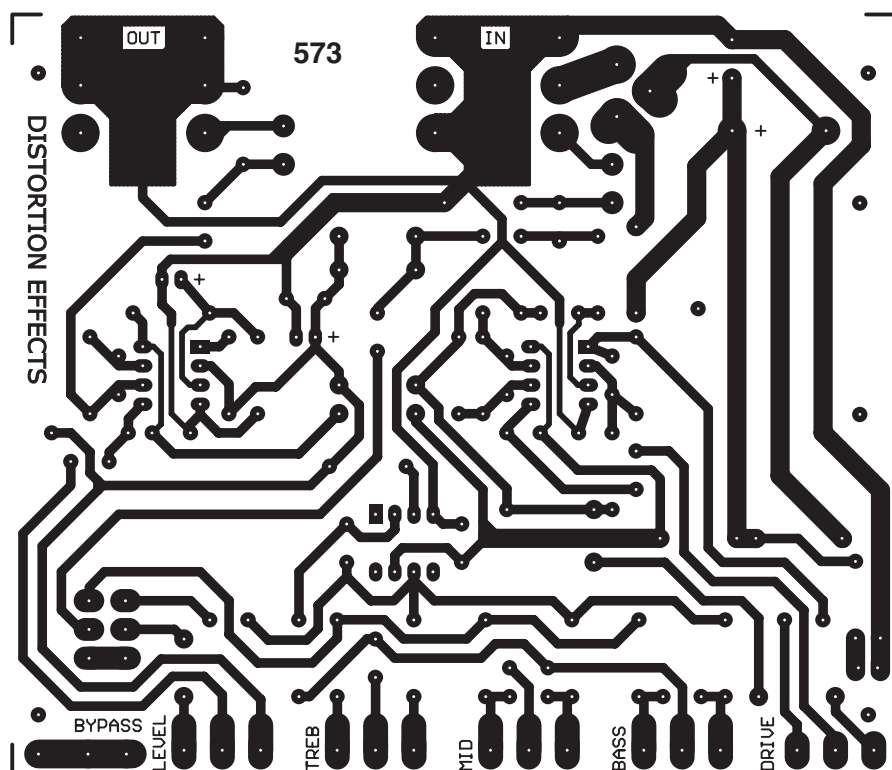


Fig.9: this is the full-size etching pattern for the PC board.

connected to the ground (0V) rail. This is achieved by soldering a single length of tinned copper wire to the metal top of each pot and terminating it to the PC board at either end. The overlay diagram (Fig.6) and the various photos show where to position this wire.

In order to get the solder to adhere to the pots, remove a small spot of the cadmium plating on each pot with an ink rubber or scouring pad and clean the area with alcohol. That done, pre-tin the spot with a fairly hot iron and large gauge multicore solder before attempting to attach the earth wire.

Installing the LED

To mount the LED, first strip and tin the ends of two 30mm lengths of light-duty hook-up wire. That done, shorten the LED leads to about 8mm, solder one end of each wire to a LED lead and insulate the connections with heatshrink tubing.

Finally, slip the LED into position in the front panel and solder the two leads to the PC board as shown in Fig.6. Be sure to install the LED with the correct polarity, though. The flat edge on the LED body goes towards the edge of the case (see Figs.1 & 6).

If necessary, the LED can be fixed in position with a spot of glue or silicone sealant.

Testing

A few quick voltage measurements around the circuit will help to confirm that your project is ready for use. You'll need a fresh 9V battery, a mono jack plug and a multimeter.

Fit the battery and insert the plug in the input socket (CON1). The plug can be on one end of your guitar lead but don't connect anything to the other end just yet!

As soon as the plug is inserted, the power LED should light. If it doesn't, then remove the plug immediately and check the orientation of the LED. Also, check that there is continuity through the DC socket (CON3) switch contacts, which can be identified by tracing the negative connection from the battery.

If the above checks don't identify the problem, then suspect a short or low resistance between the +V rail (battery positive) and ground (battery negative). You may have inadvertently reversed one of the ICs or perhaps there is a solder bridge between tracks somewhere. Follow the +V trace around the board to track it down.

Sound Fun: Experimenting With The Circuit

Like to experiment a little? Then check out these ideas!

As explained in the text, the high-pass filter formed by the 15nF capacitor and 100k Ω resistor at the input of IC1b provides for some pre-distortion equalisation.

The 3dB point of this filter is around 100Hz. A higher or lower point may better suit your system. We suggest an upper limit of about 300Hz (no lower limit). Here are some example values: for a 194Hz 3dB point, use 8.2nF instead of 15nF; for 284Hz, use 5.6nF.

It is also possible to experiment with the distortion-making section of the circuit. For example, replacing one of the Schottky diodes with a common 1N4148 will create non-symmetrical clipping for quite a different sound. You could also substitute germanium diodes, which have softer turn-on characteristics. Have fun!

OK, let's assume your LED lights up. Next, we'll check that power arrives at each op amp IC supply pin.

Set your multimeter to read DC volts and measure between pins 4 & 8 of both IC1 and IC3. That done, repeat this measurement between pins 4 & 7 of IC2. In all cases, the reading should be about 9.2V.

Now touch the negative probe of your meter to the negative battery terminal and the positive probe to pin 2 of IC2. Your reading should be very close to half the voltage measured above (about 4.6V).

Final touches

The next step is to secure the PC board to the case posts with four No. 4 \times 6mm self-tapping screws. Before tightening the screws, it's a good idea

to temporarily loosen off the pot and jack socket nuts, so that the assembly settles "comfortably" into position.

The final job is to shorten the pot shafts to match the knobs. Before doing this, screw the top half of the case into position and tighten up all of the pot nuts.

The procedure now is to grip the tip of each pot shaft (in turn) in a vice, starting with VR1. You can then carefully cut off the unneeded section of the shaft using a hacksaw. For our prototype, only 14mm of shaft length (measured from the surface of the panel) was required for the push-on type knobs. Be sure to support the weight of the assembly during the cutting.

That's it – your WidgyBox is ready to rock! **EPE**

Help – It Doesn't Work!

Before doing anything else, double-check all component values against the overlay diagram. If that doesn't turn up anything, then some detective work is in order.

If you have no output at all, then a few additional DC voltage measurements may help to narrow the problem down to a particular op amp and/or it's immediate circuitry.

Apply power and wait at least 10 seconds for the bias networks to fully charge. Don't apply a signal to the input or connect anything to the output socket during these checks.

Connect your multimeter's negative probe to battery negative and touch the positive probe to each op amp output in turn (IC1a pin 1, IC1b pin 7, IC2 pin 6 and IC3a pin 7). Although the readings will vary slightly, they should all be close to one-half battery voltage. A large variation in any reading indicates a problem in the immediate vicinity.

Alternatively, if you have output signal but varying the drive pot doesn't change the distortion level, then suspect a problem with the feedback circuitry around IC1a or IC1b.

TEACH-IN 2006

Part Eight – Digital Electronics: Introducing logic circuits; truth tables; logic families; logic gates.

MIKE TOOLEY BA



Our Teach-In 2006 series provides a broad-based introduction to electronics for the complete newcomer. The series also provides the more experienced reader with an opportunity to “brush up” on topics which may be less familiar. This month we shall be delving into the world of digital electronics – an area that has had an increasing impact on our lives during the last four decades

Digital electronics has brought us the microprocessor and microcomputer as well as a means of exchanging vast amounts of data through local and global networks. But that's not all – digital electronics is used in almost every item of consumer electronic equipment, including CD and DVD players, digital TV and digital audio broadcasting (DAB).

Part Eight of our *Teach-In* series starts by introducing the basic logic functions (AND, OR, NAND, NOR, etc.) together with the symbols and truth tables that describe the operation of the most common logic gates. We then show how these gates can be used in simple combinational logic circuits before moving on to introduce bistable devices, counters and shift registers. Our Practical Investigations this month introduce you to the operation of some simple CMOS logic circuits.

Logic

We all make decisions based on logic in our everyday lives. The sort of decisions that we make are invariably conditional (i.e. they depend on a particular set of circumstances) and they often take the form:

If (condition) then (action).

For example:

If cold then put on the heating

or

If thirsty then go to the bar

We also make compound decisions that are based on more than one set of circumstances and can take the form:

If (condition 1) or (condition 2) then (action).

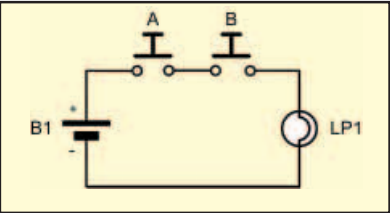


Fig.8.1. AND switch and lamp logic

or

If (condition 1) and (condition 2) then (action).

For example:

If hungry or thirsty then go to the cafe

or

If cold and dark then go to bed

Another possibility is that we might want to make a decision based on the absence of a condition rather than its presence.

For example:

If (condition 1) or (condition 2) and not (condition 3) then (action).

An example of this might be:

If hungry or thirsty and not raining then walk to the pub

The important words in the above conditional statements are “and”, “or” and “not”. These words describe logical conditions and we will next look at ways in which electronic circuits can emulate the “and” and “or” logic function using circuits that involve nothing more than batteries, switches and lamps.

Logic Circuits

Logic circuits are the basic building blocks of digital circuits and systems and, as their name suggests, they are circuits that are capable of making logical decisions.

Consider the simple circuit shown in Fig.8.1. In this circuit a battery, B1, is connected to a lamp, LP1, via two switches, A and B. It should be obvious that the lamp will only operate when both of the switches are closed (i.e. both A AND B are closed).

Switch, A	Switch, B	Lamp, LP1
Open	Open	Off
Open	Closed	Off
Closed	Open	Off
Closed	Closed	On

Fig.8.2. Possible states for the circuit of Fig.8.1

Let's look at the operation of the circuit in a little more detail. Since there are two switches (A and B) and there are two possible states for each switch (open or closed), there is a total of four possible conditions for the circuit. We can summarize these conditions in Fig.8.2.

Note that the two states (i.e. open or closed) are mutually exclusive and that the switches cannot exist in any other state than completely open or completely closed. Because of this, we can represent the state of

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Fig.8.3. Truth Table for the AND switch and lamp logic

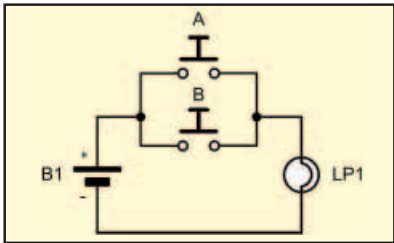


Fig.8.4. OR switch and lamp logic

Switch, A	Switch, B	Lamp, LP1
Open	Open	Off
Open	Closed	On
Closed	Open	On
Closed	Closed	On

Fig.8.5. Possible states for the circuit of Fig.8.4.

the switches using the binary digits, 0 and 1, where an open switch is represented by 0 and a closed switch by a 1. Furthermore, if we assume that “no light” is represented by a 0 and “light on” is represented by a 1, we can rewrite Fig.8.2 in the form of a Truth Table as shown in Fig.8.3, where Y is the result of the combination of A and B.

Fig.8.4 shows another circuit with two switches. This circuit differs from that shown in Fig.8.1 by virtue of the fact that the two switches are connected in *parallel* rather than in *series*. In this case the lamp will operate when either of the two switches is closed (in other words, when A OR B is closed).

As before, there is a total of four possible conditions for the circuit. We can summarize these conditions in Fig.8.5. Once again, adopting the convention that an open switch can be represented by 0 and a closed switch by 1, we can rewrite the truth table in terms of the binary states as shown in Fig.8.6.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Fig.8.6. Truth Table for the OR switch and lamp logic

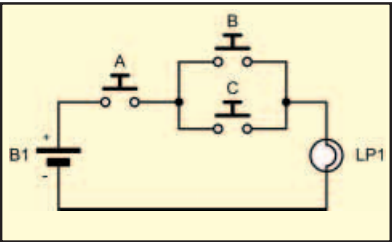


Fig.8.7. Simple switching circuit – see Example 8.1

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Fig.8.8. Truth Table for the simple switching circuit shown in Fig.8.7.

Example 8.1

Fig.8.7 shows a simple switching circuit. Describe the logical state of switches A, B and C in order to operate the lamp.
In order to operate the lamp, switch A AND either switch B OR switch C must be operated. The truth table is shown in Fig.8.8.

Check Point 8.1

Logic circuits involve signals that can only exist in one of two, mutually exclusive, states. These two states are usually denoted by 1 and 0, “on” or “off”, “closed” and “open”, etc.

Logic Function	Symbols		Truth Table															
	MIL/ANSI	BS																
Buffer			<table><tr><th>X</th><th>Y</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	X	Y	0	0	1	1									
X	Y																	
0	0																	
1	1																	
Inverter (NOT)			<table><tr><th>X</th><th>Y</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	X	Y	0	1	1	0									
X	Y																	
0	1																	
1	0																	
2-input AND			<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1
A	B	Y																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
2-input NAND			<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0
A	B	Y																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
2-input OR			<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1
A	B	Y																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
2-input NOR			<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0
A	B	Y																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
2-input Exclusive-OR			<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	0
A	B	Y																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
2-input Exclusive-NOR			<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	1
A	B	Y																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Fig.8.9. Logic gate symbols and truth tables

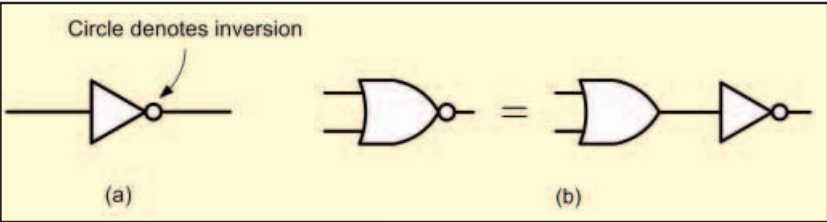


Fig.8.10. Logic gates with inverted outputs

Logic Gates

Logic gates are circuits designed to produce the basic logic functions, AND, OR, NOT, etc. These circuits are designed to be interconnected into larger, more complex, logic circuit arrangements. Each type of logic gate has its own symbol and in Fig.8.9 we have shown both the British Standard

(BS) symbol together with the more universally accepted American Standard (MIL/ANSI) symbol. Note that, while inverters and buffers each have only one input, exclusive-OR gates have two inputs and the other basic gates (e.g. AND, OR, NAND and NOR) are commonly available with up to eight inputs.

Some of the logic gates shown in Fig.8.9 are said to have inverted outputs. These gates are the NOT, NAND, NOR and Exclusive-NOR and the small circle at the output of the gate (see Fig.8.10a) indicates this inversion. It is important to note that the output of an inverted gate (e.g. NOR) is identical to that of the same (i.e. non-inverted) function with its output connected to an inverter (or NOT gate) as shown in Fig.8.10b.

The logical function of a logic gate can also be described using Boolean notation. In this type of notation the OR function is represented by a “+” symbol, the AND function by a “-” sign, and the NOT function by an overscore or “/”. Thus the output, Y, of an OR gate with inputs A and B can be represented by the Boolean algebraic expression:

$$Y = A + B$$

Similarly, the output of an AND gate can be shown as:

$$Y = A - B$$

We shall now briefly examine the logical functions of each of the basic logic gates shown in Fig.8.9:

Buffers

Buffers do not affect the logical state of a digital signal (i.e. a logic 1 input results in a logic 1 output whereas a logic 0 input results in a logic 0 output). Buffers are normally used to provide extra current drive at the output but can also be used to regularize the logic levels present at an interface. The Boolean expression for the output, Y, of a buffer with an input, X, is:

$$Y = X$$

Inverters

Inverters are used to *complement* the logical state (i.e. a logic 1 input results in a logic 0 output and vice versa). Inverters also provide extra current drive and, like buffers, are used in interfacing applications where they provide a means of regularizing logic levels present at the input or output of a digital system. The Boolean expression for the output, Y, of an inverter with an input, X, is:

$$Y = /X \text{ (or } Y = \overline{X})$$

AND Gates

AND gates will only produce a logic 1 output when all inputs are simultaneously at logic 1. Any other input combination results in a logic 0 output. The Boolean expression

for the output, Y, of an AND gate with inputs, A and B, is:

$$Y = A - B$$

OR Gates

OR gates will produce a logic 1 output whenever any one, or more, inputs are at logic 1. Putting this another way, an OR gate will only produce a logic 0 output whenever *all* of its inputs are simultaneously at logic 0. The Boolean expression for the output, Y, of an OR gate with inputs, A and B, is:

$$Y = A + B$$

NAND Gates

NAND (i.e. NOT-AND) gates will only produce a logic 0 output when all inputs are simultaneously at logic 1. Any other input combination will produce a logic 1 output. A NAND gate, therefore, is nothing more than an AND gate with its output inverted! The circle shown at the output denotes this inversion. The Boolean expression for the output, Y, of a NAND gate with inputs, A and B, is:

$$Y = A - B$$

NOR Gates

NOR (i.e. NOT-OR) gates will only produce a logic 1 output when all inputs are simultaneously at logic 0. Any other input combination will produce a logic 0 output. A NOR gate, therefore, is simply an OR gate with its output inverted. A circle is again used to indicate inversion. The Boolean expression for the output, Y, of a NOR gate with inputs, A and B, is:

$$Y = A + B$$

Exclusive-OR Gates

Exclusive-OR gates will produce a logic 1 output whenever *either* one of the two inputs is at logic 1 and the other is at logic 0. Exclusive-OR gates produce a logic 0 output whenever both inputs have the same logical state (i.e. when both are at logic 0 or both are at logic 1). The Boolean expression for the output, Y, of an exclusive-OR gate with inputs, A and B, is:

$$Y = (A - /B) + (/B - /A) \text{ (or } Y = (A - \overline{B}) + (\overline{B} - \overline{A}))$$

Exclusive-NOR Gates

Exclusive-NOR gates will produce a logic 0 output whenever *either* one of the two inputs is at logic 1 and the other is at

logic 0. Exclusive-NOR gates produce a logic 1 output whenever both inputs have the same logical state (i.e. when both are at logic 0 or both are at logic 1). The Boolean expression for the output, Y, of an exclusive-NOR gate with inputs, A and B, is:

$$Y = (/A - /B) + (B - /A) \text{ (or } Y = (\overline{A} - \overline{B}) + (B - \overline{A}))$$

Check Point 8.2

The logical function of a combinational logic circuit (i.e. an arrangement of logic gates) can be described by a truth table or by using Boolean algebra.

Combinational Logic

By using a standard range of logic levels (i.e. voltage levels used to represent the logic 1 and logic 0 states) logic circuits can be combined together in order to solve complex logic functions.

Example 8.2

A logic circuit is to be constructed that will produce a logic 1 output whenever two, or more, of its three inputs are at logic 1.

This circuit could be more aptly referred to as a “majority vote” circuit. Its truth table is shown in Fig.8.11. Fig.8.12 shows the logic circuitry required.

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Fig.8.11. Truth Table for Example 8.2

Example 8.3

Show how an arrangement of AND, OR and NOT gates can be used to produce the exclusive-OR function.

In order to solve this problem, consider the Boolean expression for the exclusive-OR function:

$$Y = (A - /B) + (B - /A)$$

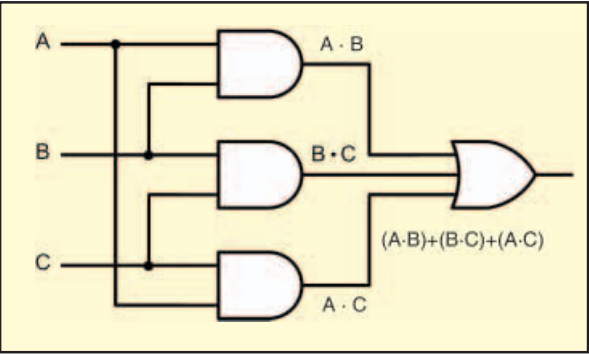


Fig.8.12. Majority vote logic circuit

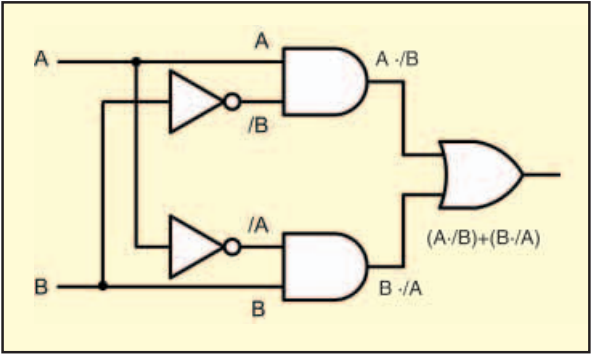


Fig.8.13. An exclusive-OR gate produced from AND, OR and NOT gates

where $\neg A$ and $\neg B$ can be obtained by simply inverting A and B respectively. Then, $A - \neg B$ and $B - \neg A$ can be obtained using two two-input AND gates. Finally, these two can be applied to a two-input OR gate in order to obtain the required logic function, $(A - \neg B) + (B - \neg A)$. The complete solution is shown in Fig.8.13.

Questions 8.1

- Q8.1. Show how three two-input AND gates can be connected together to form a four-input AND gate.
- Q8.2. Show how three two-input OR gates can be connected together to form a four-input OR gate.
- Q8.3. Draw the truth table for the logic gate arrangement shown in Fig.8.14.
- Q8.4. State the Boolean logic expression for the output of each of the gate arrangements shown in Fig.8.15.
- Q8.5. Devise a logic gate arrangement that provides an output described by the truth table shown in Fig.8.16.

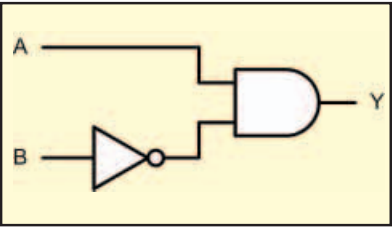


Fig.8.14. See Questions 8.1

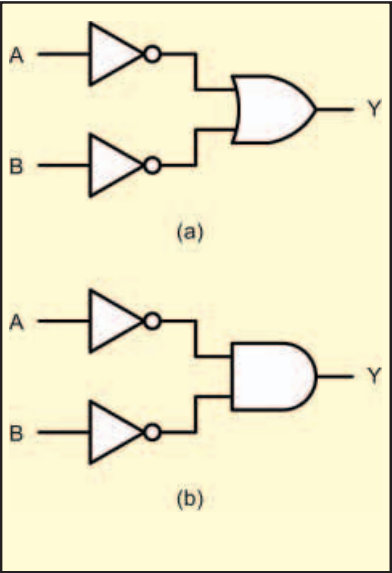


Fig.8.15. See Questions 8.1

Bistables

The output of a bistable circuit has two stable states (logic 0 or logic 1). Once set in one or other of these states, the output of a bistable will remain at a particular logic level

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

for an indefinite period until *reset*. A bistable thus forms a simple form of memory as it remains in its latched state (either *set* or *reset*) until a signal is applied to it in order to change its state (or until the supply is disconnected).

The simplest form of bistable is the R-S bistable. This device has two inputs, SET and RESET, and complementary outputs, Q and \bar{Q} . A logic 1 applied to the SET input will cause the Q output to become (or remain at) logic 1 while a logic 1 applied to the RESET input will cause the Q output to become (or remain at) logic 0. In either case, the bistable will remain in its SET or RESET state until an input is applied in such a sense as to change the state.

Two simple forms of R-S bistable based on cross-coupled logic gates are shown in Fig.8.17. Fig.8.17a is based on cross-coupled two-input NAND gates while Fig.8.17b is based on cross-coupled two-input NOR gates.

Unfortunately, the simple cross-coupled logic gate bistable has a number of serious shortcomings (consider what would happen if a logic 1 was simultaneously present on both the SET and RESET inputs!) and practical forms of bistable make use of much improved purpose-designed logic circuits such as D-type and J-K bistables.

The D-type bistable has two inputs: D (standing variously for *data* or *delay*) and CLOCK (CLK). The data input (logic 0 or logic 1) is clocked into the bistable such that the output (Q) state only changes when the clock changes state. Operation is thus said to be *synchronous*. Additional subsidiary inputs (which are invariably active low) are provided which can be used to directly set or reset the bistable. These are usually called PRESET (PR) and CLEAR (CLR). D-type bistables are

Fig.8.16. See Questions 8.1

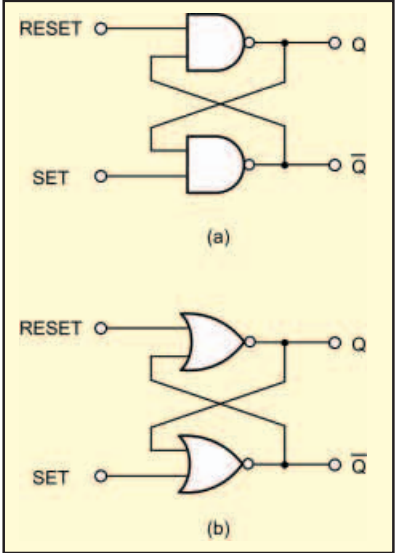


Fig.8.17. Simple R-S bistables (a) based on NAND gates and (b) based on NOR gates

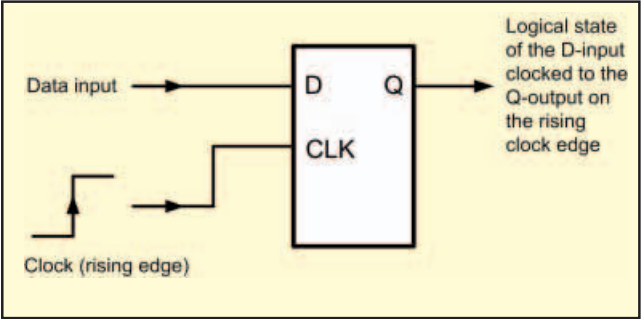


Fig.8.18. The D-type bistable

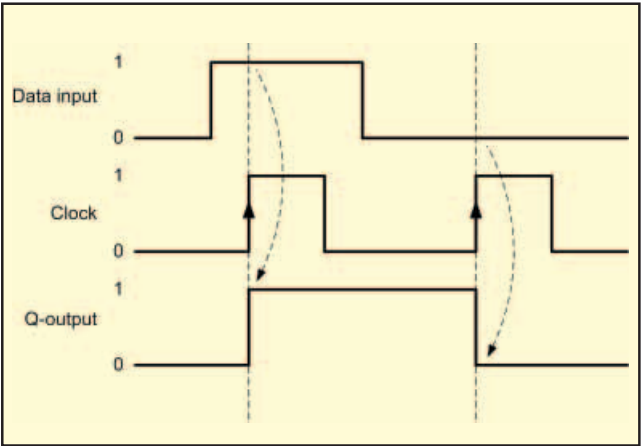


Fig.8.19. Timing diagram for the D-type bistable

used both as latches (a simple form of memory) and as binary dividers. The simple circuit arrangement in Fig.8.18 together with the *timing diagram* shown in Fig.8.19 illustrate the operation of D-type bistables.

J-K bistables (see Fig.8.20) have two clocked inputs (J and K), two direct inputs (PRESET and CLEAR), a CLOCK (CLK) input, and outputs (Q and \bar{Q}). As with R-S bistables, the two outputs are complementary (i.e. when one is 0 the other is 1, and vice

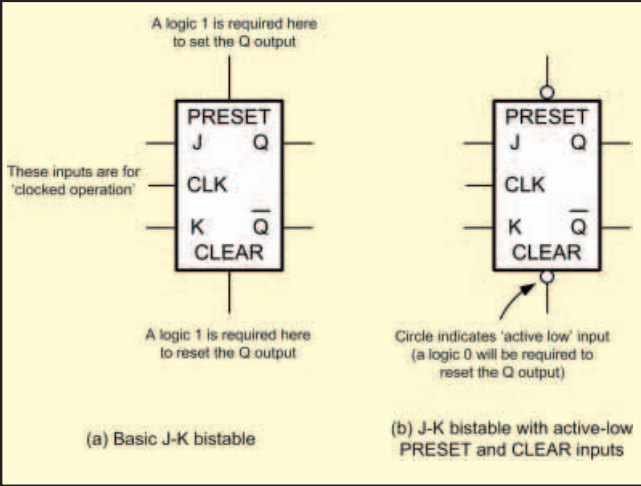


Fig.8.20. J-K bistable

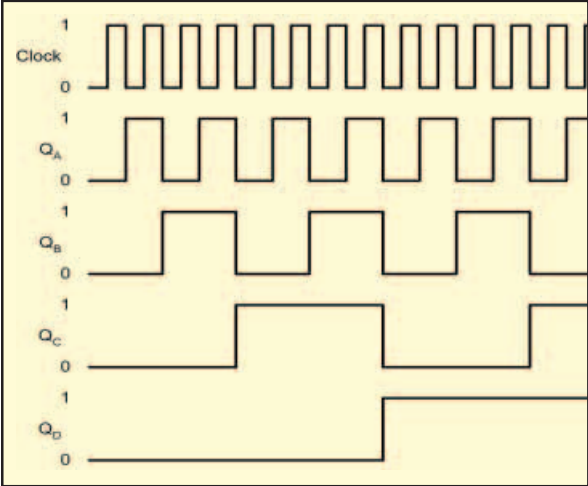


Fig.8.23. Timing diagram for the four-stage binary counter

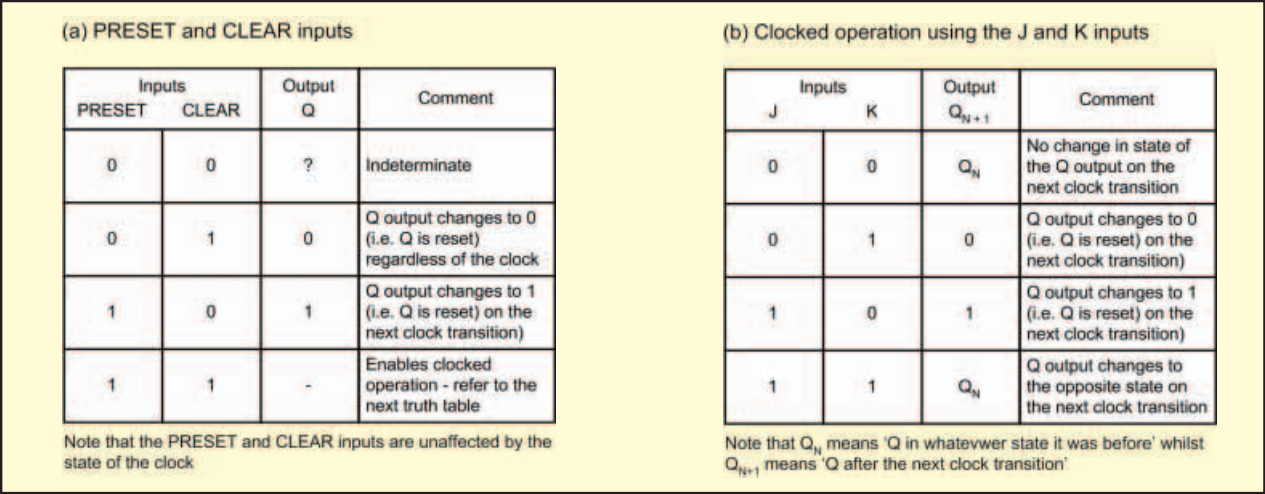


Fig.8.21. J-K bistable operation

versa). Similarly, the PRESET and CLEAR inputs are invariably both active low (i.e. a 0 on the PRESET input will set the Q output to 1 whereas a 0 on the CLEAR input will set the Q output to 0). Fig.8.21 summarizes the input and corresponding output states of a J-K bistable for various input states. J-K bistables are the most sophisticated and flexible of the bistable types and they can be configured in various ways, including binary dividers, shift registers, and latches.

Fig.8.22 shows the arrangement of a four-stage binary counter based on J-K bistables. The timing diagram for this circuit is

shown in Fig.8.23. Each stage successively divides the clock input signal by a factor of two. Note that a logic 1 input is transferred to the respective Q-output on the *falling* edge of the clock pulse and all J and K inputs must be taken to logic 1 to enable binary counting.

Fig.8.24 shows the arrangement of a four-stage shift register based on J-K bistables. The timing diagram for this circuit is shown in Fig.8.25. Note that each stage successively feeds data (Q output) to the next stage. Note that all data transfer occurs on the falling edge of the clock pulse.

Check Point 8.3

Bistable devices provide us with a way of storing a transient logical state. More advanced bistable devices (such as J-K bistables) can be configured for use in a variety of different ways, including operation as counters and shift registers.

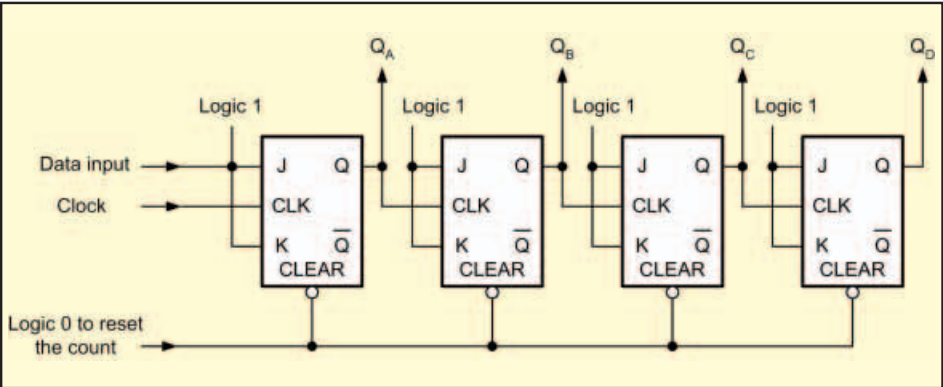


Fig.8.22. Four-stage binary counter using J-K bistables

Logic Families

The task of realizing a complex logic circuit is made simple with the aid of digital integrated circuits which are classified according to the semiconductor technology used in their fabrication (the logic family to which a device belongs is largely instrumental in determining its operational characteristics, such as power consumption, speed, and immunity to noise).

The two basic logic families are complementary metal oxide semiconductor (CMOS) and transistor-transistor logic (TTL). Each of these families is then further subdivided into classes that are based on refinements of the technology,

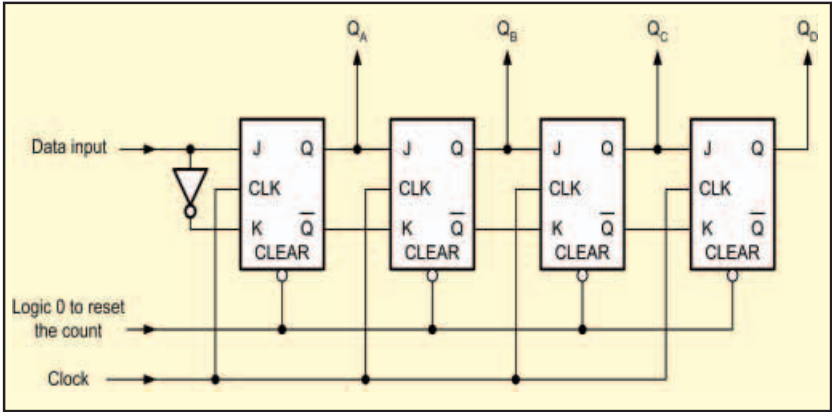


Fig.8.24. Four-stage shift register using J-K bistables

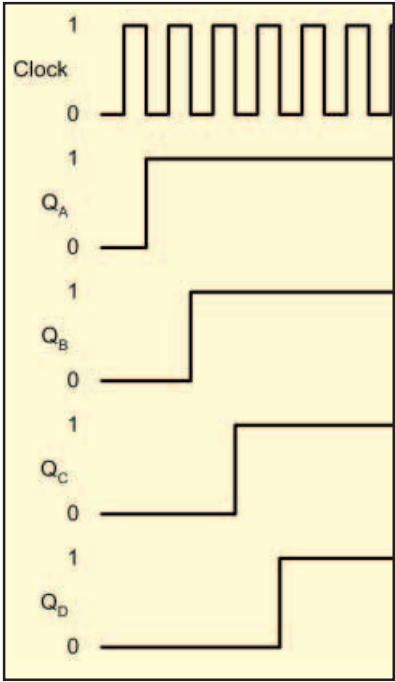


Fig.8.25. Timing diagram for the four-stage shift register

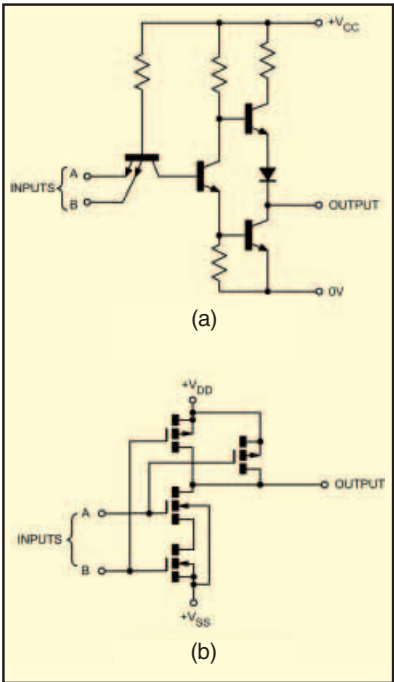


Fig.8.26. Representative internal circuitry for a two-input logic gate in (a) standard TTL and (b) standard CMOS technology

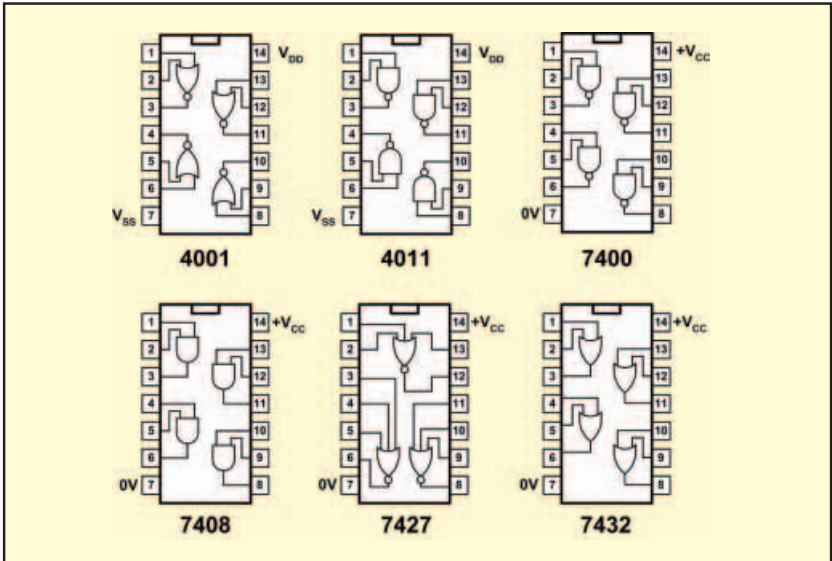


Fig.8.27. Pin connections for the DIL packaged versions of some common CMOS and TTL devices

such as “high-current” (or *buffered* output), low-noise, etc. Representative circuits for a basic two-input NAND gate using TTL and CMOS technology are shown in Fig.8.26a and Fig.8.26b, respectively.

The most common family of TTL logic devices is known as the 74-series. Devices from this family are coded with the prefix number 74, for example, 7400. Variants within the family are then distinguished by letters which follow the initial prefix, for example:

74F00 a device that uses fast TTL technology and operates at higher speed than the 7400 with which it is logic and pin-compatible

74LS08 a device that is logic and pin-compatible with the 7408 but which uses *low-power Schottky* technology

74HCT74 a high-speed CMOS version of the 7474 which has CMOS-compatible inputs

74ALS32 a device that is logic and pin-compatible with the 7432 but which uses *advanced low-power Schottky* technology

The most common family of CMOS devices is known as the 4000-series. Variants within the family are identified by the suffix letters, for example:

4001UB a standard (un-buffered) CMOS devices that is logic and pin-compatible with the 4001B

4011B a device that is logic and pin-compatible with the 4001UB but which has buffered outputs

4069UB a device that is logic and pin-compatible with the 4069B but which has unbuffered outputs

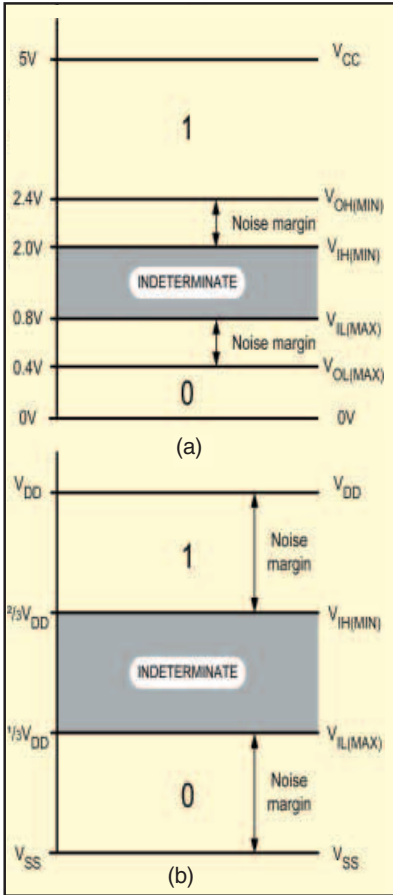


Fig.8.28. Logic levels for (a) standard TTL and (b) standard CMOS logic devices

It is important to note that manufacturers often add their own prefix and suffix letters to a basic device code. Some typical TTL and CMOS devices supplied in standard dual-in-line (DIL) packages are shown in Fig.8.27. Note that these devices are also available in different package styles, such as leadless flat packages designed for surface mounting.

Finally, it is also worth noting that the vast majority of logic devices and other digital integrated circuits are marked with a four digit date code. The code often appears alongside or below the device code. The first two digits of this code give the year of manufacture while the last two digits specify the week of manufacture.

Logic Levels

Logic levels are simply the range of voltages used to represent the logic states 0 and 1. The logic levels for CMOS differ markedly from those associated with TTL. In particular, CMOS logic levels are relative to the supply

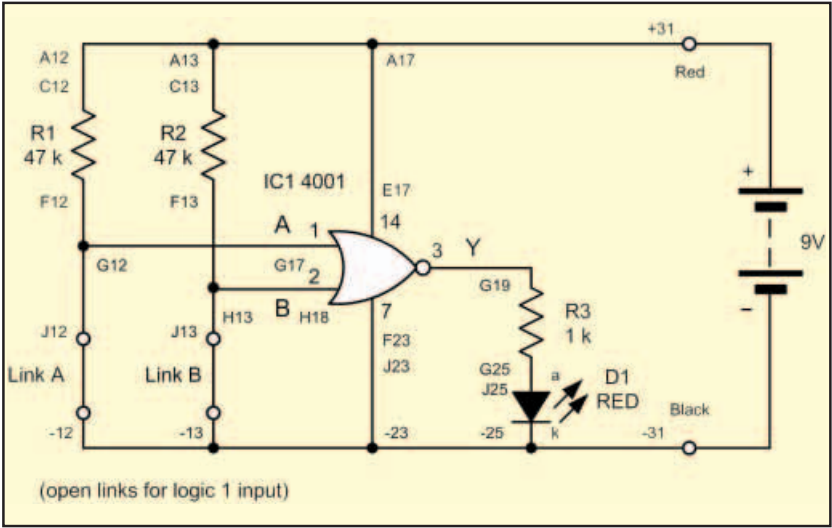


Fig.8.29. Circuit diagram for Practical Investigation 8.1

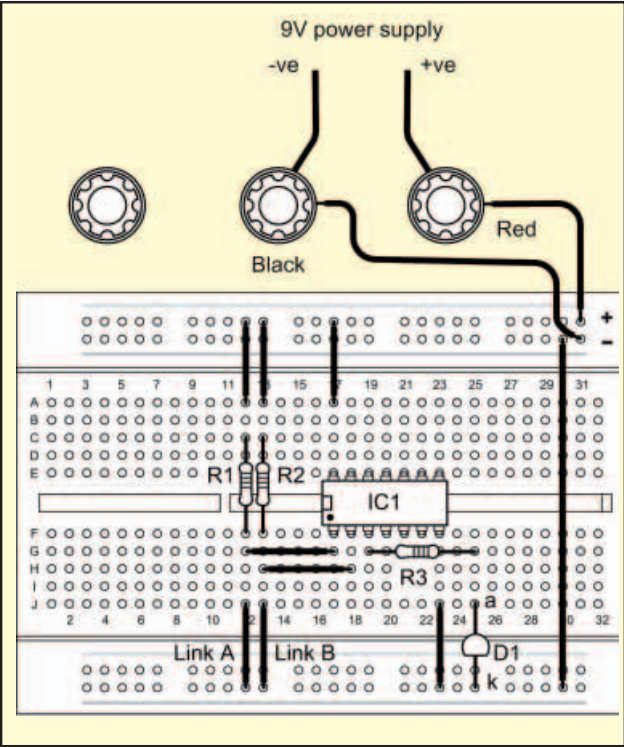


Fig.8.30. Wiring diagram for Practical Investigation 8.1

voltage used while the logic levels associated with TTL devices tend to be absolute (see Fig.8.28).

The noise margin of a logic device is a measure of its ability to reject noise and spurious signals; the larger the noise margin the better is its ability to perform in an environment in which noise is present. Noise margin is defined as the difference between the minimum values of high state output and high state input voltage and the maximum values of low state output and low state input voltage. Hence:

$$\begin{aligned} \text{noise margin} &= V_{OH(MIN)} - V_{IH(MIN)} \\ \text{or} \\ \text{noise margin} &= V_{OL(MAX)} - V_{IL(MAX)} \end{aligned}$$

where $V_{OH(MIN)}$ is the minimum value of

high state (logic 1) output voltage, $V_{IH(MIN)}$ is the minimum value of high state (logic 1) input voltage, $V_{OL(MAX)}$ is the maximum value of low state (logic 0) output voltage, and $V_{IL(MAX)}$ is the minimum value of low state (logic 0) input voltage.

The noise margin for standard 7400 series TTL is typically 400mV while that for CMOS is $1/3V_{DD}$, as shown in Fig.8.28.

Practical Investigation 8.1

Objective: To investigate the operation and obtain the truth table for (a) a two-input CMOS NOR gate and (b) a two-input CMOS NAND gate.

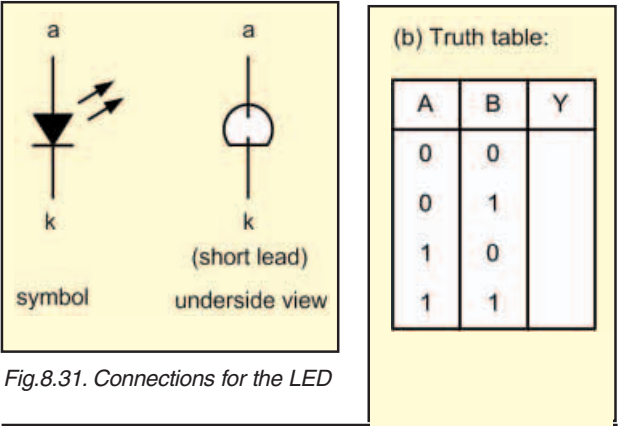


Fig.8.31. Connections for the LED

(a) Table of results:

Link A	Link B	LED D1
present	present	
present	removed	
removed	present	
removed	removed	

Link present = 0 LED non-illuminated = 0
Link removed = 1 LED illuminated = 1


Fig.8.32. Table of results for the two-input NOR gate investigation

Check Point 8.4

The two main logic families are CMOS and TTL. These two families have quite different characteristics, supply requirements, and logic levels. CMOS logic devices operate from a wide range of voltage levels and consume very little power (and are therefore often preferred for portable low-power applications). TTL logic devices, on the other hand, tend to be faster but have a much lower noise margin and are therefore more susceptible to noise and interference.

Table 8.1. Breadboard wiring for Practical Investigation 8.1

Step	Connection, link or component	From	To
1	9V supply (negative)	Supply negative	Black terminal
2	9V supply (+9V)	Supply positive	Red terminal
3	Red wire	Red terminal	+31
4	Black wire	Black terminal	-31
5	Link	-30 (top)	-30 (bottom)
6	Link	J23	-23 (bottom)
7	Link (Link A)	J12	-12 (bottom)
8	Link (Link B)	J13	-13 (bottom)
9	Link	+12	A12
10	Link	+13	A13
11	Link	+17	A17
12	Link	G12	G17
13	Link	H13	H18
14	IC1 4001	Pin 1	F17
15	IC1 (as above)	Pin 7	F23
16	IC1 (as above)	Pin 8	E23
17	IC1 (as above)	Pin 14	E17
18	R1 47kΩ	C12	F12
19	R2 47kΩ	C13	F13
20	R3 1kΩ	G19	G25
21	D1 LED	anode	J25
22	D1 (as above)	cathode	-25 (bottom)

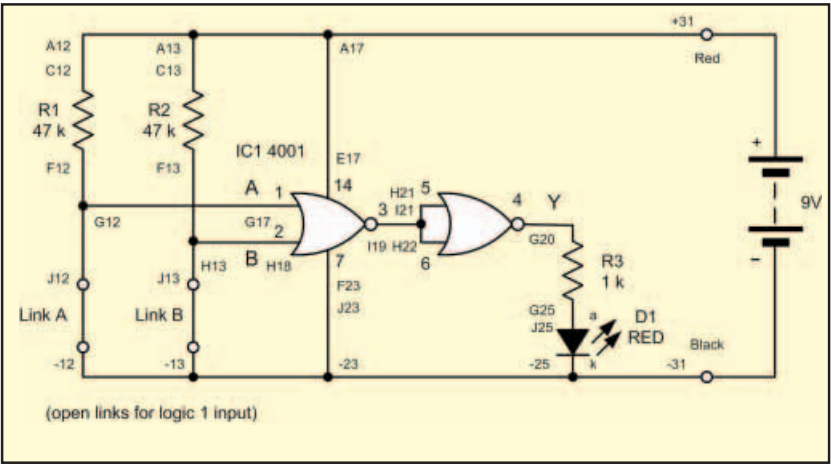

Ingenuity Unlimited



WIN A PICO PC-BASED OSCILLOSCOPE WORTH £586

- 5GS/s Dual Channel Storage Oscilloscope
- 50MHz Spectrum Analyser
- Multimeter
- Frequency Meter
- USB Interface.

If you have a novel circuit idea which would be of use to other readers then a

Pico Technology PC-based oscilloscope could be yours. Every 12 months, Pico Technology will be awarding a PicoScope 3205 digital storage oscilloscope for the best IU submission. In addition a DrDAQ Data Logger/Scope worth £59 will be presented to the runner up.

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're

looking for novel applications and circuit designs, not simply mechanical, electrical or software ideas. Ideas *must be the reader's own work* and **must not have been published or submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and include a full circuit diagram showing all component values. **Please draw all circuit schematics as clearly as possible**. Send your circuit ideas to: *Ingenuity Unlimited*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. (We **do not** accept submissions for IU via email). Your ideas could earn you some cash **and a prize!**

Super Vibration Switch – A Gentle Turn-on

THE circuit in Fig.1 represents a substantial increase in sensitivity compared to other designs. It is designed as a drop-in replacement for the traditional vibration switch. An indicator light D1 indicates that vibration has been detected, and it has three terminals, +12V, 0V, and OUT. OUT goes logic “high” when vibration is detected.

Circuit Details

The Super Vibration Switch uses a cheap, standard piezo element which flexes slightly in response to vibrations, thus creating a minute electrical output. At the heart of its “front end” (see Fig.1) is the veteran LM380N. This IC is chosen for its lightly biased inputs, its automatically centred output, and its internal positive feedback, which enormously amplifies the electrical output of piezo element X1. Not only this, but X1 is isolated from the rest of the circuit, so that supply decoupling is not a critical issue.

Potentiometer VR1 biases the trigger input of monostable IC2. Since a single component (VR1) is used here, there is no danger of drift from mismatched temperature coefficients. Capacitor C1 serves for DC blocking.

IC2 is wired as a standard monostable timer. With the values of R2 and C3 as shown, this delivers a positive-going output pulse of about one second, illuminating LED D1. The author chose an ultrabright LED for D1, since this was easier to see at a distance.

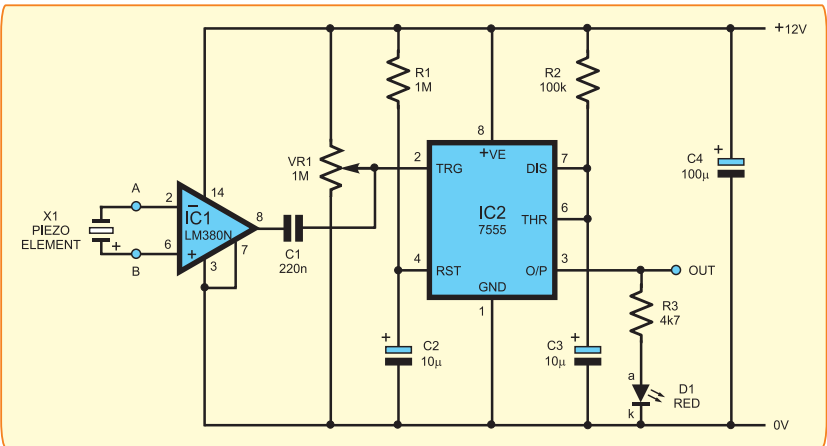


Fig. 1. Complete circuit diagram for the Super Vibration Switch

IC2 includes a timed delay of a few seconds at reset pin 4 (R1 and C2), to prevent any spurious triggering at switch-on.

Sensor Elements

To mount the sensor (see Fig.2), the author drilled a 3mm hole at one edge of the piezo element, near the base of its wires, and soldered a washer to the hole. He inserted a 20mm long, 3mm diameter bolt through the washer, and secured the piezo element as shown. This assembly was then fixed to the PCB, with the bolt serving as the negative terminal. The “suspended” end

of the piezo element ideally needs to be weighted, in such a way that most of the element will be free to flex.

The greater the weight, the better, since that increases inertia. However, since this is a flimsy(ish) piezo element, it has a natural limit. One could say a few grams.

The Super Vibration Switch draws about 13mA on standby. Therefore for long-term use it should use a regulated power supply. Attach a 12V battery or regulated power supply, and wait a few seconds for IC2 to reset.

If LED D1 illuminates all the time, then VR1 needs to be adjusted towards +12V. If

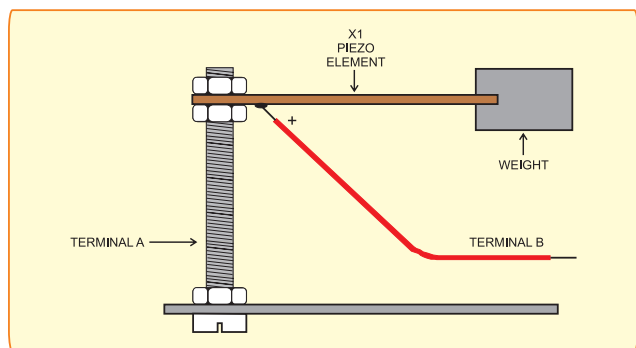


Fig.2. Mechanical setup for the vibration element

D1 does not illuminate at all, then VR1 needs to be adjusted towards 0V. The Super Vibration Switch is best placed on a surface which is most directly affected by the vibration you want to pick up.

If an ordinary encased piezo sounder is used in place of X1, the circuit may serve as a sensitive clap switch. Alternatively, a neodymium magnet may be used to weight the piezo element, in which case this would convert the circuit into a magnetic switch, responding to a moving magnet with a range of up to about 100mm.

Without any special effort, the switch may be adjusted very sensitively indeed. The author's prototype was capable of picking up a pin striking a wooden floor at a few metres' distance, and easily picked up the vibration of cars passing in the street.

Thomas Scarborough
Cape Town, South Africa.

Simple Sonar – Disco Tech

AS IF there were no end to what may be done with the LM380N amplifier IC, the circuit in Fig.3 shows a Simple Sonar employing just four components. The circuit description is equally simple.

Piezo sounder X1 serves as a microphone, while piezo X2 serves as a sounder. When X1 and X2 are brought into close proximity, a feedback loop is created, so that X2 sounds loudly at its resonant frequency. Ideally X1 and X2 will be identical; they are the usual cheap brass discs enclosed in plastic (without integral electronic driver circuits).

Resistor R1 is necessary to limit output current. Its value may be reduced to as little

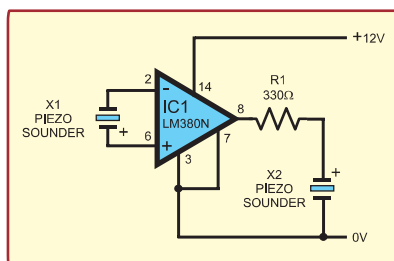


Fig.3. Full circuit diagram for the Simple Sonar

as a few tens of ohms if desired, to increase sensitivity by about a third. Without R1, the

circuit would work initially, but IC1 would soon go into thermal shutdown.

X1 and X2 may be mounted a few centimetres apart – just far enough not to create feedback. When an object (e.g. a car bumper) comes within about 10cm of X1 and X2, piezo sounder X2 screeches at its resonant frequency. Since the LM380N's current consumption is not the most modest (about 12mA in this application), this circuit would ideally be run off a 12V DC plugpack power supply.

Thomas Scarborough
Cape Town, South Africa

EPE IS PLEASED TO BE ABLE TO OFFER YOU THESE ELECTRONICS CD-ROMS

ELECTRONICS PROJECTS




Logic Probe testing

Electronic Projects is split into two main sections: **Building Electronic Projects** contains comprehensive information about the components, tools and techniques used in developing projects from initial concept through to final circuit board production. Extensive use is made of video presentations showing soldering and construction techniques. The second section contains a set of ten projects for students to build, ranging from simple sensor circuits through to power amplifiers. A shareware version of Matrix's CADPACK schematic capture, circuit simulation and p.c.b. design software is included.

The projects on the CD-ROM are: Logic Probe; Light, Heat and Moisture Sensor; NE555 Timer; Egg Timer; Dice Machine; Bike Alarm; Stereo Mixer; Power Amplifier; Sound Activated Switch; Reaction Tester. Full parts lists, schematics and p.c.b. layouts are included on the CD-ROM.


ELECTRONICS CAD PACK

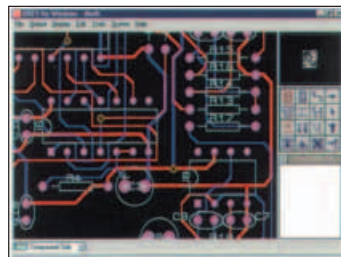

PCB Layout

Electronics CADPACK allows users to design complex circuit schematics, to view circuit animations using a unique SPICE-based simulation tool, and to design printed circuit boards. CADPACK is made up of three separate software modules. (These are restricted versions of the full Labcenter software.) **ISIS Lite** which provides full schematic drawing features including full control of drawing appearance, automatic wire routing, and over 6,000 parts. **PROSPICE Lite** (integrated into ISIS Lite) which uses unique animation to show the operation of any circuit with mouse-operated switches, pots, etc. The animation is compiled using a full mixed mode SPICE simulator. **ARES Lite** PCB layout software allows professional quality PCBs to be designed and includes advanced features such as 16-layer boards, SMT components, and an autorouter operating on user generated Net Lists.


ELECTRONIC CIRCUITS & COMPONENTS V2.0

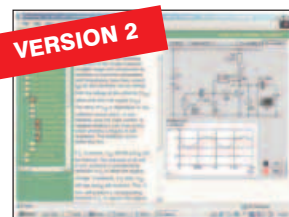

Circuit simulation screen

Provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding. Version 2 has been considerably expanded in almost every area following a review of major syllabuses (GCSE, GNVQ, A level and HNC). It also contains both European and American circuit symbols. Sections include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**. The **Parts Gallery** will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Included in the Institutional Versions are multiple choice questions, exam style questions, fault finding virtual laboratories and investigations/worksheets.

ANALOGUE ELECTRONICS

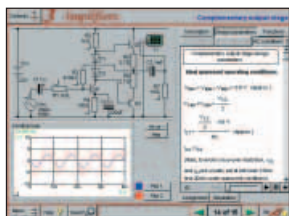


Complimentary output stage

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections), **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators. **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections), **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections), **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators. **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.


DIGITAL ELECTRONICS V2.0

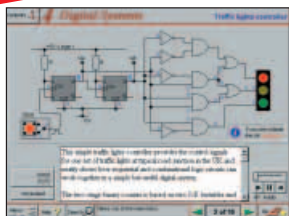

Virtual laboratory – Traffic Lights

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (opposite), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen. Covers binary and hexadecimal numbering systems, ASCII, basic logic gates, monostable action and circuits, and bistables – including JK and D-type flip-flops. Multiple gate circuits, equivalent logic functions and specialised logic functions. Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers. A/D and D/A converters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units. Sections on Boolean Logic and Venn diagrams, displays and chip types have been expanded in Version 2 and new sections include shift registers, digital fault finding, programmable logic controllers, and microcontrollers and microprocessors. The Institutional versions now also include several types of assessment for supervisors, including worksheets, multiple choice tests, fault finding exercises and examination questions.

ANALOGUE FILTERS

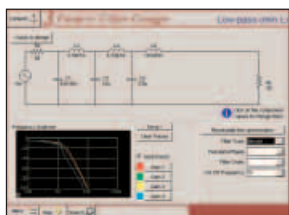

Filter synthesis

Analogue Filters is a complete course in designing active and passive filters that makes use of highly interactive virtual laboratories and simulations to explain how filters are designed. It is split into five chapters: **Revision** which provides underpinning knowledge required for those who need to design filters. **Filter Basics** which is a course in terminology and filter characterization, important classes of filter, filter order, filter impedance and impedance matching, and effects of different filter types. **Advanced Theory** which covers the use of filter tables, mathematics behind filter design, and an explanation of the design of active filters. **Passive Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev ladder filters. **Active Filter Design** which includes an expert system and filter synthesis tool for the design of low-pass, high-pass, band-pass, and band-stop Bessel, Butterworth and Chebyshev

ROBOTICS & MECHATRONICS



Case study of the Milford Instruments Spider

Robotics and Mechatronics is designed to enable hobbyists/students with little previous experience of electronics to design and build electromechanical systems. The CD-ROM deals with all aspects of robotics from the control systems used, the transducers available, motors/actuators and the circuits to drive them. Case study material (including the NASA Mars Rover, the Milford Spider and the Furby) is used to show how practical robotic systems are designed. The result is a highly stimulating resource that will make learning, and building robotics and mechatronic systems easier. The Institutional versions have additional worksheets and multiple choice questions.

- Interactive Virtual Laboratories
- Little previous knowledge required
- Mathematics is kept to a minimum and all calculations are explained
- Clear circuit simulations

PRICES

Prices for each of the CD-ROMs above are:

(Order form on third page)

Hobbyist/Student	£45 inc VAT
Institutional (Schools/HE/FE/Industry)	£99 plus VAT
Institutional 10 user (Network Licence)	£249 plus VAT
Site Licence	£499 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

PICmicro TUTORIALS AND PROGRAMMING


HARDWARE

VERSION 3 PICmicro MCU DEVELOPMENT BOARD

Suitable for use with the three software packages listed below.

This flexible development board allows students to learn both how to program PICmicro microcontrollers as well as program a range of 8, 18, 28 and 40-pin devices from the 12, 16 and 18 series PICmicro ranges. For experienced programmers all programming software is included in the PPP utility that comes with the development board. For those who want to learn, choose one or all of the packages below to use with the Development Board.

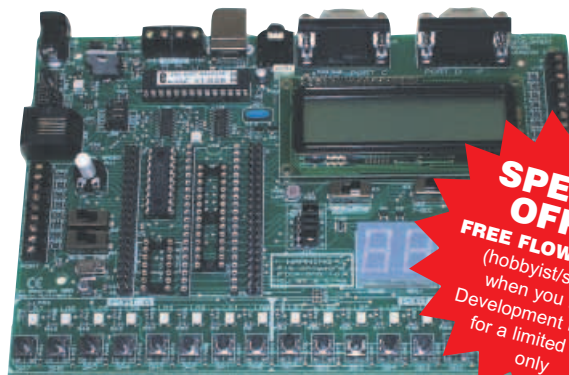- Makes it easier to develop PICmicro projects
- Supports low cost Flash-programmable PICmicro devices
- Fully featured integrated displays – 16 individual I.e.d.s, quad 7-segment display and alphanumeric I.c.d. display
- Supports PICmicro microcontrollers with A/D converters
- Fully protected expansion bus for project work
- USB programmable
- Can be powered by USB (no power supply required)



SPECIAL OFFER
FREE FLOWCODE V2
(hobbyist/student)
when you buy a
Development Board –
for a limited time
only

£158 including VAT and postage

**supplied with USB cable and
programming software**


SOFTWARE

Suitable for use with the Development Board shown above.

ASSEMBLY FOR PICmicro V3 (Formerly PICtutor)

Assembly for PICmicro microcontrollers V3.0 (previously known as PICtutor) by John Becker contains a complete course in programming the PIC16F84 PICmicro microcontroller from Arizona Microchip. It starts with fundamental concepts and extends up to complex programs including watchdog timers, interrupts and sleep modes. The CD makes use of the latest simulation techniques which provide a superb tool for learning: the Virtual PICmicro microcontroller. This is a simulation tool that allows users to write and execute MPASM assembler code for the PIC16F84 microcontroller on-screen. Using this you can actually see what happens inside the PICmicro MCU as each instruction is executed which enhances understanding.

- Comprehensive instruction through 45 tutorial sections
- Includes Vlab, a Virtual PICmicro microcontroller: a fully functioning simulator
- Tests, exercises and projects covering a wide range of PICmicro MCU applications
- Includes MPLAB assembler
- Visual representation of a PICmicro showing architecture and functions
- Expert system for code entry helps first time users
- Shows data flow and fetch execute cycle and has challenges (washing machine, lift, crossroads etc.)
- Imports MPASM files.

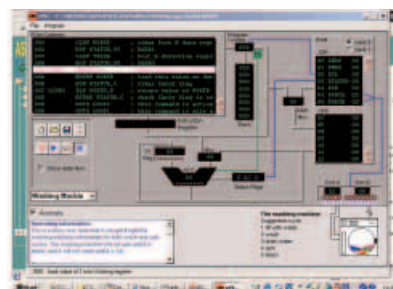

'C' FOR PICmicro VERSION 2

The C for PICmicro microcontrollers CD-ROM is designed for students and professionals who need to learn how to program embedded microcontrollers in C. The CD contains a course as well as all the software tools needed to create Hex code for a wide range of PICmicro devices – including a full C compiler for a wide range of PICmicro devices.

Although the course focuses on the use of the PICmicro microcontrollers, this CD-ROM will provide a good grounding in C programming for any microcontroller.

- Complete course in C as well as C programming for PICmicro microcontrollers
- Highly interactive course
- Virtual C PICmicro improves understanding
- Includes a C compiler for a wide range of PICmicro devices
- Includes full Integrated Development Environment
- Includes MPLAB software
- Compatible with most PICmicro programmers
- Includes a compiler for all the PICmicro devices.



Minimum system requirements for these items: Pentium PC running Windows 98, NT, 2000, ME, XP; CD-ROM drive; 64MB RAM; 10MB hard disk space.


FLOWCODE FOR PICmicro V2

Flowcode is a very high level language programming system for PICmicro microcontrollers based on flowcharts. Flowcode allows you to design and simulate complex robotics and control systems in a matter of minutes.

Flowcode is a powerful language that uses macros to facilitate the control of complex devices like 7-segment displays, motor controllers and I.c.d. displays. The use of macros allows you to control these electronic devices without getting bogged down in understanding the programming involved.

Flowcode produces MPASM code which is compatible with virtually all PICmicro programmers. When used in conjunction with the Version 2 development board this provides a seamless solution that allows you to program chips in minutes.

- Requires no programming experience
- Allows complex PICmicro applications to be designed quickly
- Uses international standard flow chart symbols (ISO5807)
- Full on-screen simulation allows debugging and speeds up the development process
- Facilitates learning via a full suite of demonstration tutorials
- Produces ASM code for a range of 18, 28 and 40-pin devices
- Professional versions include virtual systems (burglar alarm, buggy and maze, plus RS232, IrDa etc.).

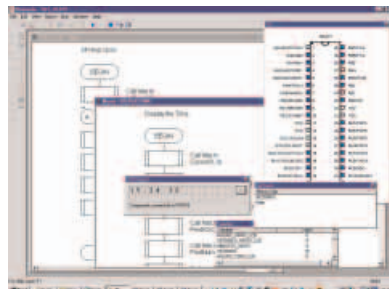

PRICES

Prices for each of the CD-ROMs above are:

(Order form on next page)

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

Hobbyist/Student
Flowcode V2 Hobbyist/Student
Institutional (Schools/HE/FE/Industry)
Flowcode Professional
Institutional/Professional 10 user (Network Licence)
Site Licence


£45 inc VAT
£57 inc VAT
£99 plus VAT
£99 plus VAT
£300 plus VAT
£599 plus VAT

TEACH-IN 2000 – LEARN ELECTRONICS WITH EPE

EPE's own *Teach-In* CD-ROM, contains the full 12-part *Teach-In 2000* series by John Becker in PDF form plus the *Teach-In* interactive software (Win 95, 98, ME and above) covering all aspects of the series. We have also added Alan Winstanley's highly acclaimed *Basic Soldering Guide* which is fully illustrated and which also includes *Desoldering*. The *Teach-In* series covers: Colour Codes and Resistors, Capacitors, Potentiometers, Sensor Resistors, Ohm's Law, Diodes and L.E.D.s, Waveforms, Frequency and Time, Logic Gates, Binary and Hex Logic, Op.amps, Comparators, Mixers, Audio and Sensor Amplifiers, Transistors, Transformers and Rectifiers, Voltage Regulation, Integration, Differentiation, 7-segment Displays, L.C.D.s, Digital-to-Analogue. Each part has an associated practical section and the series includes a simple PC interface (Win 95, 98, ME ONLY) so you can use your PC as a basic oscilloscope with the various circuits.


A hands-on approach to electronics with numerous breadboard circuits to try out.
£12.45 including VAT and postage. Requires Adobe Acrobat (available free from the Internet – www.adobe.com/acrobat).

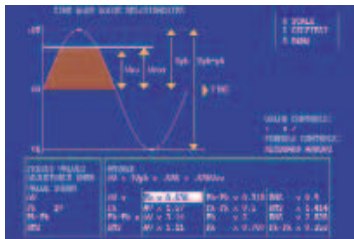FREE WITH EACH TEACH-IN CD-ROM – *Understanding Active Components* booklet, *Identifying Electronic Components* booklet and *The Best Of Circuit Surgery* CDROM.




Sine wave relationship values

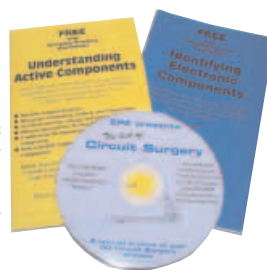FREE TWO BOOKLETS PLUS CD-ROM WITH TEACH-IN 2000



DIGITAL WORKS 3.0

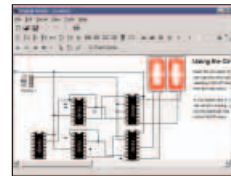

Counter project

Digital Works Version 3.0 is a graphical design tool that enables you to construct digital logic circuits and analyze their behaviour. It is so simple to use that it will take you less than 10 minutes to make your first digital design. It is so powerful that you will never outgrow its capability. ● Software for simulating digital logic circuits ● Create your own macros – highly scalable ● Create your own circuits, components, and i.c.s ● Easy-to-use digital interface ● Animation brings circuits to life ● Vast library of logic macros and 74 series i.c.s with data sheets ● Powerful tool for designing and learning. **Hobbyist/Student £45 inc. VAT. Institutional £99 plus VAT. Institutional 10 user £249 plus VAT. Site Licence £599 plus VAT.**

NEW

PROJECT DESIGN WITH CROCODILE TECHNOLOGY

An Interactive Guide to Circuit Design

An interactive CD-ROM to guide you through the process of circuit design. Choose from an extensive range of input, process and output modules, including CMOS Logic, Op-Amps, PIC/PICAXE, Remote Control Modules (IR and Radio), Transistors, Thyristors, Relays and much more. Click Data for a complete guide to the pin layouts of i.c.s, transistors etc. Click More Information for detailed background information with many animated diagrams. Nearly all the circuits can be instantly simulated in Crocodile Technology* (not included on the CD-ROM) and you can customise the designs as required.

WHAT'S INCLUDED

Light Modules, Temperature Modules, Sound Modules, Moisture Modules, Switch Modules, Astables including 555, Remote Control (IR & Radio), Transistor Amplifiers, Thyristor, Relay, Op-Amp Modules, Logic Modules, 555 Timer, PIC/PICAXE, Output Devices, Transistor Drivers, Relay Motor Direction & Speed Control, 7 Segment Displays. Data sections with pinouts etc., Example Projects, Full Search Facility, Further Background Information and Animated Diagrams.


Runs in Microsoft Internet Explorer

*All circuits can be viewed, but can only be simulated if your computer has Crocodile Technology version 410 or later. A free trial version of Crocodile Technology can be downloaded from: www.crocodile-clips.com. Animated diagrams run without Crocodile Technology.

Single User £39.00 inc. VAT.

Multiple Educational Users (under 500 students) £59.00 plus VAT. Over 500 students £79.00 plus VAT.

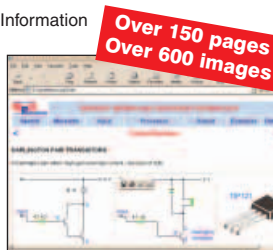(UK and EU customers add VAT at 17.5% to "plus VAT" prices)



ELECTRONIC COMPONENTS PHOTOS

A high quality selection of over 200 JPG images of electronic components. This selection of high resolution photos can be used to enhance projects and presentations or to help with training and educational material. They are royalty free for use in commercial or personal printed projects, and can also be used royalty free in books, catalogues, magazine articles as well as worldwide web pages (subject to restrictions – see licence for full details). Also contains a **FREE** 30-day evaluation of Paint Shop Pro 6 – Paint Shop Pro image editing tips and on-line help included!

Price £19.95 inc. VAT



Minimum system requirements for these CD-ROMs: Pentium PC, CD-ROM drive, 32MB RAM, 10MB hard disk space. Windows 95/98/NT/2000/ME/XP, mouse, sound card, web browser.

Please send me: CD-ROM ORDER FORM

- ☐ Electronic Projects
- ☐ Electronic Circuits & Components V2.0
- ☐ Analogue Electronics
- ☐ Digital Electronics V2.0
- ☐ Analogue Filters
- ☐ Electronics CAD Pack
- ☐ Robotics & Mechatronics
- ☐ Assembly for PICmicro V3
- ☐ 'C' for PICmicro V2
- ☐ Flowcode V2 for PICmicro
- ☐ Digital Works 3.0

Version required:

- ☐ Hobbyist/Student
- ☐ Institutional
- ☐ Institutional/Professional 10 user
- ☐ Site licence



- ☐ PICmicro Development Board V3 (hardware)

- ☐ Teach-In 2000 + FREE BOOK
- ☐ Electronic Components Photos
- ☐ Project Design – Single User
- ☐ Project Design – Multiple User (under 500 students)
- ☐ Project Design – Multiple User (over 500 students)

Note: The software on each version is the same, only the licence for use varies.

Full name:

Address:

Post code: Tel. No:

Signature:

☐ I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch: £

Valid From: Card expiry date:

Card No: Switch Issue No:

Card Security Code (The last 3 digits on or just under the signature strip)

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world
EU residents outside the UK add £5 for airmail postage per order

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU (European Union) country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:
Direct Book Service
Wimborne Publishing Ltd
408 Wimborne Road East
Ferndown, Dorset BH22 9ND

To order by phone ring

01202 873872. Fax: 01202 874562

Goods are normally sent within seven days

E-mail: orders@wimborne.co.uk

Online shop:

www.epemag.wimborne.co.uk/shopdoor.htm

PHONE RING & TEST



UK, US and European ring tones plus a basic test

By TERRY DE VAUX-BALBIRNIE

THIS circuit will ring a telephone in the UK, US or European style and also perform a basic check on the speech circuit. Of course, some people will wish to construct it for only one of these purposes.

One application would be to ring a phone for a stage production. The effect would be convincing to the audience (not usually the case when a person offstage using a bell push, battery and buzzer tries to imitate the UK style ring!).

The circuit will operate either a modern electronic phone or a traditional one having a mechanical sounder. It could therefore be useful for period productions. Note, however, that any traditional phone would need to be fitted with a modern BT type plug and converted as necessary.

Tape recorded telephone rings are sometimes used for plays but these are never altogether satisfactory. One reason is that it is usually obvious to the audience that the sound is not coming from the phone. A further point is that the operator off-stage needs to stop the tape machine as soon as the person lifts the receiver and this requires

some care. With this device, the ringing stops as the handset is lifted.

Being self-contained and battery operated, the unit may be taken to a car boot sale to check phones offered for sale. Bargains

are to be had but there is also a lot of rubbish on offer.

Appearance

The circuit is built in a plastic box (see photograph). On the side, there are four switches labelled ON, RING/SHOW, TEST and UK/US/EUR. The latter is a rotary unit which selects the ring style. There is also a neon indicator and a control which varies the ring signal frequency. This is not normally

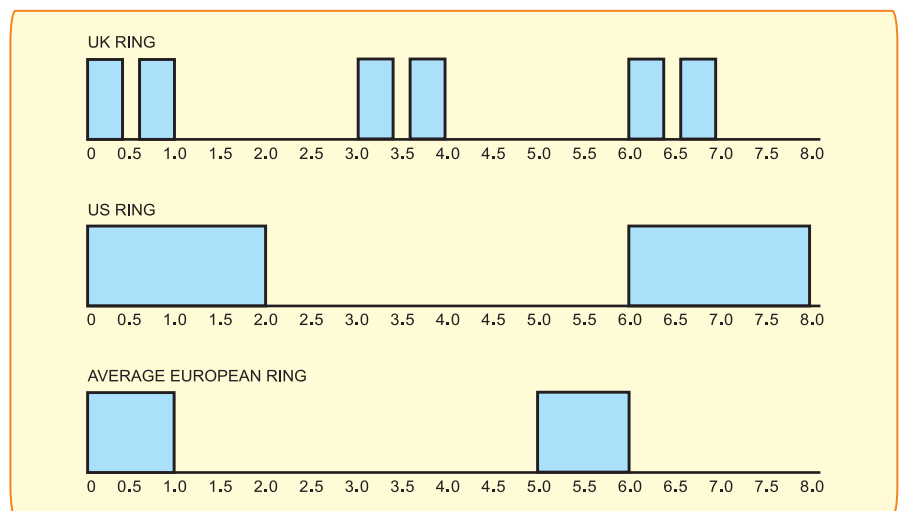


Fig.1: Cadence of UK, USA and average European ring styles

used for modern telephones but may need to be adjusted when using old units having a mechanical bell system. On top of the box there is a UK-style telephone socket.

The RING/SHOW switch may be used to start the ringing cycle at the right time. This is useful for stage performances. For example, for the UK tone, it is best for the phone to “switch on” just before the double ring. With the switch set to SHOW, the neon indicator will flash in sympathy with the ring signal. The user then switches to RING at the chosen moment. The TEST pushbutton switch allows the user to listen to his or her own voice through the earpiece. More will be said about this later.

Dead Ringer

A double ring cadence (ring-ring ring-ring) is used in the UK, Australia, the Irish Republic and several other countries. This generally follows the pattern 0.4s on, 0.2s off, 0.4s on, 2s off then repeat. One cycle therefore occupies three seconds. Other countries usually use some form of single ring (although a continuous tone is occasionally found).

The North American model follows the pattern two seconds on, four seconds off then repeat – the cycle taking six seconds. In continental Europe, the ring tone is generally on for one second and off for three or four seconds. In France, it is on for 1.5 seconds and off for 3.5 seconds. Due to the wide variation in detail of European ring tones, this circuit is set to give an average effect of one second on and four seconds off as used, for example, in Germany, Italy and the Netherlands. Fig.1 shows the UK, US and “average European” cadence.

It is said that television viewers in the United States are familiar with the UK-style double ring tone because it is often heard in programmes broadcast there. This leads many people to think that it is the pattern used throughout Europe. Nothing could be further from the truth!

However, knowing that this misconception exists, the UK ring tone is often used by American producers for a programme set in any European country and this perpetuates the myth. On the other hand, those living in the UK are familiar with the single ring pattern heard when on holiday in the USA or on the continent, but many do not know that variations exist between the various countries.

Facts and Figures

Whatever the pattern, the ringing signal comprises bursts of alternating current (in Europe the frequency is usually 25Hz while in the US it is 20Hz). The signal is then sent

along the telephone line at some 70 volts. The value varies from country to country (it may be as high as 150V) and falls with increasing load (the number of telephones connected to the line). Using a high-voltage

system reduces the voltage drop across the resistance of a long telephone line.

The operating frequency is not critical when using an electronic phone. However, old units having a mechanical ringer need a



Parts List – Phone Ring & Test

1 PC board coded 574, available from the *EPE PCB Service*

1 plastic case, size 150 × 100 × 60mm

1 small form UK secondary telephone socket (65mm square – see text)

1 3VA 230V min. mains transformer, 12V-0V-12V secondary

1 wire-ended neon indicator (no series resistor) – see text

1 8-pin d.i.l. socket

1 14-pin d.i.l. socket

1 16-pin d.i.l. socket

1 9V battery pack, with holder

2 plastic control knobs

multistrand connecting wire; single link wire; small fixings; solder etc.

Switches

1 4-way d.i.l. switch (see text)

1 3-pole 4-way rotary switch (see text)

1 min. pushbutton switch, push-to-make

1 s.p.s.t. toggle switch, 2A

1 s.p.s.t. toggle switch 1A 230V a.c.

Semiconductors

11 1N4148 signal diodes

1 1N4001 rectifier diode

1 1N5817 Schottky diode

1 2N3702 *pnp* transistor

1 2N3704 *nnp* transistor

2 BUZ11A *n*-channel power MOSFET or similar

1 555 timer i.c.

1 556 dual timer i.c.

2 4017 decade counter i.c.

Capacitors

1 470 μ radial elect. 16V

6 10n metallised polyester

5 100n metallised polyester

Resistors (0.25W, 5% except where indicated)

3 5k6 1 470k

3 47k 1 680k

1 100k 1 1M

1 150k 5 2M2k Ω

1 10k 0.6W metal film

Potentiometers

1 470k min. rotary carbon, lin.

1 2M2 round carbon preset, vert.

1 4M7 round carbon preset, vert.

1 10M round carbon preset, vert.

signal of the frequency it was designed for. This type of sounder comprises a pivoted arm which moves a clapper between a pair of bells. In the UK it appears that these are tuned to a musical interval of a fifth to produce the familiar chord.

For the arm to vibrate most efficiently so that the bells are struck as hard as possible and so give the loudest sound, the signal must be set to the natural frequency of vibration of the system – that is, it should resonate. To achieve this, the frequency adjustment control may be used to tune the circuit for best results. In fact, tests using the prototype unit showed that the frequency is not too critical.

Circuit Description

The complete circuit diagram for the Phone Ring & Test circuit is shown in Fig.2.

Assume for the moment, that rotary selector switch S4 is set to “UK”. Current flows from the 9V battery through On-Off switch S5 and diode D13. The diode provides reverse-polarity protection. Thus, if the supply were to be connected the wrong way round, it would be reverse-biased and nothing would happen. Capacitor C12 provides a reserve of charge and prevents excessive “dipping” of the supply voltage on high-current peaks.

Look at IC1a which is one section of a dual timer integrated circuit, type 556. This is configured as an astable (pulse generator) which provides a continuous train of pulses at its output (pin 5). The other section, IC1b, is also used as an astable and is associated with the single ring style phones. This will be looked at presently.

The astable frequency is determined by the values of resistors R1, R3 and R4, preset potentiometers VR1 and VR3 and capacitor C1. Ignore resistor R3 and VR3 for the moment – these are usually short-circuited by the normally on state of transistor TR1 and therefore have no effect. The reason for including them will be explained presently. Preset VR1 is used to adjust the frequency to 5Hz (five pulses per-second) at the end of construction. Capacitor C5 is for decoupling and C3 is the bypass capacitor needed for the bipolar timer.

Clock Watching

The next section is based on IC2, a decade counter. Pulses from IC1a output pin 5 are applied to its clock input, pin 14, via capacitor C6. Resistor R9 keeps IC2 clock input low between pulses and resistor R6 (in conjunction with R9) provides a discharge path for C6. On the arrival of successive pulses, each of IC2's ten outputs 0 to 9 go high in turn for 0.2 seconds, then the process repeats.

WARNING

The voltage of the ringing signal is high enough to deliver a painful and potentially dangerous shock – take extreme care when testing or while making any adjustments to the unit

IC2 output Q0 is initially high so, on the arrival of the first and second pulses, output Q1 then output Q2 go high taking 0.4 seconds altogether. There is then an off period of 0.2 seconds while unconnected output Q3 goes high. This is followed by outputs Q4 and Q5 going high, again, taking 0.4 seconds. Each high state proceeds to the “UK” contact of selector switch S4a, via one of the group of diodes D4 to D7.

Although this provides a basic UK-type ring signal, the repeat time is too short. To produce the correct delay, we need an off period of two seconds. As the circuit stands, it would give a delay of only one second (the time taken for unused outputs Q6, Q3 and Q0 to go high). To increase it, the astable is temporarily slowed down. This is done by turning transistor TR1 off for part of the cycle so that fixed resistor R3 and preset VR3 become active.

Since TR1 is a *pnp* device, it will be switched off when its base (b) is made high. However, it is kept normally on by making the base low via resistor R8. Assuming switch S1 is on, IC2 output Q7 is connected through diode D1 to TR1's base so that when this output goes high, TR1 switches off and the astable rate is reduced.

Diodes D2 and D3 are associated with IC2 outputs Q8 and Q9 and may be “switched in” by closing S2, or S2 and S3, as necessary. This, together with some adjustment to preset VR3 will provide the correct timing. With switches S1 to S3 all off, the circuit functions without additional delay and this will aid setting-up at the end.

Making the Switch

The signal at the pole of switch S4a is applied to IC4's reset input, pin 4. IC4 is a further timer i.e. configured as an astable. With its reset pin high, it is enabled and output pin 3 provides bursts of pulses at a nominal frequency of 20Hz in sympathy with the ring pattern.

The frequency is determined by the values of fixed resistors R12 and R13, potentiometer VR4, and capacitor C9. Fixed resistor R14 maintains IC4's reset input normally low and prevents false operation. Capacitor C10 is for decoupling and C11 is the bypass capacitor.

Although the signal at IC4 pin 3 now has the correct form, it is only at the nominal

supply voltage of 9V so must be increased before it will ring a telephone.

Inversion

For this, the signal splits into two paths. One is via resistor R15 to the base of *npn* transistor TR2. An inverted signal therefore appears at its collector. Thus, when the base is high, the collector (c) will be low and vice versa. At the same time, a signal is obtained direct from IC4 pin 3. The two signals are applied to the gates of MOSFETs TR3 and TR4 respectively.

The MOSFETs therefore switch on in turn as each gate (g) goes high. Current flows from supply positive through either the top or bottom section of transformer T1's “primary” winding, returning to 0V via the conducting MOSFET.

Transformer T1 is a mains step-down unit used in reverse – that is, the winding intended to be the primary is used as the secondary and vice versa. Instead of reducing the voltage, it therefore increases it. Note that the labelling of the primary and secondary windings in Fig.2 refers to the way it would be used conventionally.

In this circuit, the waveform is not sinusoidal and the frequency is lower than mains frequency so the value of the final voltage is not easy to predict. However, measurement shows that it is some 100 volts peak on load using a 9V supply. This will vary between different transformers and will fall as the battery ages, but its value is not particularly critical.

Using the transformer in this way is inefficient and quite a high current is drawn from the supply – approximately 1A peak, although the average value is only about 500mA. This fairly high current drain is unimportant because the unit will not be used for long periods. The circuit will operate satisfactorily until the battery voltage falls to about 6V.

Back E.M.F.

The circuit generates a high voltage “spike” in the opposite direction to that of the supply (back e.m.f.) each time current flowing through a transformer primary half-winding is interrupted. This could destroy semiconductor devices if they were not protected. This is the purpose of Schottky diode D12 connected directly between the power supply rails.

As far as the supply is concerned it does nothing because it is reverse biased. However, to any reverse “spikes”, it will be forward biased and the energy will be shunted through the diode. Note that the MOSFETs are not protected in this way but these will withstand the voltage spikes.

PHONE RING & TEST

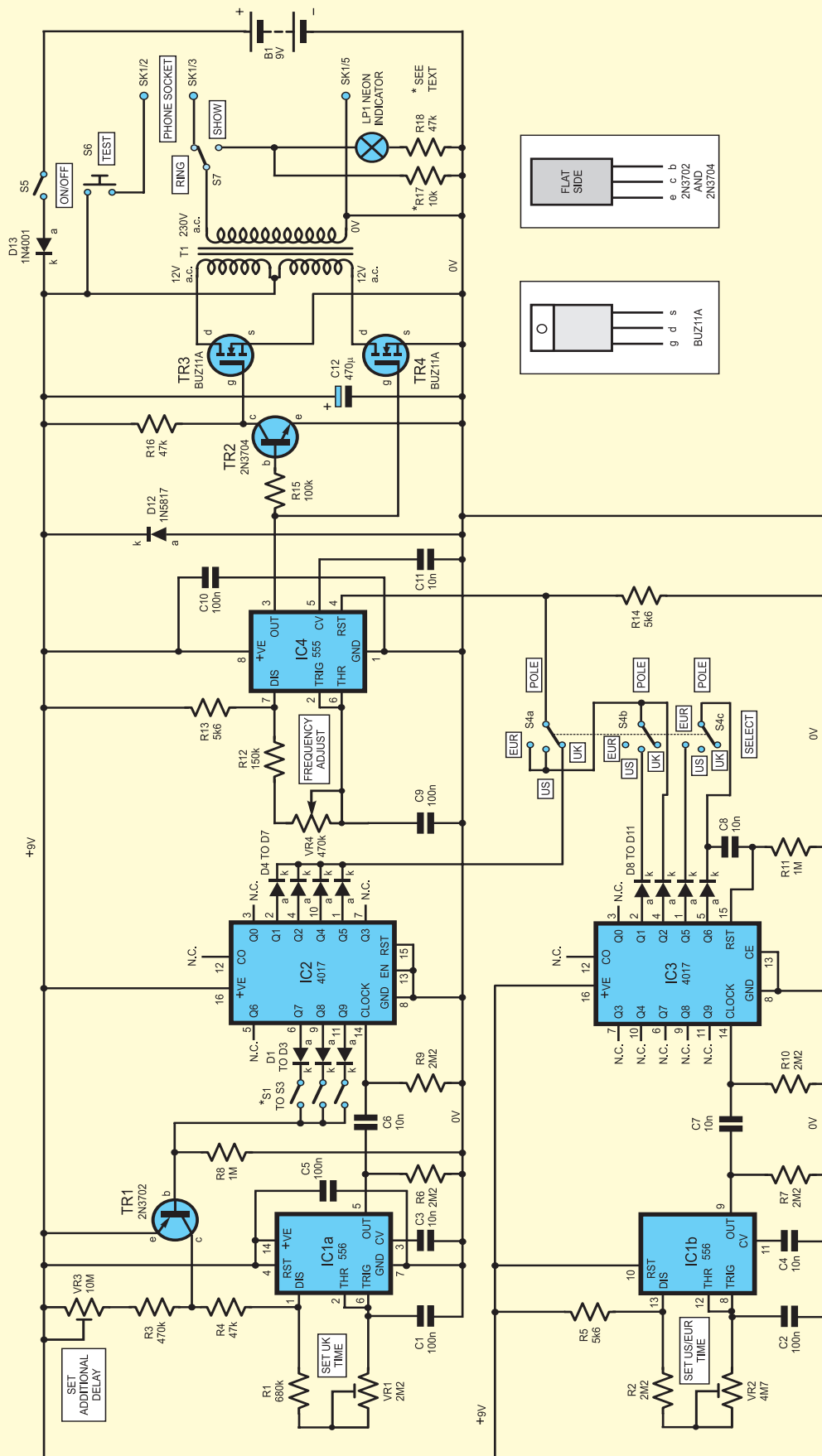


Fig.2. Complete circuit diagram for the Phone Ring & Test. Note the mains transformer T1 is used here in a "step-up" formation, i.e. instead of reducing the output voltage it increases it

Neon indicator LP1 operates through RING/SHOW switch S7 (when set to SHOW) and resistor R18. This allows the “rings” to be monitored silently. Neon gas requires some 65 volts to conduct and resistor R18 “drops” the excess voltage and limits the current.

Operation might be unstable if the transformer output were not supplying current during the whole of a “ring”. Normally, no current would be drawn until the neon “struck”. Such problems are avoided by connecting resistor R17 between switch S7’s SHOW contact and 0V. With switch S7 set to RING, the signal is applied to terminals 3 and 5 (ringer input) of the telephone socket, SK1.

Time Difference

Now let us look at the US ring pattern (switch S4 set to “US”). The astable centred on IC1b is now used together with decade counter IC3. Resistors R2 and R5, in conjunction with preset VR2 and capacitor C2, determine the operating frequency. Preset VR2 will be set to provide one pulse per second at the end of construction.

The pulses are transferred from IC1b output pin 9 to IC3 clock input pin 14, via capacitor C7 which operates in conjunction with fixed resistors R7 and R10 in the same way as for the UK section. Each of IC3’s outputs therefore go high in turn for one second.

Since output Q0 is initially high, on the arrival of the first and second pulses, outputs Q1 and Q2 will go high, taking two seconds altogether. Switch S4b allows the signal from outputs Q1 and Q2 (via diodes D8 and D9) to proceed to switch S4a’s pole, so a two-second high pulse appears at IC4’s reset input (pin 4).

There follows a three second “off” period while IC3 unused outputs Q3 to Q5 go high. When output Q6 does so, a pulse is applied to IC3’s reset input via diode D11 and capacitor C8 and this returns the counter to output Q0. Resistor R11 keeps the reset pin normally low and prevents false operation.

It takes a further one second for output Q1 to go high then the cycle repeats. The total “off” period is therefore four seconds. IC4 output pin 3 provides the US ring timing and its voltage is boosted by transformer T1 in the same way as for the UK signal.

To produce the European ring tone, switch S4 is set to “EUR”. Selector switch S4b removes diode D8 from the circuit, so instead of a two-second “on” state, this is reduced to one second. Also, switch S4c provides a reset pulse from IC3 output Q5, via diode D10, to maintain the correct “off” time of four seconds.

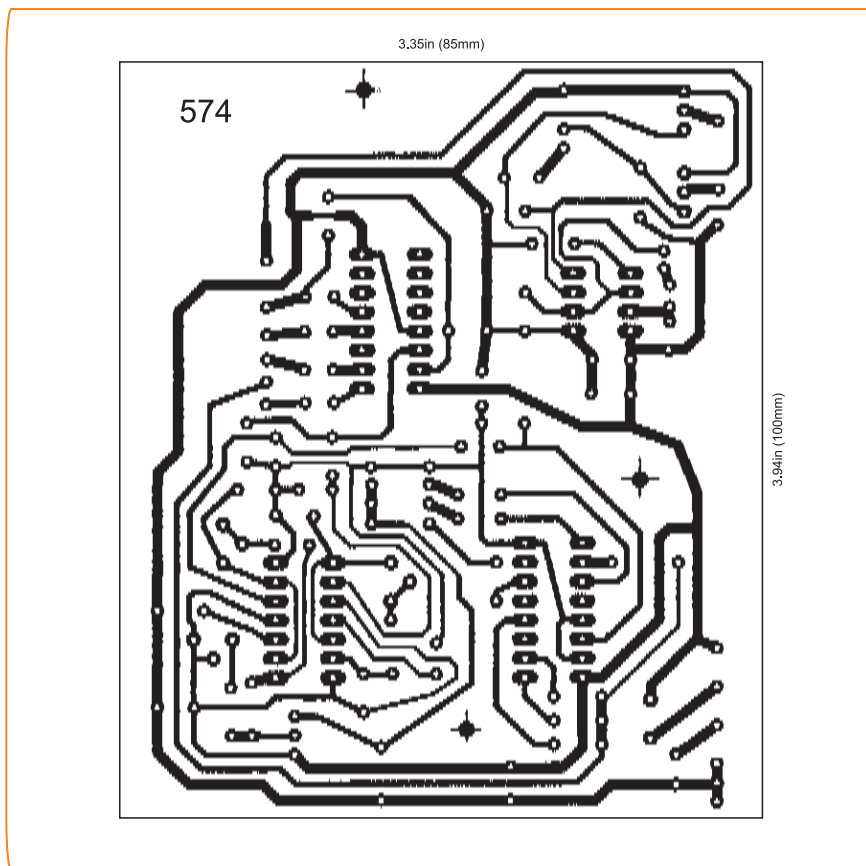


Fig.3: Full-size underside copper track master for the Phone Ring & Test board

Check It Out

Pushbutton TEST switch S6 connects the 9V supply between terminals 2 and 5 of the telephone socket. This allows the phone to operate in “talk” mode. However, since there is only one telephone involved, you will have to be content with talking to yourself!

Perhaps you have never noticed when making a call that you hear your own voice in the earpiece as well as that of the person at the other end (this is called the side-tone). Its absence is interpreted by the user as a “dead” phone. It also helps the user regulate his or her speaking volume (although in many cases it doesn’t help!).

Construction

The component and track layout details for the printed circuit board for the Phone Ring & Test circuit are shown in Fig.3 and Fig. 4. This board is available from the *EPE PCB Service*, code 574.

Solder the i.c. sockets and link wire in place. Solder the four d.i.l. (dual-in-line) switches (only three are actually used but it seems that 3-way units are not readily available). Follow with all resistors, presets VR1 to VR3, and capacitors. Note that resistor R17 is situated off-board. Take care to observe the polarity of electrolytic capacitor C12.

Solder the diodes and transistors TR1 and TR2 in place, taking care over their orientation. Note that the flat face of TR1 is to the left while that of TR2 is to the right. Solder pieces of light-duty stranded connecting wire to all the points indicated – using different colours will help to avoid errors later.

To prevent possible damage to the MOSFETs, remove any static charge from the body by touching something which is earthed before handling them. Solder the MOSFETs in place ensuring that their metal tabs *do not* touch.


Perform a thorough check of the assembly so far and check that when the power is applied, +9V (battery voltage) appears at the IC holder pins as shown in Fig.2.

Insert IC2 and IC3 into their sockets, again observing the same anti-static precautions. Insert IC1 and IC4. Do not use the CMOS equivalents (7556/7555) – the specified bipolar units are more robust for the purpose. Adjust the presets to approximately mid-track position.

Boxing Up

Drill holes in the box for p.c.b. and transformer mounting, and also for a bracket to secure the batteries. Drill holes

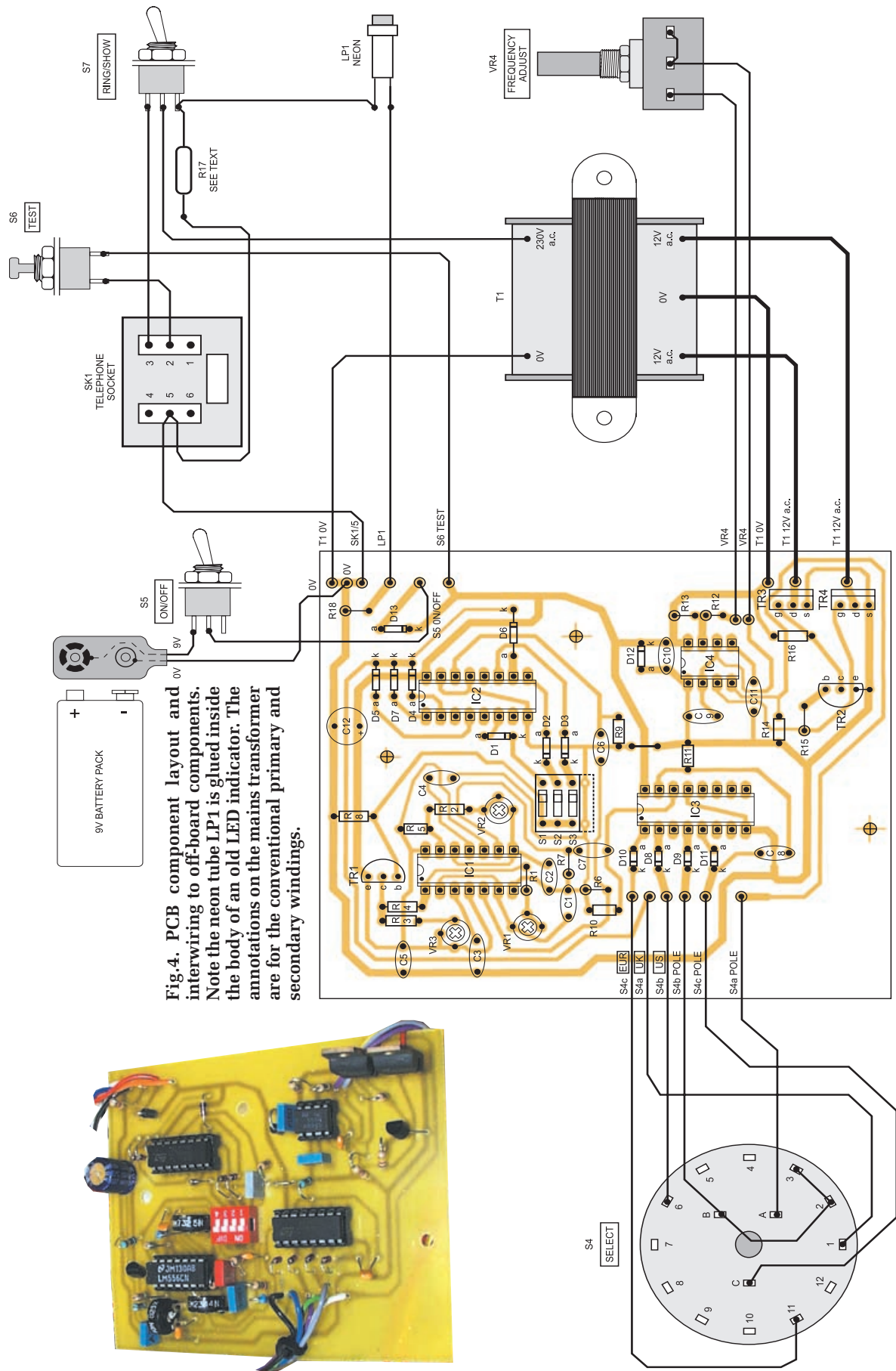PHONE RING & TEST CIRCUIT BOARD AND WIRING



for the switches and for the neon indicator (the author used the body of an old l.e.d. indicator with the neon tube glued inside).

Cut a “window” in the lid for the telephone socket terminals and attach the socket (see photograph). It will be easier to use the type having screw terminals rather than IDC connectors which need a special tool to fit the wires. Readers in other countries will need to obtain the correct type of socket and wire it up in the appropriate way. Remove the securing nut and tab washer from the bush of rotary switch S4. Adjust the position of the tab so that the switch is “stopped” with only three positions.

Attach the p.c.b. on short spacers and fit all remaining parts. Refer to Fig.4 and complete the interwiring. Resistor R17 is hard-wired between the SHOW tag of switch S7 and 0V (pin 5 of the telephone socket). The diagram shows the conventional numbering of S4’s tags. Apply strain relief to the telephone socket wires so that they cannot pull free when the lid is removed.

The transformer used in the prototype unit had integral leads. If the unit used has solder tags, those used for the ringer *must* be insulated so that they cannot be touched when the lid is removed. If the transformer has twin 120V primary windings, connect them in series. If there are two separate 12V windings, connect them in series with the common (c) connection taken to the mid-point.


Testing

Important note: the voltage of the ringing signal is high enough to deliver a painful and potentially dangerous shock – take care while adjusting!

The circuit is best set up by observing the neon indicator (switch S7 set to SHOW). Set switches S1 to S3 Off (the bottom one in the group does nothing so may be left in either position). This disables the “additional delay” aspect of the circuit. Set Frequency control VR4 to approximately mid-track position.

Connect the batteries, set the selector switch S4 to “UK” and switch on. The neon indicator should emit double flashes. Adjust VR1 so that the time for one cycle is two seconds (30 cycles per minute). Now, switch S1 on. Re-test and note that the timing has increased.

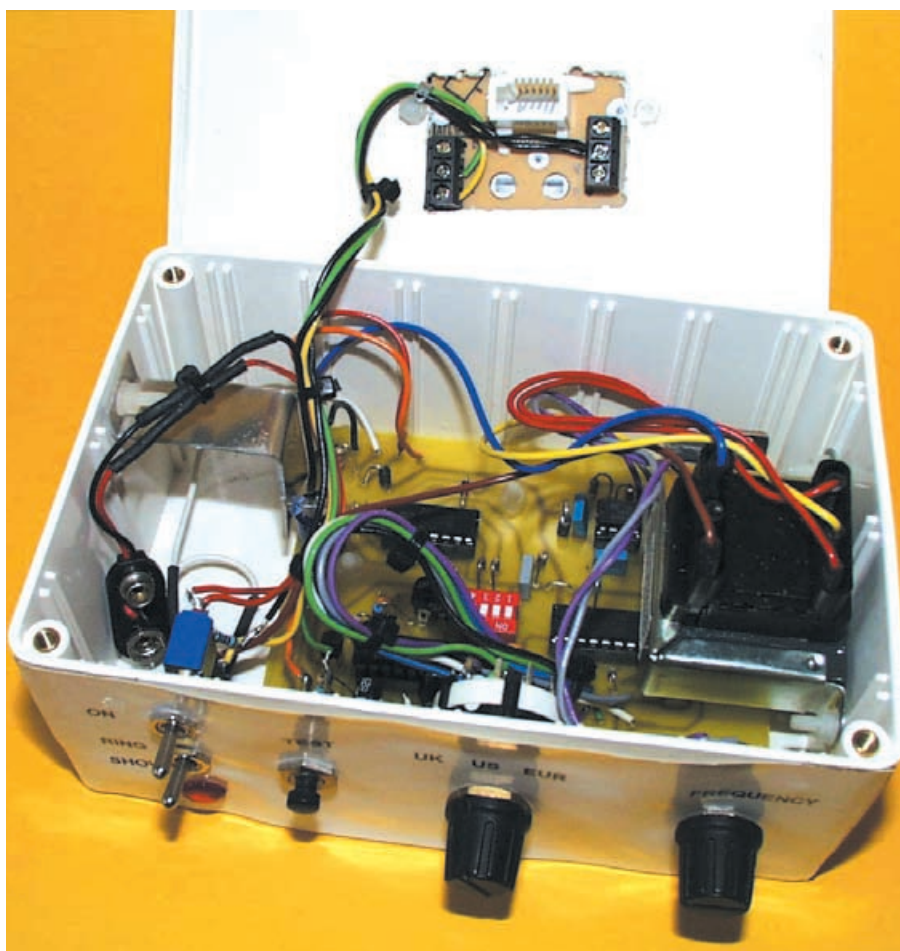Adjust preset VR3 so that each cycle takes three seconds (20 cycles per minute). If this is found to be impossible, switch S2 on also and, if necessary, all three switches S1 to S3.



Layout of components inside the plastic case. The transformer is bolted to one side panel and the phone socket mounted on the lid

In the Mode

It is now necessary to adjust the circuit for US and European tones. Set the selector switch to “US” – the neon should emit single flashes. Adjust preset VR2 so that each cycle takes six seconds (10 per minute). It should now operate for two seconds on and four seconds off. When switched to “Euro”, it should provide one second on and four seconds off automatically. Test using a

telephone (switch S7 set to RING). If you have a traditional unit, adjust VR4 to give the loudest sound.

Set switch S7 to SHOW and press TEST button S6. Speak or blow into the microphone. If you hear it in the earpiece, the speech circuit is working (ignore the fact that it may not be very loud or clear and you will hear some breakthrough of the ring signal).

EPE

Circuit Surgery

Ian Bell



Op amp Output Capabilities

THIS month we look at a query from the EPE Chat Zone from member **Kenon**, which refers to the circuit in Fig.1 and raises some issues about the output capabilities of op amps:

"When the load is disconnected, the output voltage of the op amp is 5V. On the other hand, when the load is connected with the op amp, the voltage across the load is zero. I found that the output resistance of LM741 is 75Ω. Is it the problem of impedance mismatch or the op amp has not enough power to drive the load?"

The simple answer, as was quickly pointed out on the forum, is that a 5V output from the op amp into 1Ω would require 5A – well beyond the capabilities of the 741. In fact the 741 has short circuit protection, limiting the output current to 25mA, which corresponds to 25mV across 1Ω, probably much lower than the intended output voltage.

Op amp Outputs

In response to this question, we will look at the output capabilities of op amps in a little more detail, starting with the output resistance. The question also raises the issue of impedance matching, which often causes difficulties, so we will look at that too. We will also look at the output short circuit protection which enables the 741 (and most other op amps) to survive having its output shorted to ground.

The datasheet value for the 741's output resistance, as Kenon mentions is 75Ω. However, the output resistance of the inverting amplifier configuration used in the circuit in Fig.1 is much less than this due the beneficial effects of the negative feedback used. Fig.2 shows Fig.1 redrawn for looking at the output resistance.

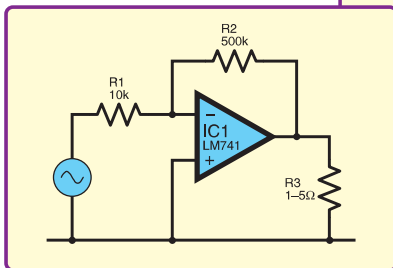


Fig.1. Kenon's original circuit

In Fig.2 we have removed the troublesome load, included a voltage source to represent the op amp's output signal, and added a resistor to represent the output resistance of the op amp. The full analysis involves setting $V_{in} = 0$, applying a voltage to the circuit output and finding the resulting current. We will just skip to the result.

Finding Output Resistance

The output resistance of the inverting amplifier circuit as a whole, R_{Out} , see Fig.2, is related to the output resistance of the op amp, R_O , by

$$R_{Out} = \frac{R_O}{1 + \beta A}$$

where A is the open loop gain of the op amp and β is the feedback fraction, that is the proportion of the output signal that is fed back to the op amp's inverting input. This is given by the "potential divider formula" for R_1 and R_2 .

$$\beta = \frac{R_1}{R_1 + R_2}$$

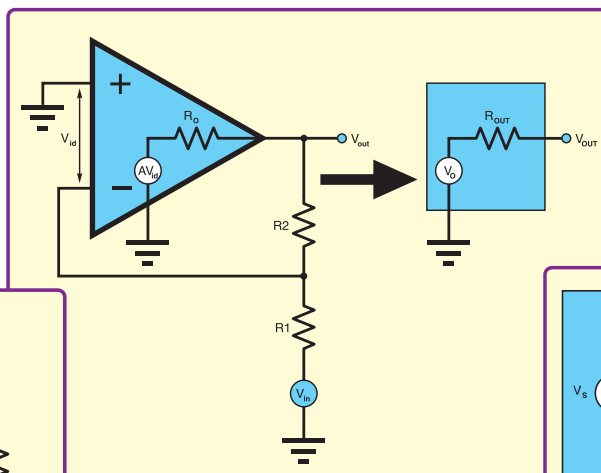


Fig.2. Inverting op amp amplifier showing op amp output resistance, R_O , and equivalent circuit for the complete amplifier with output resistance R_{OUT}

For Kenon's circuit $R_1 = 10k$ and $R_2 = 500k$ so $\beta = 10/510 = 0.0196$.

For a typical open loop gain of 200000 for the 741 (quoted as 200V/mV on the datasheet) the output resistance is just under 0.02Ω:

$$R_{Out} = \frac{75}{1 + (0.0196 \times 200000)} = 0.0191\Omega$$

Now we know the output resistance we can consider matching and loading. Although we have already stated that the problem with the circuit is due to overloading, we can have a look at matching and see if that is a problem as well. We will imagine for a while that the op amp's output current is not limited.

There are a number of different scenarios and problems which could be put under the heading of "matching", but here we have what is probably the simplest case – that of a source with resistance R_S connected to load of resistance R_L as shown in Fig.3.

Matching

The matching problem is basically one of choosing the most appropriate R_L given that we know R_S (or vice versa). Of course if R_L and R_S are already determined we can work out what is going to happen using the same theory.

The two resistances in Fig.3 form a potential divider. Thus the voltage across the load is given by:

$$V_L = \frac{R_L}{(R_S + R_L)} V_S$$

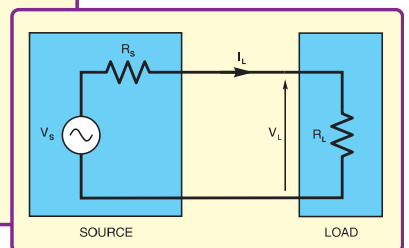


Fig.3. A source and load connected together

We get this equation by using Ohm's law to get the current through the two resistances (V_S divided by the total resistance: R_L plus R_S) and applying Ohm's law again to get the voltage drop across R_L (by multiplying the current by R_L).

From the equation we see that if we want V_L to be as large as possible then R_L must be much larger than R_S . If R_L is very much larger than R_S then the load voltage is effectively equal to the source voltage.

The current in the load is given by

$$I_L = \frac{V_S}{(Z_S + Z_L)}$$

Thus if we want the current in the load to be as high as possible we need to make Z_L much smaller than Z_S . As might be expected this is the opposite requirement to the one for maximising the voltage across the load.

Unmatched Load and Source

Given that the term "matching" might imply $R_S = R_L$, the two scenarios we have just looked at – maximum V_L by making R_L much larger than R_S , and maximum I_L by making R_L much smaller than R_S , indicate what happens when load and source are not "matched". However, in general we should really be asking *what is the most appropriate load for this source?* – matching in the sense of $R_S = R_L$ is not always what we want.

For example (briefly moving away from the specific circuit we are looking at here), a high impedance input (R_L much greater than R_S) may be most appropriate for amplifying the voltage from a sensor (here R_S is the sensor output resistance and R_L the amplifier input resistance). Similarly, Kenon may want the output voltage to be unaffected by the load so that we get the required voltage gain (50) from the circuit, thus again we would need R_L to be much greater than R_S .

The loss of (voltage) signal in decibels due to loading (load loss) can be calculated as follows:

$$\text{Load loss} = 20 \log \left[\frac{R_L}{(R_S + R_L)} \right]$$

In general it is a good idea to have R_L about ten times as large as R_S if you want to maximise the voltage signal. This results in a load loss of less than 1dB.

For Kenon's circuit (assuming that voltage across the load is the important factor, not power to the load, and still ignoring the fact that the 741 is actually overloaded) we would get a loss of 0.17dB for $R_L = 1.0$ and $R_S = 0.02$. This result just serves to highlight that the lack of output voltage is due to *over-loading* rather than "matching".

The circuit fails to produce the required output voltage because it is not capable of delivering the required current, rather than because the output resistance is too high. Of course, once the op amp goes into overload and switches on its protection circuits the conditions under which the output resistance was calculated no longer hold and value does not really mean anything.

It is also worth noting that the open loop op amp output resistance of 75Ω would

lead to a load loss of 38dB with the same load (again assuming no overloading), demonstrating the strong effect of feedback on circuit behaviour. When working with op amp circuits it is important to remember that the *circuit's* characteristics are not necessarily the same as the *op amp's*. The amount of feedback and specific circuit configuration used must be taken into account.

Power Transfer

To broaden the discussion on matching for a moment, consider what happens when $R_S = R_L$ – why might this be useful? The answer is that maximum *power* is transferred from source to load. In order to prove this you have to use calculus to find the maximum of the relationship between load power and load resistance.

The power transfer aspect of matching is important in power amplifier outputs. For example, consider a power amplifier producing a 3V RMS signal with 1Ω output resistance; the power into loads of various resistances are listed below. The maximum power is obtained for a load of 1 – matching the source resistance. The maximum power delivered to the load is half of the power taken from the source at that point, as the load resistance increases above being equal to R_S a greater proportion of the source's power ends up in the load, but the actual power delivered decreases.

Load	RMS Power in Load (1Ω source at 3V RMS))
0.25Ω	1.4W
0.5Ω	2.0W
1Ω	2.3W
1.5Ω	2.2W
2Ω	2.0W
3Ω	1.7W

It is worth pointing out that Fig.3 does not apply to all situations where the issue of matching may arise. An important case is high frequencies on long wires, where the wire must be considered as a transmission line. We then have to model the wire between the source and load rather than assuming a simple connection. Secondly, not all "sources" are really sources in the sense of Fig.3. For example, some sensors vary in impedance, but do not contain a voltage source.

Short Circuit Protection

As we have already said, Kenon's circuit will cause the 741 to activate its short circuit protection. To see what is going on we have to look inside the op amp. Fig.4 shows the 741's output circuit (μA741 from Texas Instruments www.ti.com). Note that other sources on 741 schematics may vary from the one given, but the basic configuration should be similar.

Fig.5 shows a simplified version of the output circuit with the protection circuit (TR4, TR5, R1, R2) removed and biasing circuitry (TR6, TR7, TR8, R3, R4) simplified to a current source and two diodes. The diodes are the base-emitter junctions of TR7 and TR8. Hopefully, Fig.5 makes it easier to see that the circuit is basically a push-pull emitter follower in which TR1 conducts for positive signal voltages and TR2 for negative voltages.

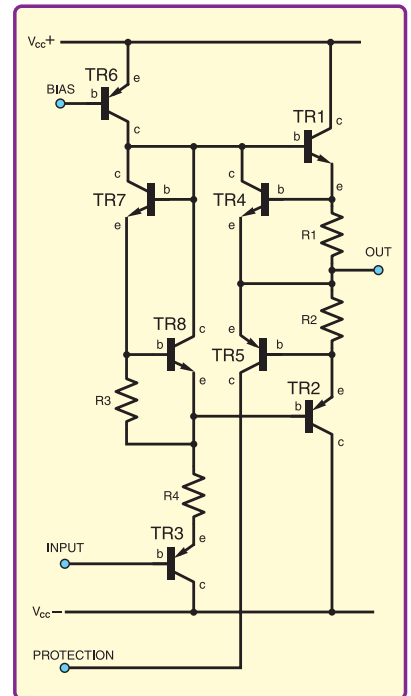


Fig.4. The μA741 output circuit (from TI data sheet)

As the input signal varies, the diodes maintain a constant $2 \times V_{BE}$ difference between the two base voltages ensuring that they are both biased to the point of just conducting with no signal present. The actual base voltages will vary with the signal, but the difference between them is fixed by this biasing arrangement. The diodes are ideally at the same temperature as the output transistors so that changes in their voltage drop with temperature tracks those of the output transistor.

The push-pull amplifier is likely to be damaged if its output is short-circuited to ground due to the excessive collector current which will flow in the conducting transistor. Part of the short-circuit protection circuitry is shown in Fig.6. The protection circuitry monitors the current flowing in the output and turns off the output transistor if the current exceeds some pre-defined limit. The current detection is achieved by using a small resistor (R_1 , about 22Ω) in the output signal path, and a transistor to switch off the output.

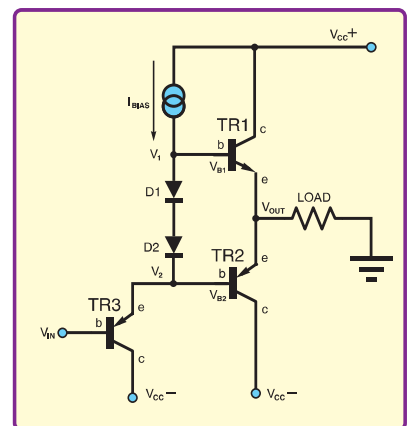


Fig.5. Simplified output circuit

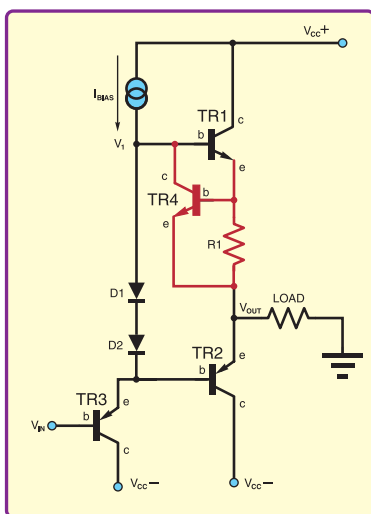


Fig.6. Output stage with part of the protection circuit (protection circuit is shown in red)

The output current causes a voltage drop across the resistor. The protection transistor (TR4) switches on when the resistor voltage reaches 0.55V to 0.6V. The protection transistor is connected so that when it is on it effectively short-circuits the input to the power transistors, so they have no signal to amplify.

The protection resistor values, $R1 = \frac{V_{BE\ TR4}}{I_{max}}$ where $V_{BE\ TR4}$ is the turn-on voltage of the protection transistor (typically 0.55V) and I_{max} is the maximum output current, i.e. the current at which the protection kicks in. For $R1 = 22\Omega$ and $V_{BE\ TR4} = 0.55V$ we get a current limit of 25mA.

The other part of the protection circuit, TR5 and R2, works in the same way but connects back to earlier in the circuit to also switch off other transistors which would otherwise be subject to excessive power dissipation.

Which Op amp?

As the 741 is not capable of driving the loads required by Kenon's circuit, the question arises as to what might do the job.

One possibility, particularly if voltage amplification is the key requirement, is to use a high power op amp. For example, the LM675 from National Semiconductor is capable of delivering output currents in excess of 3A, operating at supply voltages of up to 60V. The OPA541 from Texas Instruments is capable of operation from power supplies up to $\pm 40V$ and delivering continuous output currents up to 5A. Another possibility, if power amplification is the main aim, would be to use a power amplifier IC (such as an audio power amplifier).

A search of manufacture's web sites will provide more devices to investigate. In all cases the data sheets need to be consulted to check the suitability for the application. Many power op amps are designed for use in circuits with gains of five or 10 or more (not a problem here). If the load is capacitive or inductive, then the ratings of the device may be reduced and special circuit techniques may be advised on the datasheet. Correct heatsinking is also essential for success with high power ICs.

NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of **Everyday Practical Electronics** for me each month

Name and Address

..... Post Code Tel

Everyday Practical Electronics is published on the second Thursday of each month and distributed S.O.R. by SEYMOUR
Make sure of your copy each month – cut out or photocopy this form, fill it in and hand it to your newsagent

Net Work

Alan Winstanley



OUR Internet column continues with our theme of using Skype, the free Internet-based telephony and video calling service. Having set up the Skype software as described previously, try clicking your own name in the contacts list followed by the Edit My Profile button: instead of the default “head and shoulders” icon, click Change.... and point to an image or logo on your hard disk. Skype will resize it and your graphic will now appear against your name in all your friends’ contact lists.

You can also right-click Skype usernames in your contacts list and change them to something more recognisable, for example instead of “fredsmith1927057” you could rename it to “Fred”.

If you are gathering quite a number of entries in your Contacts list, trying sorting them into Groups to manage them (e.g. friends, work-mates): go View/Show Contact Groups and then drag names to the appropriate labels.

VoIP Phones

For those users who want to get into Skype in a big way, they might consider using a dedicated VoIP (Voice over Internet Protocol) telephone instead, which offers a more familiar-feeling way of communicating with fellow users. A number of new VoIP phones are coming onto the market that are certified for use with Skype: simply plug them into a PC’s USB port and install the phone’s USB drivers, and then use the handset to call Skype users for free, or ring non-Skype telephone numbers anywhere in the world using “SkypeOut” credits. Quality and price varies, and one cheap unbranded VoIP phone tested by the writer failed to work at all and was scrapped.

More sophisticated phones may have a built-in address book and other features including mono or colour LCD display, and some may offer wireless operation, such as the Qpe Wireless VoIP Phone from Maplin (www.maplin.co.uk). On the web, Watford Electronics (www.savastore.com) currently offer the US Robotics USR809600 VoIP USB Skype phone for just £20 which is good value compared to unbranded ones. It has an LCD display and supports Skype Caller ID. They also list the interesting-looking Linksys CIT200-UK DECT cordless Skype Handset for £71.


Displaying a trend towards converging communications, “hybrid” phones are emerging with Panasonic introducing their new Skype compatible KX-TG9000 handset in some countries: it connects to a POTS landline as well as to a broadband connection, so you can choose how to route your calls.

Possibly the neatest alternative of all is to try a Bluetooth cordless headset for hands-free use with a PC. In the writer’s own experience, setting up Bluetooth on a PC has always been a troublesome process. A USB Bluetooth dongle is required (note, Class 1 Bluetooth devices have a 100 metre range – Class 2 types are limited to about 10 metres), but be prepared for plenty of hairpulling when trying to make Bluetooth devices talk to each other. Some technical hints and tips on

Bluetooth headsets may be found in a Skype forum at <http://tinyurl.com/9kj3j>.

Video Stars

One of Skype’s major benefits is the ability to video-communicate with friends and relatives no matter where they are in the world. Seeing and hearing distant family and friends in this way can be a hugely rewarding and enjoyable experience. Not only will Skype play the contact’s video image live in a window, a small thumbnail of yourself is also provided (see screenshot). Full screen video can also be selected.

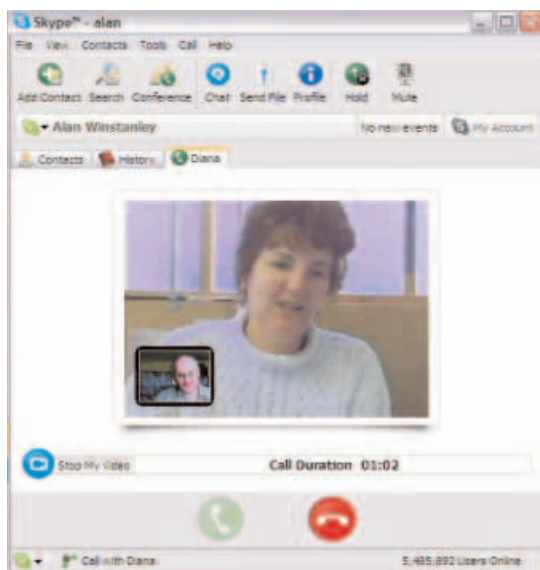

A Skype video call in progress, with a thumbnail self-image. Full screen video can also be selected. Note the Hold and microphone Mute buttons in the toolbar

It should be pointed out from the start that neither sound nor vision will be perfect: expect some sound lag at times and occasional pixelation of images. Performance seems to tail off in the evening as general Internet traffic increases, but overall the quality of Skype video is more than acceptable – especially as it’s free. Sometimes, sound performance has also been astonishingly good.

A web camera is needed and in this respect buyers are spoiled for choice. Try checking your digital still camera for a webcam or “USB Cam” mode that allows a direct connection to a computer. A small desktop tripod can be bought for a few pounds and a separate microphone will possibly be required; a mains adaptor for the camera may be useful. Note that a number of digicams have a “video out” mode but this may be intended for displaying digital images on a television screen. This is not suitable for Skype video.

Most users will probably opt to buy a dedicated webcam. As always, you get what you pay for and popular brands include Logitech, Creative and Philips (e.g. see www.amazon.co.uk). They are USB connected and may have a clamp to fit them on top of an LCD monitor or laptop. Also look for a built-in microphone, a snapshot button and an “on air” l.e.d.; some webcams include a separate privacy headset as well. Image resolution is measured in pixels: almost all seem to offer native VGA 640 x 480 pixels, which is perfectly adequate for webcam use.

The author’s Logitech 5000 camera is somewhat bulky but has an extra-wide field of view to allow family members to appear in one image with less distortion. It also has a pop-down privacy visor. Sound quality via the integral microphone is good (remember to make a test call to Skype to check out your sound system – see last month).

The more expensive cameras such as the Logitech 5000 and the Philips SPC 900NC include intelligent face-tracking software which is quite eerie to behold: it zooms in or “electronically” follows the subject around the room (within limits) without physically moving. (Unfortunately the current Skype software seems to forget these default settings in between sessions.)

Next month, I will outline some alternatives to Skype that will enable you to use an ordinary telephone on your broadband connection. You can Email the writer at alan@epemag.demon.co.uk



EPE EVERYDAY PRACTICAL ELECTRONICS



UK readers you can
SAVE 55p
on every issue of *EPE*

How would you like to pay £2.75 instead of £3.30 for your copy of *EPE*?
Well you can – just take out a one year subscription and save 55p an issue,
or £6.60 over the year

You can even save over 75p an issue if you subscribe for two years
– a total saving of £18.20

Overseas rates also represent exceptional value

You also:

- Avoid any cover price increase for the duration of your subscription
- Get your magazine delivered to your door each month
- Ensure your copy, even if the newsagents sell out

Order by phone or fax with a credit card or by post with a cheque or postal order, or
buy on-line from www.epemag.co.uk (click on “Subscribe Now”)

EPE SUBSCRIPTION PRICES

Subscriptions for delivery direct to any address in the UK:
6 months £17.50, 12 months £33, two years £61; Overseas:
6 months £20.50 standard air service or £29.50 express airmail,
12 months £39 standard air service or £57 express airmail,
24 months £73 standard air service or £109 express airmail.
Cheques or bank drafts (in **£ sterling only**) payable to *Everyday Practical Electronics* and sent to *EPE Subs. Dept.*, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872. Fax: 01202 874562. Email: subs@epemag.wimborne.co.uk. Also via the **Web** at <http://www.epemag.co.uk>. Subscriptions start with the next available issue. We accept MasterCard, Amex, Diners Club, Maestro or Visa. (For past issues see the *Back Issues* page.)

ONLINE SUBSCRIPTIONS

Online subscriptions, for downloading the magazine via the Internet, \$15.99US (approx. £9.50) for one year available from www.epemag.com.

USA/CANADA SUBSCRIPTIONS

To subscribe to *EPE* from the USA or Canada please telephone Express Mag toll free on 1877 363-1310 and have your credit card details ready. Or fax (514) 355 3332 or write to Express Mag, PO Box 2769, Plattsburgh, NY 12901-0239 or Express Mag, 8155 Larrey Street, Anjou, Quebec, H1J 2L5.
Email address: expsmag@expressmag.com.

Web site: www.expressmag.com.
USA price \$60(US) per annum, Canada price \$97(Can) per annum – 12 issues per year.

Everyday Practical Electronics, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to *Everyday Practical Electronics*, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.

SUBSCRIPTION ORDER FORM



- ☐ 6 Months: UK £17.50, Overseas £20.50
(standard air service), £29.50 (express airmail)
☐ 1 Year: UK £33.00, Overseas £39.00 (standard air service)
£57 (express airmail)
☐ 2 Years: UK £61.00, Overseas £73.00 (standard air service)
£109 (express airmail)

To: *Everyday Practical Electronics*,
Wimborne Publishing Ltd., 408 Wimborne Road East,
Ferndown, Dorset BH22 9ND

Tel: 01202 873872 Fax: 01202 874562
E-mail: subs@epemag.wimborne.co.uk

I enclose payment of £ (cheque/PO in £ sterling only), payable to *Everyday Practical Electronics*

My card number is:
Please print clearly, and check that you have the number correct

Signature

Card Security Code (The last 3 digits on or just under the signature strip)

Card Ex. Date Maestro Issue No.

Name

Address

Post code Tel.

Subscriptions can only start with the next available issue.

READOUT

Email: john.becker@wimborne.co.uk

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

All letters quoted here have previously been replied to directly.

WIN AN ATLAS LCR ANALYSER WORTH £79

An Atlas LCR Passive Component Analyser, kindly donated by Peak Electronic Design Ltd., will be awarded to the author of the *Letter Of The Month* each month.

The Atlas LCR automatically measures inductance from 1 μ H to 10H, capacitance from 1pF to 10,000 μ F and resistance from 1 Ω to 2M Ω with a basic accuracy of 1%.
www.peakelec.co.uk



★ LETTER OF THE MONTH ★

Interak and Greenbank

Dear EPE,

Firstly, the new magazine style looks superb – much better quality overall, the diagrams and schematics are clearer and a pleasure to read.

Secondly, it was great to see the letter from David Parkins (*Readout* Jan '06), as he is someone whom I had not heard of for almost 20 years. I had searched for links to him on the Internet but had been unable to find any.

His letter contained some thought provoking comments and really anyone who writes to your magazine with some criticism is only doing so because they do not want to lose a rare and valuable publication. As David says – he has “seen most of them come and go” and electronics magazines are now rarer than hens’ teeth.

During the 1970s and 80s, David was the guiding force behind the Interak computer, this was closely linked to his business Greenbank Electronics. I still use this computer today (it could be the only one left now), which is a Z80 based rack and card system. My system uses CP/M 2.2 as an OS, although there were many other options. The computer was built up by buying specific cards from Greenbank or making your own using a prototype card.

What makes the Interak such a great computer is that it is so versatile – it is really easy to expand and adapt so that almost any type of circuit can be connected to it. Of course it does not have the amazing graphics capability of

modern PCs but I find it ideal as a reliable electronics workhorse.

When the Interak was being sold, David went to great lengths to ensure that his customers were satisfied and the after-sales service was outstanding. I think he would agree that he is something of a perfectionist and this shows in his attention to detail in the copious documentation and circuit diagrams. If he could be persuaded to write some articles on the life and times of Greenbank Electronics I’m sure they would make very interesting reading.

My keen interest in electronics means that I am curious to know what effect every byte and bit are having and I like having control of what goes where in the memory – with today’s PCs this is almost impossible. The Interak allows complete control of every function, it is also great for robotics plus it is fun to use. There are many features of this computer which I find really appealing!

My present project is to use a Compact Flash card as a hard drive storage device. Since most CP/M applications use 20K or less a 64MB Compact Flash will provide more than enough storage. The recent *EPE* articles on Compact Flash were a great assistance and so far I can read the CF Identity Information. I am presently modifying the BIOS to be able to read and write files from the CF.

Regarding the *Readout* issue of programming languages, it depends what you want from your hobby/interest. I appreciate that there are some brilliant high-level languages around now and I can understand some people being very enthusiastic about their favourites but

(and please correct me if I am wrong) I see *EPE* as a practical “hands on” type of publication. I have seen other magazines which cater exclusively for software and because of the vast number of languages around, *EPE* would soon be overburdened in an effort to please everyone.

The languages I use are Z80 assembler, PIC assembler, PicBasicPro, BASIC and Visual Basic. I enjoy assembler because I can (usually) picture the operation of every bit as it is controlled by the code. These few languages seem to be sufficient for my needs at present, which are control and testing of electronic circuits. It would also be interesting to see notes on other languages and perhaps the reason why they work with a particular project. In some cases though, I would question the point of using a high-level language to operate an electronic door lock or for many of the other projects in *EPE*.

Alan Paton, via email

Thanks for an interesting letter, Alan. I don’t think I knew of David’s Greenbank/Interak connection, although Mike would have done.

I agree with EPE’s attitude towards languages. For many years I’ve standardised on PIC assembler and VB6, which do all I want and are interesting to use. You may see a little coverage of other languages from time to time, but we always have to consider what most readers appear to have in terms of facilities and knowledge, and we are not really a “programming” mag in the wider sense.

Increment-Decrement

Dear EPE

I am busy with a PIC program using an LCD, but I am struggling – please help! I have written the program for a PIC16F84A. The program counts up and down in BCD with LEDs as outputs. When the circuit increments, the LCD must display the message “WELCOME”. When it decrements, the LCD must display the message “GOOD-BYE”. When the count reaches 99 the

LCD must display the message “FULL”.
Gordon Mofokeng, South Africa,
via email

I regret that we don’t normally have time to offer design advice to readers in this way, Gordon, but you might raise the question of your problem on our Chat Zone, access via our main page at www.epemag.co.uk and see if any readers might care to advise.

But it seems that you could simply use subtraction of your previous count value

from the current one to find increment or decrement conditions, reading the Carry/Borrow bit of Status to detect greater than or less than, and then using an equality check of the value of 99 with the count value i.e.:

<code>movlw 99</code>	<code>; put 99 into W</code>
<code>xorwf Count,W</code>	<code>; XOR with value in Count</code>
<code>btfss Status, Z</code>	<code>; is answer equal to 0?</code>
<code>return</code>	<code>; no</code>
<code>goto Full</code>	<code>; yes, action display</code>

Electrovalue

David Longland of Electrovalue recently wrote direct to Alan Winstanley regarding our website "history" page:

I am at last emerging from a cloud under which I sank in Sept last year when I had to close down my company, Electrovalue Ltd. Someone told me there was "talk" on the internet on the hole left on our closing. You are running a good chat site which I found this afternoon and also a bit of history promoting fond memories, on www.epemag.wimbome.co.uk/history2.htm.

Many times in the past I have been asked whether we are an offshoot of RS Components, which we were not. I presumed that is was a confusion on their part between Electrovalue and Electrocomponents, the RS holding company. However on reading *history2*, it says that "RS later launched ElectroValue". If this was published, then this could have been the origin (I have no problem with it). I started my company in 1964 trading as "Longland's" and advertised in *Practical Wireless*, later in *Practical Electronics*. In Nov '65 I registered the name Electrovalue and started trading as that.

Anyway, its nice to make contact with the old world and now I'll continue with my retirement.

David Longland, via email

Alan replied to David:

It is very good of you to write, David, and we're pleased to hear from you again. I've copied it to John.

It came as a huge shock to me to learn that you had ceased trading. I always had a healthy respect for the extremely interesting range of components that you sold, and especially those tricky parts – LED bezels, C&K miniature toggle switch dress nuts and PVC tang covers, and the famous range of Siemens components, RF parts and filters. Alfacs transfers and Seno GS etchant. All the quality parts that made my projects look good. And you listed the first blue LED that I ever saw (£30!)

I was aware of you were independent of RS, but now that you mention it, I have not until now connected your Electrovalue name with that of the RS offshoot (the RS catalogue with a different cover – was it ElectroSpares I now ask myself?). Now I'm not sure any more! Perhaps John knows.

If there is any error on my web pages then I would definitely like to correct it, and also I'll add your comments into the text as I'm sure readers will be pleased to see them.

It is encouraging if you feel able to turn the corner after having endured such a shock. One thing I have learned in life is that what seems like the end of a road usually turns out to be a bend. So I hope something new comes up that will help you along again.

Alan Winstanley

I replied to David and Alan:

David, I'm very sorry to learn about Electrovalue closing. You have been one of the stalwart names for many years. The marketplace will miss you. But Alan's right; my own similar statement is that as one door closes another can open, sometimes with great benefit, as I've discovered over the years.

Alan, Electromail was the RS outlet! Certainly Doran (the Door to Amateur electronics) was another, but that went long before Electromail.

All our very best wishes David.

Digital Terrestrial TV Again

Dear EPE,

Just thought I would drop you a line in reply to Ken Wood's letter in *Readout* April '06 about Digital Terrestrial TV, and also the comments about remote control ranges.

There is a device already available to convert the video output from a digital receiver to an analogue RF signal. This is an RF modulator and some have either a Scart input or an RCA phono input that converts from composite video to RF on the standard coaxial connectors. They can also be tuned across the analogue band between channels 21 to 69 thus giving an interference-free picture.

The modulator can be fitted on the output of the Freeview box connected via the Scart output, the RF from the modulator then connects into the VCR on the system then the output from here is "piped" into the distribution amplifier and fed to the various outlets around the house.

The setup of the modulator can be a little tricky and usually results in an initial poor quality picture, this is usually attributed to being on the same frequency as a terrestrial TV channel or maybe the same frequency as the VCR! This in effect generates an RF signal of its own through its own internal modulator. A simple way to fix this problem is by tuning the modulator to a different frequency, clear ones can be found by tuning the TV or VCR to what can be seen as a "blank" area on the band i.e. just snow. (If you do get a poor picture just unplug the modulator and see if there is a faint signal in the background, dead give-away!)

The modulators usually have an aerial input as well as output so the existing terrestrial aerial can be fed through it. If this is a problem then an aerial combiner or diplexer can be used. This connects two aerial inputs to one output.

The remote control can be assisted using a remote extender. This is a two-part device that has an infra red receiver and transmitter. They convert the signals to RF between them and the most common look like pyramids. The receiver goes next to the TV or other equipment to be controlled. The transmitter goes usually in the bedroom or wherever the control is being used, the remote is aimed at the transmitter and an RF signal is sent to the receiver that converts the

signal back to infra red. It was mainly used for remote control from the bedroom down to the living room.

The components are available from CPC, www.cpc.co.uk, RF modulator SR05358, at approx. £35 and from <http://cpc.farnell.com/jsp/endecaSearch/partDetail.jsp?SKU=AVVRX569>, at £13.61.

Dave Barsby, via email

Modulators used to be far more common, Dave. I recall buying little oblong tins with them in and used them for all sorts of purposes. Then along comes Channel 5, which transmits on a similar frequency, and which I used, and indeed was set in my VCR at the time, and which became unusable. When C5 started locally (I live not far from the Crystal Palace transmitter), teams of C5 reps went round households with such VCRs and somehow returned all the modulators in them. But ours never seemed the same again. Got DVD now and am not sure what they use, if at all.

PIC Development

Dear EPE,

Over the past couple of years I've noticed quite a large amount of cheap and cheerful electronic games and gadgets being sold that contain both an LCD display and some kind of input device, some including a full qwerty keypad. This got me thinking that these would make ideal low cost development systems for a PIC.

Most PIC projects seem to require an LCD and every one some kind of human input device so why not cut down on hardware building and modify one of these devices?

I have actually already read all the *EPE* articles on LCD interfacing etc. I'm now interested in developing smaller and cheaper handheld units though as the standard keypads and LCDs you buy for hobby development are rather large and also expensive.

This is what made me think of all the current cheap handheld devices that are about and could possibly be used for other purposes. So far, all the devices I've dismantled to investigate use a "die on board construction" which makes the product cheaper to produce but also impossible for anyone to experiment with.

I was wondering whether maybe one of your readers has had a similar idea but has actually managed to find a useable device (i.e. one where it's actually possible to connect to the LCD, keypad and micro.)

Lee Archer, via email

Lee, at various times I've shown in *EPE* how to interface LCDs, GLCDs, keypads, keyboards and mice to PICs, but you've obviously read them. You could also ask the question via our Chat Zone (access also via www.epemag.co.uk). Readers, any suggestions for Lee?

DIRECT BOOK SERVICE

NOTE: ALL PRICES INCLUDE UK POSTAGE

FREE Two booklets and a Circuit Surgery CD-ROM with Teach-In 2000 CD-ROM



EPE TEACH-IN 2000 CD-ROM

The whole of the 12-part *Teach-In 2000* series by John Becker (published in *EPE* Nov '99 to Oct 2000) is now available on CD-ROM. Plus the *Teach-In 2000* interactive software (Win 95, 98, ME and above) covering all aspects of the series and Alan Winstanley's *Basic Soldering Guide* (including illustrations and Desoldering).

Teach-In 2000 covers all the basic principles of electronics from Ohm's Law to Displays, including Op.Amps, Logic Gates etc. Each part has its own section on the interactive software where you can also change component values in the various on-screen demonstration circuits.

The series gives a hands-on approach to electronics with numerous breadboard circuits to try out, plus a simple computer interface (Win 95, 98, ME only) which allows a PC to be used as a basic oscilloscope.

ONLY **£12.45** including VAT and p&p

Order code Teach-In CD-ROM

Circuits and Design

A BEGINNER'S GUIDE TO TTL DIGITAL ICs R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip/flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the "real world".

142 pages

Order code BP332

£5.45

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias – tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Order code BP53

£5.49

MICROCONTROLLER COOKBOOK Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£23.99

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

FOR A FURTHER
SELECTION OF BOOKS
SEE THE NEXT TWO
ISSUES OF EPE

All prices include UK
postage

Computing & Robotics

WINDOWS XP EXPLAINED N. Kantaris and P. R. M. Oliver

If you want to know what to do next when confronted with Microsoft's Windows XP screen, then this book is for you. It applies to both the Professional and Home editions. The book was written with the non-expert, busy person in mind. It explains what hardware requirements you need in order to run Windows XP successfully, and gives an overview of the Windows XP environment.

The book explains: How to manipulate Windows, and how to use the Control Panel to add or change your printer, and control your display; How to control information using WordPad, Notepad and Paint, and how to use the Clipboard facility to transfer information between Windows applications; How to be in control of your filing system using Windows Explorer and My Computer; How to control printers, fonts, characters, multimedia and images, and how to add hardware and software to your system; How to configure your system to communicate with the outside world, and use Outlook Express for all your email requirements; How to use the Windows Media Player 8 to play your CDs, burn CDs with your favourite tracks, use the Radio Tuner, transfer your videos to your PC, and how to use the Sound Recorder and Movie Maker; How to use the System Tools to restore your system to a previously working state, using Microsoft's Website to update your Windows set-up, how to clean up, defragment and scan your hard disk, and how to backup and restore your data; How to successfully transfer text from those old but cherished MS-DOS programs.

268 pages

Order code BP514

£7.99

INTRODUCING ROBOTICS WITH LEGO MINDSTORMS Robert Penfold

Shows the reader how to build a variety of increasingly sophisticated computer controlled robots using the brilliant Lego Mindstorms Robotic Invention System (RIS). Initially covers fundamental building techniques and mechanics needed to construct strong and efficient robots using the various "click-together" components supplied in the basic RIS kit. Explains in simple terms how the "brain" of the robot may be programmed on screen using a PC and "zapped" to the robot over an infra-red link. Also, shows how a more sophisticated Windows programming language such as Visual BASIC may be used to control the robots.

Detailed building and programming instructions provided, including numerous step-by-step photographs.

288 pages – large format

Order code BP901

£14.99

MORE ADVANCED ROBOTICS WITH LEGO MINDSTORMS – Robert Penfold

Covers the Vision Command System

Shows the reader how to extend the capabilities of the brilliant Lego Mindstorms Robotic Invention System (RIS) by using Lego's own accessories and some simple home constructed units. You will be able to build robots that can provide you with 'waiter service' when you clap your hands, perform tricks, 'see' and avoid objects by using 'bats radar', or accurately follow a line marked on

the floor. Learn to use additional types of sensors including rotation, light, temperature, sound and ultrasonic and also explore the possibilities provided by using an additional (third) motor. For the less experienced, RCX code programs accompany most of the featured robots. However, the more adventurous reader is also shown how to write programs using Microsoft's VisualBASIC running with the ActiveX control (Spirit.OCX) that is provided with the RIS kit.

Detailed building instructions are provided for the featured robots, including numerous step-by-step photographs. The designs include rover vehicles, a virtual pet, a robot arm, an 'intelligent' sweet dispenser and a colour conscious robot that will try to grab objects of a specific colour.

298 pages

Order code BP902

£14.99

PIC YOUR PERSONAL INTRODUCTORY COURSE SECOND EDITION John Morton

Discover the potential of the PIC microcontroller through graded projects – this book could revolutionise your electronics construction work!

A uniquely concise and practical guide to getting up and running with the PIC Microcontroller. The PIC is one of the most popular of the microcontrollers that are transforming electronic project work and product design.

Assuming no prior knowledge of microcontrollers and introducing the PICs capabilities through simple projects, this book is ideal for use in schools and colleges. It is the ideal introduction for students, teachers, technicians and electronics enthusiasts. The step-by-step explanations make it ideal for self-study too: this is not a reference book – you start work with the PIC straight away.

The revised second edition covers the popular reprogrammable EEPROM PICs: P16C84/16F84 as well as the P54 and P71 families.

270 pages

Order code NE36

£16.99

INTRODUCTION TO MICROPROCESSORS John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

222 pages

Order code NE31

£21.99

EASY PC CASE MODDING R.A. Penfold

Why not turn that anonymous grey tower, that is the heart of your computer system, into a source of visual wonderment and fascination. To start, you need to change the case or some case panels for ones that are transparent. This will then allow the inside of your computer and it's working parts to be clearly visible.

There are now numerous accessories that are relatively inexpensive and freely available, for those wishing to customise their PC with added colour and light. Cables and fans can be made to glow, interior lights can be added, and it can all be seen to good effect through the transparent case. Exterior lighting and many other attractive accessories may also be fitted.

This, in essence, is case modding or PC Customising as it is sometimes called and this book provides all the practical details you need for using the main types of case modding components including: Electro luminescent (EL) 'go-faster' stripes; Internal lighting units: Fancy EL panels: Data cables with built-in lighting: Data cables that glow with the aid of 'black' light from an ultraviolet (UV) tube: Digital display panels: LED case and heatsink fans: Coloured power supply covers.

192 pages

Order code BP542

£8.99

NEWNES PC TROUBLESHOOTING POCKET BOOK – THIRD EDITION Howard Anderson, Mike Tooley

All the essential data for PC fault-finding and upgrading. This book provides a concise and compact reference that describes, in a clear and straightforward manner, the principles and practice of fault-finding and upgrading PCs and peripherals. The book is aimed at anyone who is involved with the installation, configuration, maintenance, upgrading, repair or support of PC systems. It also provides non-technical users with sufficient background information, charts and checklists to enable the diagnosis of faults and help to carry out simple modifications and repairs. In order to reflect rapid changes in computer technology (both hardware and software) this new edition has been completely revised and rewritten.

256 pages

Order code NE41

£19.99

NEWNES INTERFACING COMPANION Tony Fischer-Cripps

A uniquely concise and practical guide to the hardware, applications and design issues involved in computer interfacing and the use of transducers and instrumentation.

Newnes Interfacing Companion presents the essential information needed to design a PC-based interfacing system from the selection of suitable transducers, to collection of data, and the appropriate signal processing and conditioning.

Contents: Part 1 – Transducers; Measurement systems; Temperature; Light; Position and motion; Force, pressure and flow. Part 2 – Interfacing; Number systems; Computer architecture; Assembly language; Interfacing: A to D and D to A conversions; Data communications; Programmable logic controllers; Data acquisition project. Part 3 – Signal processing; Transducer function; Active filters; Instrumentation amplifier; Noise; Digital signal processing.

320 pages

Order code NE38

£26.99

Testing, Theory and Reference

THE AMATEUR SCIENTIST CD-ROM

The complete collection of The Amateur Scientist articles from *Scientific American* magazine. Over 1,000 classic science projects from a renowned source of winning projects. All projects are rated for cost, difficulty and possible hazards.

Plus over 1,000 pages of helpful science techniques that never appeared in *Scientific American*.


Exciting science projects in: Astronomy; Earth Science; Biology; Physics; Chemistry; Weather ... and much more! The most complete resource ever assembled for hobbyists, and professionals looking for novel solutions to research problems. Includes extensive Science Software Library with even more science tools.

Suitable for Mac, Windows, Linux or UNIX. 32MB RAM minimum, Netscape 4.0 or higher or Internet Explorer 4.0 or higher.

Over 1,000 projects

Order code AS1 CD-ROM

£19.95

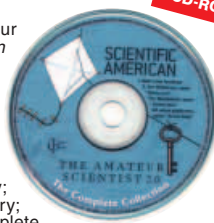

BEBOP BYTES BACK (and the Beboputer Computer Simulator) CD-ROM

Clive (Max) Maxfield and Alvin Brown

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design ... and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the CD-ROM contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the CD-ROM contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this!

Over 800 pages in Adobe Acrobat format

Order code BEB2 CD-ROM £21.95



GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic products.

96 pages

Order code BP239

£5.49

OSCILLOSCOPES – FIFTH EDITION

Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models are available.

This handy guide to oscilloscopes is essential reading for anyone who has to use a 'scope for their work or hobby; electronics designers, technicians, anyone in industry involved in test and measurement, electronics enthusiasts ... Ian Hickman's review of all the latest types of 'scope currently available will prove especially useful for anyone planning to buy – or even build – an oscilloscope.

The contents include a description of the basic oscilloscope; Advanced real-time oscilloscope; Accessories; Using oscilloscopes; Sampling oscilloscopes; Digital storage oscilloscopes; Oscilloscopes for special purposes; How oscilloscopes work (1): the CRT; How oscilloscopes work (2): circuitry; How oscilloscopes work (3): storage CRTs; plus a listing of Oscilloscope manufacturers and suppliers.

288 pages


Order code NE37

£22.99

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

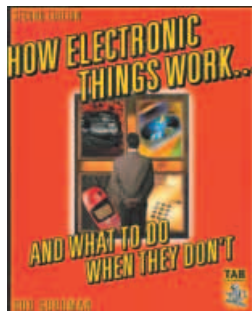To be a real fault finder, you must be able to get a feel for what is going on in the circuit you are examining. In this book Robin Pain explains the basic techniques needed to be a fault finder.



Simple circuit examples are used to illustrate principles and concepts fundamental to the process of fault finding. This is not a book of theory, it is a book of practical tips, hints and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialised.

The fundamental principles of analogue and digital fault finding are described (although, of course, there is no such thing as a "digital fault" – all faults are by nature analogue). This book is written entirely for a fault finder using only the basic fault-finding equipment: a digital multimeter and an oscilloscope. The treatment is non-mathematical (apart from Ohm's law) and all jargon is strictly avoided.

274 pages

Order code NE22

£25.99

ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

In most applications of electronics, test instruments are essential for checking the performance of a system or for diagnosing faults in operation, and so it is important for engineers, technicians, students and hobbyists to understand how the basic test instruments work and how they can be used.

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of these instruments are also examined.

206 pages

Order code PC109

£9.95

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages

Order code PC106

£9.95

UNDERSTANDING ELECTRONIC CONTROL SYSTEMS

Owen Bishop

Owen Bishop has produced a concise, readable text to introduce a wide range of students, technicians and professionals to an important area of electronics. Control is a highly mathematical subject, but here maths is kept to a minimum, with flow charts to illustrate principles and techniques instead of equations.

Cutting edge topics such as microcontrollers, neural networks and fuzzy control are all here, making this an ideal refresher course for those working in industry. Basic principles, control algorithms and hardwired control systems are also fully covered so the resulting book is a comprehensive text and well suited to college courses or background reading for university students.

The text is supported by questions under the headings Keeping Up and Test Your Knowledge so that the reader can develop a sound understanding and the ability to apply the techniques they are learning.

228 pages

Order code NE35

£20.99

HOW ELECTRONIC THINGS WORK – AND WHAT TO DO WHEN THEY DON'T

Robert Goodman

You never again have to be flummoxed, flustered or taken for a ride by a piece of electronics equipment. With this fully illustrated, simple-to-use guide, you will get a grasp on the workings of the electronic world that surrounds you – and even learn to make your own repairs.

You don't need any technical experience. This book gives you: Clear explanations of how things work, written in everyday language. Easy-to-follow, illustrated instructions on using test equipment to diagnose problems. Guidelines to help you decide for or against professional repair. Tips on protecting your expensive equipment from lightning and other electrical damage. Lubrication and maintenance suggestions.

Covers: colour TVs, VCRs, radios, PCs, CD players, printers, telephones, monitors, camcorders, satellite dishes, and much more!

394 pages

Order code MGH3

£21.99

VINTAGE RADIOS – COLLECTING • SERVICING • RESTORING

Tony Thompson

The essential guide to collecting, repairing and restoring vintage valve radios. These receivers are becoming ever more popular as collectibles, this is a good thing because it means that a very large piece of technological history is being reclaimed when at one time many thought it lost forever. If you look around, you will find plenty of valve radio sets just waiting for a loving restoration. They may not yet be the most highly prized, and they are unlikely to be in top condition, but they can be yours and, if you develop the skills outlined in this book, you will possess radio receivers to be proud of.

The book covers radio history, styling, faultfinding, chassis and cabinet restoration, types of set.

124 pages spiral bound

Order code TT1

£13.50

All prices include UK P&P

Project Building

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby.

135 pages

Order code BP392

£5.49

BUILDING VALVE AMPLIFIERS

Morgan Jones

The practical guide to building, modifying, fault-finding and repairing valve amplifiers. A hands-on approach to valve electronics – classic and modern – with a minimum of theory. Planning, fault-finding, and testing are each illustrated by step-by-step examples.

A unique hands-on guide for anyone working with valve (tube in USA) audio equipment – as an electronics experimenter, audiophile or audio engineer.

Particular attention has been paid to answering questions commonly asked by newcomers to the world of the vacuum tube, whether audio enthusiasts tackling their first build, or more experienced amplifier designers seeking to learn the ropes of working with valves. The practical side of this book is reinforced by numerous clear illustrations throughout.

368 pages

Order code NE40

£21.99

Theory and Reference

THE EMERGENCE OF BROADCASTING IN BRITAIN

Brian Hennessy

The beginning of any great enterprise should be recorded for posterity. Few knew that the *Children's Hour* "Uncles", Arthur, Jeff and Caractacus, were also the engineers who struggled by day to develop technical equipment – and would soon become Assistant Controller, Station Director and Organiser of Programmes for the BBC.

This is a very human account, from the dawn of radio to the attainment of a Royal Charter in the late 1920s. It tells of the struggles and frustrations of engineers in developing innovative equipment and of the great John Reith who battled with everyone to bring the BBC from a staff of four up to a Corporation of several hundred.

Brian Hennessy's book also describes the development of broadcasting equipment, the search for premises and looming bankruptcy before ending with the emergence of a firmly established Chartered Corporation – the BBC.

Meticulous research over many years, over a hundred photographs, plans and diagrams as well as interviews with many of those who were there at the time, make this a valuable and original work for those involved in media studies, for radio enthusiasts or simply for those interested in radio and the fascinating story of the emergence of broadcasting.

436 pages

Order code EBB

£26.00

COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages

Order code BP160

£4.49

PRACTICAL ELECTRONIC FILTERS

Owen Bishop

This book deals with the subject in a non-mathematical way. It reviews the main types of filter, explaining in simple terms how each type works and how it is used.

The book also presents a dozen filter-based projects with applications in and around the home or in the constructor's workshop. These include a number of audio projects such as a rhythm sequencer and a multi-voiced electronic organ.

Concluding the book is a practical step-by-step guide to designing simple filters for a wide range of purposes, with circuit diagrams and worked examples.

188 pages

Order code BP299

£5.49

ELECTRONIC PROJECTS FOR EXPERIMENTERS

R. A. Penfold

Many electronic hobbyists who have been pursuing their hobby for a number of years seem to suffer from the dreaded "seen it all before" syndrome. This book is fairly and squarely aimed at sufferers of this complaint, plus any other electronics enthusiasts who yearn to try something a bit different.

The subjects covered include:- Magnetic field detector, Basic Hall effect compass, Hall effect audio isolator, Voice scrambler/descrambler, Bat detector, Bat style echo location, Noise cancelling, LED stroboscope, Infra-red "torch", Electronic breeze detector, Class D power amplifier, Strain gauge amplifier, Super hearing aid.

138 pages

Order code BP371

£5.45

PRACTICAL FIBRE-OPTIC PROJECTS

R. A. Penfold

While fibre-optic cables may have potential advantages over ordinary electric cables, for the electronics enthusiast it is probably their novelty value that makes them worthy of exploration. Fibre-optic cables provide an innovative interesting alternative to electric cables, but in most cases they also represent a practical approach to the problem. This book provides a number of tried and tested circuits for projects that utilize fibre-optic cables.

The projects include:- Simple audio links, F.M. audio link, P.W.M. audio links, Simple d.c. links, P.W.M. d.c. link, P.W.M. motor speed control, RS232C data links, MIDI link, Loop alarms, R.P.M. meter.

All the components used in these designs are readily available, none of them require the constructor to take out a second mortgage.

132 pages

Order code BP374

£5.45

STARTING ELECTRONICS, THIRD EDITION

KEITH BRINDLEY

A punchy practical introduction to self-build electronics. The ideal starting point for home experimenters, technicians and students who want to develop the real hands-on skills of electronics construction.

A highly practical introduction for hobbyists, students, and technicians. Keith Brindley introduces readers to the functions of the main component types, their uses, and the basic principles of building and designing electronic circuits.

Breadboarding layouts make this very much a ready-to-run book for the experimenter, and the use of multimeter, but not oscilloscopes, and readily available, inexpensive components makes the practical work achievable in a home or school setting as well as a fully equipped lab.

288 pages

Order code NE42

£10.99

VIDEO PROJECTS FOR THE ELECTRONICS CONSTRUCTOR

R. A. Penfold

Written by highly respected author R. A. Penfold, this book contains a collection of electronic projects specially designed for video enthusiasts. All the projects can be simply constructed, and most are suitable for the newcomer to project construction, as they are assembled on stripboard.

There are faders, wipers and effects units which will add sparkle and originality to your video recordings, an audio mixer and noise reducer to enhance your soundtracks and a basic computer control interface. Also, there's a useful selection on basic video production techniques to get you started.

Circuits include: video enhancer, improved video enhancer, video fader, horizontal wiper, improved video wiper, negative video unit, fade to grey unit, black and white keyer, vertical wiper, audio mixer, stereo headphone amplifier, dynamic noise reducer, automatic fader, pushbutton fader, computer control interface, 12 volt mains power supply.

124 pages

Order code PC115

£5.45

BOOK ORDERING DETAILS

All prices include UK postage. For postage to Europe (air) and the rest of the world (surface) please add £2 per book. For the rest of the world airmail add £3 per book. CD-ROM prices include VAT and/or postage to anywhere in the world. Send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or card details, Visa, Mastercard, Amex, Diners Club or Maestro to:

**DIRECT BOOK SERVICE, WIMBORNE PUBLISHING LTD.,
408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND.**

Books are normally sent within seven days of receipt of order, but please allow 28 days for delivery – more for overseas orders. *Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.*

For a further selection of books see the next two issues of **EPE**.

Tel 01202 873872 Fax 01202 874562. Email: dbs@wimborne.co.uk

Order from our online shop at: www.epemag.co.uk

BOOK ORDER FORM

Full name:

Address:

.....

.....

..... Post code: Telephone No:

Signature:

☐ I enclose cheque/PO payable to DIRECT BOOK SERVICE for £

☐ Please charge my card £ Card expiry date.....

Card Number Switch/Maestro Issue No.....

Card Security Code (the last three digits on or just under the signature strip)

Please send book order codes:

.....

Please continue on separate sheet of paper if necessary
If you do not wish to cut your magazine, send a letter or copy of this form

We can supply back issues of *EPE* by post, most issues from the past three years are available. An *EPE* index for the last five years is also available at www.epemag.co.uk or see order form below. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photocopy of any *one article* (or *one part* of a series) can be purchased for the same price. Issues from Jan. 99 are available on CD-ROM – see next page – and issues from the last six months are also available to download from www.epemag.com.

Please make sure all components are still available before commencing any project from a back-dated issue.

DID YOU MISS THESE?

FEB '05 Photocopies only

PROJECTS • PIC Electric MK2 Pt1 • Sneaky • Sound Card Mixer • Smart Karts - 5.
FEATURES • Interface • Circuit Surgery • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • E-Blocks and Flowcode V2.0 Reviews • Net Work – The Internet Page

MAR '05

PROJECTS • Cat Flap • Stereo Headphone Monitor • PIC Electric Mk2 Pt2 • Smart Karts - 6 • Bingo Box.

FEATURES • TK3 Simulator and PIC18F Upgrade • Circuit Surgery • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • Practically Speaking • Net Work – The Internet Page

APR '05

PROJECTS • Spontaflex Radio Receiver • Safety Interface • Fridge/Freezer Door Alarm • Smart Karts - 7.

FEATURES • Back To Logic Basics - 1 • Circuit Surgery • Ingenuity Unlimited • Interface • PIC18F Microcontroller Family Introduction • Techno Talk • Net Work – The Internet Page

MAY '05

PROJECTS • Crossword Solver • DAB Radio Aerial • 20W Amplifier Module • Smart Karts - 8 • Water Level Detector • Burglar Alarm

FEATURES • Back To Logic Basics - 2 • Circuit Surgery • Ingenuity Unlimited • Passive Component Testing • Practically Speaking • Techno Talk • Net Work – The Internet Page



JUNE '05

PROJECTS • PIC Ultrasonic Radar • Radio Control Model Switcher • Super-Ear Audio Telescope • Electronic Scarecrow • Digital Lock

FEATURES • Catch the Wave (Tsunami) • Back To Basics - 3 • Digital TV Switchover • Programming PIC 18F Interrupts • Circuit Surgery • Interface • Ingenuity Unlimited • Net Work – The Internet Page

JULY '05

PROJECTS • Cybervox • LF and VLF Converter • Multi-Clap Switch • Doorchime • Electronic Dice

FEATURES • Discovering PICs Reviewed • Back To Basics - 4 • Digital TV Switchover • Practically Speaking • Circuit Surgery • Interface • Net Work – The Internet Page

AUG '05

PROJECTS • Motor Amplifier • Pain Monitor • Audio System-Communications • Kitchen Timer • Room Thermometer

FEATURES • Back To Basics - 5 • Circuit Surgery • Interface • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • NetWork – The Internet Page

SEPT '05

PROJECTS • All Band Radio • Snooker and Darts Scoreboard • Multicore Cable Tester • Controlling Model Railway Signals • Daily Reminder • Whistle Switch

FEATURES • Back To Logic Basics - 6 • Circuit Surgery • Practically Speaking • Ingenuity Unlimited • Techno Talk • PIC 'N' Mix • Net Work – The Internet Page



OCT '05

PROJECTS • Halloween Howler • PIC Based USB Interface • Photic Phone • Telephone Switch • Parking Radar

FEATURES • Introducing the Virtual DIY Calculator • Ingenuity Unlimited • Back To Basics - 7 • Circuit Surgery • Techno Talk • PIC 'N' Mix • Interface • NetWork – The Internet Page

NOV '05

Photocopies only

PROJECTS • Speed Camera Watch Mk2 • PIC Chromatone • Multi-Function R/C Switch • Noughts and Crosses Enigma • Weather Vane Repeater

FEATURES • Teach-In 2006 – Part 1 • Circuit Surgery • Back To Basics - 8 • Techno Talk • Practically Speaking • Ingenuity Unlimited • PIC 'N' Mix • NetWork – The Internet Page

DEC '05

PROJECTS • Vehicle Frost Box Mk2 • Propeller Monitor • Solid-State Hammond • Solid State Valve Power Supply

FEATURES • Teach-In 2006 – Part 2 • Techno Talk • Viewing The Future • Circuit Surgery • Interface • PIC 'N' Mix • NetWork – The Internet Page

JAN '06

Photocopies only

PROJECTS • A "Tiptronic-Style" Gear Indicator • Sunset Switch • PIC Ambilux • Current Clamp Adapter For Multimeters

FEATURES • Teach-In 2006 – Part 3 • Circuit Surgery • Techno Talk • Practically Speaking • PIC 'N' Mix • NetWork – The Internet Page

FEB '06 Photocopies only

PROJECTS • Highly Flexible Keypad Alarm • Active 3-way Crossover • Status Monitor • Jazzy Heart.

FEATURES • Teach-In 2006 – Part 4 • Techno Talk • Circuit Surgery • Interface • PIC-'N'-Mix • Network – The Internet Page

MAR '06

PROJECTS • PortaPAL Public Address Amplifier – Part 1 • Telescope Interface • Power Up • Video – Audio Booster

FEATURES • Teach-In 2006 – Part 5 • Practically Speaking • Circuit Surgery • Techno Talk • PIC-'N'-Mix • Net Work – The Internet Page



APR '06

PROJECTS • A Programmable Continuity Tester • Omni Pendulum • PortaPAL Public Address Amplifier – Part 2 • 'Smart' Slave Flash Trigger

FEATURES • Teach-In 2006 – Part 6 • Consumer Electronics Show • E-Chip Review • Techno Talk • PIC-'N'-Mix • Net Work – The Internet Page

MAY '06

PROJECTS • LED Lighting For Your Car • Smart Card Reader and Programmer • Nail Sniffer and Volts Hound • Digital Reaction Timer.

FEATURES • Teach-In 2006 – Part 7 • Practically Speaking • Ingenuity Unlimited • Circuit Surgery • Techno Talk • PIC 'N' Mix • Net Work – The Internet Page

BACK ISSUES ONLY £3.80 each inc. UK p&p.

Overseas prices £4.50 each surface mail, £5.50 each airmail.

We can also supply issues from earlier years: 2001 (except Feb., May, Aug., to Nov.), 2002 (except Feb., June, Aug. to Nov.), 2003 (except June), 2004 (except June, July, Oct. and Dec), 2005 (except Feb.), 2006 (except Jan., Feb.) Where we do not have an issue a photocopy of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOCOPIES – INDEXES

- ☐ Send back issues dated
☐ Send photocopies of (article title and issue date)
☐ Send copies of last five years indexes (£3.80 for five inc. p&p – Overseas £4.50 surface, £5.50 airmail)

Name

Address

Tel:

☐ I enclose cheque/P.O./bank draft to the value of £

☐ Please charge my Visa/Mastercard/Amex/Diners Club/Switch £

Card No. Switch Issue No.

Valid From Card Expiry Date Card Security Code

(The last 3 digits on or just under the signature strip)

SEND TO: **Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH21 9ND.**

Tel: 01202 873872. Fax: 01202 874562.

E-mail: orders@epemag.wimborne.co.uk

On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

M06/06

STORE YOUR BACK ISSUES ON CD-ROMS



**VOL 13
NOW AVAILABLE**

**ONLY
£14.45 each**
including VAT
and p&p


A great way to buy **EPE Back Issues** – our CD-ROMs contain back issues from our **EPE Online** website plus bonus articles, all the relevant PIC software and web links. Note: no free gifts are included. All this for just £14.45 each including postage and packing.

- VOL 1: BACK ISSUES** – January 1999 to June 1999
Plus some bonus material from Nov and Dec 1998
- VOL 2: BACK ISSUES** – July 1999 to December 1999
- VOL 3: BACK ISSUES** – January 2000 to June 2000
- VOL 4: BACK ISSUES** – July 2000 to December 2000
- VOL 5: BACK ISSUES** – January 2001 to June 2001
- VOL 6: BACK ISSUES** – July 2001 to December 2001
- VOL 7: BACK ISSUES** – January 2002 to June 2002
- VOL 8: BACK ISSUES** – July 2002 to December 2002
- VOL 9: BACK ISSUES** – January 2003 to June 2003
- VOL 10: BACK ISSUES** – July 2003 to December 2003
- VOL 11: BACK ISSUES** – January 2004 to June 2004
- VOL 12: BACK ISSUES** – July 2004 to December 2004
- VOL 13: BACK ISSUES** – January 2005 to June 2005

Order on-line from

[www.epemag.wimborne.co.uk/
shopdoor.htm](http://www.epemag.wimborne.co.uk/shopdoor.htm)

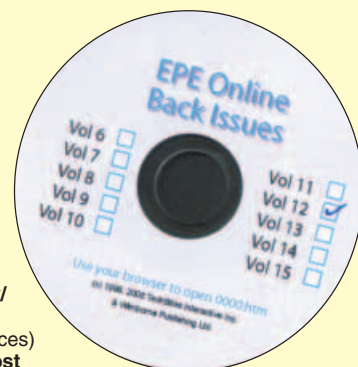or www.epemag.com (USA \$ prices)
or by phone, Fax, E-mail or Post



NOTE: These CD-ROMs are suitable for use on any PC with a CD-ROM drive. They require Adobe Acrobat Reader (available free from the Internet – www.adobe.com/acrobat)

WHAT IS INCLUDED

All volumes include the **EPE Online** editorial content of every listed issue, plus all the available **PIC Project Codes** for the PIC projects published in those issues.

Note: Some supplements etc. can be downloaded free from the Library on the **EPE Online** website at www.epemag.com. No advertisements are included in Volumes 1 and 2; from Volume 5 onwards the available relevant software for *Interface* articles is also included.

EXTRA ARTICLES – ON ALL VOLUMES

BASIC SOLDERING GUIDE – Alan Winstanley's internationally acclaimed fully illustrated guide. **UNDERSTANDING PASSIVE COMPONENTS** – Introduction to the basic principles of passive components. **HOW TO USE INTELLIGENT L.C.D.s**, by Julian Ilett – An utterly practical guide to interfacing and programming intelligent liquid crystal display modules. **PhyzyB COMPUTERS BONUS ARTICLE 1** – Signed and Unsigned Binary Numbers. By Clive "Max" Maxfield and Alvin Brown. **PhyzyB COMPUTERS BONUS ARTICLE 2** – Creating an Event Counter. By Clive "Max" Maxfield and Alvin Brown. **INTERGRAPH COMPUTER SYSTEMS 3D GRAPHICS** – A chapter from Intergraph's book that explains computer graphics technology. **FROM RUSSIA WITH LOVE**, by Barry Fox – Russian rockets launching American Satellites. **PC ENGINES**, by Ernest Flint – The evolution of Intel's microprocessors. **THE END TO ALL DISEASE**, by Aubrey Scoon – The original work of Rife. **COLLECTING AND RESTORING VINTAGE RADIOS**, by Paul Stenning. **THE LIFE & WORKS OF KONRAD ZUSE** – a brilliant pioneer in the evolution of computers. A bonus article on his life and work written by his eldest son, including many previously unpublished photographs.

Note: Some of the **EXTRA ARTICLES** require WinZip to unzip them.

BACK ISSUES CD-ROM ORDER FORM

Please send me the following Back Issue CD-ROMs. Volume Numbers:

Price £14.45 each – includes postage to anywhere in the world.

Name

Address

Post Code

☐ I enclose cheque/P.O./bank draft to the value of £

☐ Please charge my Visa/Mastercard/Amex/Diners

Club/Maestro

£

Card No.

Card Security Code (The last 3 digits on or just under the signature strip)

Valid From Expiry Date

Maestro Issue No.

SEND TO: **Everyday Practical Electronics,
Wimborne Publishing Ltd.,
408 Wimborne Road East, Ferndown, Dorset BH22 9ND.**

Tel: 01202 873872. Fax: 01202 874562.
E-mail: orders@epemag.wimborne.co.uk

Payments must be by card or in £ Sterling – cheque or bank draft drawn on a UK bank.

Normally supplied within seven days of receipt of order.

PCB SERVICE

Printed circuit boards for most recent *EPE* constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday Practical Electronics, Wimborne Publishing Ltd., 408 Wimborne Road East, Ferndown, Dorset BH22 9ND. Tel: 01202 873872; Fax 01202 874562; Email: orders@epemag.wimborne.co.uk. On-line Shop: www.epemag.wimborne.co.uk/shopdoor.htm.** Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Back numbers or photocopies of articles are available if required – see the *Back Issues* page for details. We do not supply kits or components for our projects.

Please check price and availability in the latest issue.
A large number of older boards are listed on our website.
Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Super Vibration Switch	DEC '04	474 £4.75
Wind Direction Indicator		475 £6.18
★PIC Flasher Mk2 – Control Board		476 £4.75
– Transmitter		477 £4.44
– Multipurpose Board		478 £4.75
– Simple Cycler		479 £4.44
– Luxeon V Controller		480 £4.44
– Power Supply		473 £4.76
Light Detector	JAN '05	481 £4.44
★Camera Watch		482 £6.03
Gate Alarm – Oscillator		483 £4.92
– Delay/Timer		484 £4.92
★Sneaky – Transmitter	FEB '05	485 £4.60
– Receiver		486 £4.91
★PIC Electric Mk2 – Control		487 £5.87
– Sensor		488 £5.71
Sound Card Mixer		489 £7.29
Headphone Monitor	MAR '05	490 £5.71
EPE Cat Flap		491 £6.02
★Bingo Box – Main		492 £9.04
– Big Digit Display		493 £10.31
Spontaflex Radio– Tuner	APR '05	494 £5.55
– Coil Pack		495 £5.71
– Audio Amplifier		496 £5.55
– Tuning Capacitor Board		497 £6.18
★Safety Interface		498 £5.39
Back-To-Basics 1– Fridge/Freezer Door Alarm		499 £6.66
★Crossword Solver	MAY '05	500 £5.14
20W Amplifier Module		501 £5.39
Back-To-Basics 2 – Water Level Alarm		502 £5.87
– Burglar Alarm		503 £6.66
★PIC Ultrasonic Scanner	JUN '05	504 £5.87
★Radio Control Model Switcher		505 £5.55
Back-To-Basics 3 – Scarecrow		506 £6.66
– Digital Lock		507 £6.66
CompactFlash Interface Board		508 £5.71
LF/VLF Converter	JUL '05	509 £5.86
– Fixed Capacitor Board		510 £5.23
– Mixer/Oscillator Board		511 £5.23
– Buffer Amplifier		512 £4.28
– Q-Multiplier		513 £6.34
– Tuning Capacitor Board		514 £6.02
Back-To-Basics 4 – Doorchime		515 £6.82
– Electronic Dice		516 £6.66
★Cybervox		517 £6.02
Multi-Clap Switch		518 £5.23
Audio System	AUG '05	519 £6.02
– Preamplifier		520 £7.14
– Mic. Supply Board		521 £7.45
– Power Amp		522 £5.87
★Pain Monitor		523 £5.71
MotorAmp		524 £5.23
Back-To-Basics 5 – Kitchen Timer		525 £6.19
– Room Thermometer		526 £5.55
All-Band Radio – Full Version	SEPT '05	527 £6.19
– Mini Version		528 £5.87
★Multicore Cable Tester – Main		529 £6.19
– Active		530 £8.72
Back-To-Basics 6 – Daily Reminder		531 £6.98
– Whistle Switch		532 £5.71
★Model Railway Signal Control		533 £5.55
★Snooker/Darts Scoreboard		534 £6.02
Photic Phone – Transmitter	OCT '05	535 £6.19
– Receiver		536 £6.19
Back-To-Basics 7 – Parking Radar		537 £6.82
– Telephone Switch		538 £6.66
★Halloween Howler		539 £6.18
★PIC-Based USB Interface		540 £5.87
★PIC Chromatone	NOV '05	541 £6.35
Back-To-Basics 8 – Noughts and Crosses Enigma		542 £6.66
– Weather Vane Repeater		543 £6.18
★Multi-Function R/C Switch		544 £5.87
★Speed Camera Watch Mk2		545 £6.35

PROJECT TITLE	Order Code	Cost
Solid-State Valve Power Supply	DEC '05	542 £6.35
★Vehicle Frost Box Mk2		543 £5.71
★Propeller Monitor		544 £6.02
Solid-State Hammond		545 £6.18
★PIC Ambilux	JAN '06	546 £5.71
Sunset Switch		547 £6.98
Current Clamp Adaptor for Multimeters		548 £5.39
★Tiptronic-Style Gear Indicator		549 £7.61
– Micro Board		550 } per set
– Display Board		551 }
– Hall Speed Board		
★Keypad Alarm	FEB '06	552 £6.02
3-Way Active Crossover		553 £9.20
Jazzy Heart		554 £6.02
Status Monitor – Transmitter		555 £7.61
– Reciever		556 }
Power Up	MAR '06	557 £6.82
Video/Audio Booster (double-sided)		558 £12.00
★Telescope Interface		559 £6.50
'Smart' Slave Flash	APR '06	560 £6.18
Programmable Continuity Tester		561 £5.87
PortaPAL		562 £6.18
– Microphone Board		563 £5.87
– Auxiliary Board		564 £8.56
– Main Board		565 £6.66
– Charger Board		566 £6.34
Omni Pendulum		567 £7.61
Smart Card Reader/Programmer	MAY '06	568 £14.75
LED Lighting For Your Car (set of 15 boards)		569 £7.13
Digital Reaction Timer		570 £5.71
Poor Man's Metal Locator	JUN '06	571 £7.77
★Digital Instrument Display for Cars		572 } pair
– Micro Board		573 }
– Display Board		574 }
Widgy Box		575 £7.29
Phone Ring & Test		576 £6.82

EPE SOFTWARE

★ All software programs for *EPE* Projects marked with an asterisk, and others previously published, can be downloaded free from our Downloads site, accessible via our home page at: www.epemag.co.uk.

PCB MASTERS

PCB masters for boards published from the March '06 issue onwards can also be downloaded from our UK website (www.epemag.co.uk); go to the "Downloads" section.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name

Address

Tel. No.

I enclose payment of £..... (cheque/PO in £ sterling only) to:



**Everyday
Practical Electronics**



**MasterCard, Amex, Diners
Club, Visa or Switch/Maestro**



Card No.

Valid From Expiry Date

Card Security Code Switch/Maestro Issue No
(The last 3 digits on or just under the signature strip)

Signature

NOTE: You can also order p.c.b.s by phone, Fax, Email or via our
Web site on a secure server:

<http://www.epemag.wimborne.co.uk/shopdoor.htm>

NEXT MONTH

PIC SUDOKU

A hand held PIC-based unit that generates Sudoku puzzles, plus optional PC software which automatically solves most Sudoku puzzles.

PIC INFRA-RED REMOTE RECEIVER

Use a universal remote control to power up your PC remotely, to control the PC DVD player or MP3 player or, if you are a keen programmer, to control just about any Windows application.

DIGITAL INSTRUMENT DISPLAY FOR CARS PART 2

Connecting different sensors to the unit plus calibration procedure.

A DIRT CHEAP HIGH CURRENT BENCH SUPPLY

This article tells you how to modify an old PC power supply to provide 13-5V at up to 18A for a bench supply. But be warned this is not a project for the inexperienced constructor.

JULY '06 ISSUE ON SALE JUNE 8



ADVERTISERS INDEX

AGAR	.67
AUDON ELECTRONICS	.70
BETA-LAYOUT	.67
BREADBOARDING SYSTEMS	.15
BRUNNING SOFTWARE	.50
BULL GROUP	Cover (ii)
DISPLAY ELECTRONICS	.80
EASYDAQ	.70
EASYSYNC	.64
ESR ELECTRONIC COMPONENTS	.6
FERN ELECTRONIC	.62
JAYCAR ELECTRONICS	.40/41
JPG ELECTRONICS	.80
LABCENTER	Cover (iv)
LASER	.67
MAGENTA ELECTRONICS	.5
MICROCHIP	.27
MILFORD INSTRUMENTS	.63
NURVE NETWORKS LLC	.17
OBD CABLES	.70
PEAK ELECTRONIC DESIGN	Cover (iii)
PICO TECHNOLOGY	.4
QUASAR ELECTRONICS	.2/3
RAPID ELECTRONICS	.52
SHERWOOD ELECTRONICS	.70
STEWART OF READING	.4

ADVERTISEMENT OFFICES:

408 WIMBORNE ROAD EAST, FERNDOWN, DORSET BH22 9ND

PHONE: 01202 873872

FAX: 01202 874562

EMAIL: epeads@wimborne.co.uk

For Editorial address and phone numbers see page 7

Everyday Practical Electronics, periodicals pending, ISSN 0262 3617 is published twelve times a year by Wimborne Publishing Ltd., USA agent USACAN at 1320 Route 9, Champlain, NY 12919. Subscription price in US \$60(US) per annum. Periodicals postage paid at Champlain NY and at additional mailing offices. POSTMASTER: Send USA and Canada address changes to Everyday Practical Electronics, c/o Express Mag., PO Box 2769, Plattsburgh, NY, USA 12901-0239.